

EE101 Tutorial 5 Solution Sheet

1.

Given,
 2. $V_{out} = \alpha \tanh[\beta(V_{in1} - V_{in2})]$

For finding small-signal gain,


$$\frac{dV_{out}}{d(V_{in1} - V_{in2})} = \frac{d}{d(V_{in1} - V_{in2})} [\alpha \tanh[\beta(V_{in1} - V_{in2})]]$$

$$= \alpha \frac{d}{d(V_{in1} - V_{in2})} [\tanh[\beta(V_{in1} - V_{in2})]]$$

$$= \alpha \frac{d}{d(V_{in1} - V_{in2})} \left[\beta(V_{in1} - V_{in2}) - \frac{1}{3} (\beta(V_{in1} - V_{in2}))^3 + \dots \right]$$

$$\left(\because \tanh x = x - \frac{1}{3} x^3 + \frac{x^5}{15} - \dots \right)$$

$$= \alpha \beta //$$

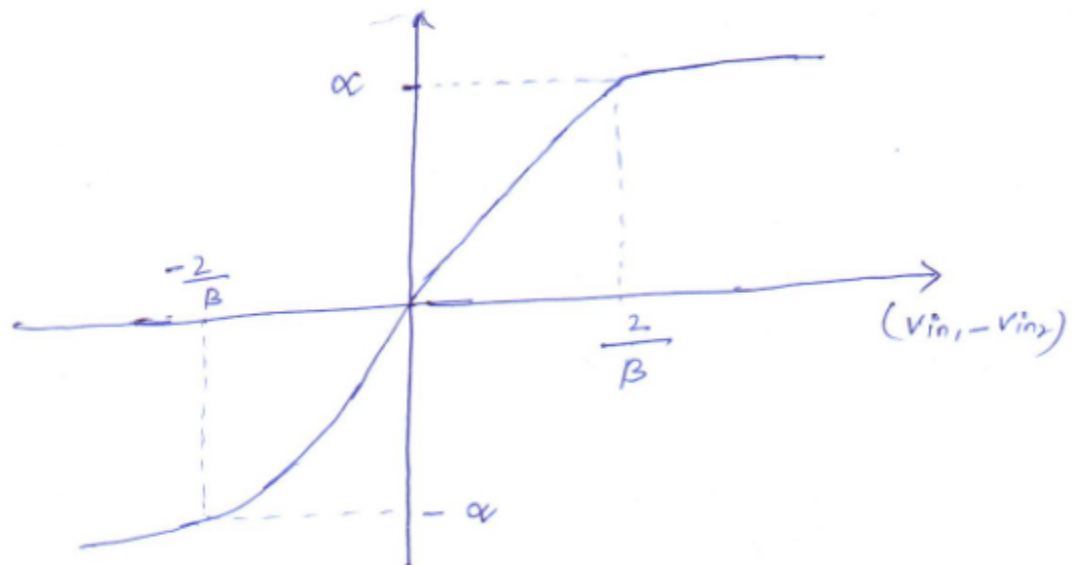

2.

$$\begin{aligned}
V_- &= V_+ = V_{in} \\
V_- &= \frac{R_4 \parallel (R_2 + R_3)}{R_1 + R_4 \parallel (R_2 + R_3)} \frac{R_2}{R_2 + R_3} V_{out} = V_{in} \\
\frac{V_{out}}{V_{in}} &= \left[\frac{R_4 \parallel (R_2 + R_3)}{R_1 + R_4 \parallel (R_2 + R_3)} \frac{R_2}{R_2 + R_3} \right]^{-1} \\
&= \boxed{\frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]}}
\end{aligned}$$

If $R_1 \rightarrow 0$, we expect the result to be:

$$\begin{aligned}
V_{in} &= \frac{R_2}{R_2 + R_3} V_{out} \\
\left. \frac{V_{out}}{V_{in}} \right|_{R_1=0} &= \frac{R_2 + R_3}{R_2} = 1 + \frac{R_3}{R_2}
\end{aligned}$$

Taking limit of the original expression as $R_1 \rightarrow 0$, we have:

$$\begin{aligned}
\lim_{R_1 \rightarrow 0} \frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]} &= \frac{(R_2 + R_3) [R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]} \\
&= 1 + \frac{R_3}{R_2}
\end{aligned}$$

This agrees with the expected result. Likewise, if $R_3 \rightarrow 0$, we expect the result to be:


$$\begin{aligned}
V_{in} &= \frac{R_2 \parallel R_4}{R_1 + R_2 \parallel R_4} V_{out} \\
\left. \frac{V_{out}}{V_{in}} \right|_{R_3=0} &= \frac{R_1 + R_2 \parallel R_4}{R_2 \parallel R_4} \\
&= 1 + \frac{R_1}{R_2 \parallel R_4}
\end{aligned}$$

Taking the limit of the original expression as $R_3 \rightarrow 0$, we have:

$$\begin{aligned}
\lim_{R_3 \rightarrow 0} \frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]} &= \frac{R_2 (R_1 + R_2 \parallel R_4)}{R_2 (R_2 \parallel R_4)} \\
&= \frac{R_1 + R_2 \parallel R_4}{R_2 \parallel R_4} \\
&= 1 + \frac{R_1}{R_2 \parallel R_4}
\end{aligned}$$

3.

3. Since op-amp is inverting amp:-

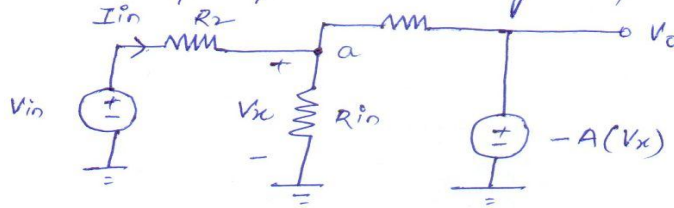

Also, $V_o = -AV_x$

$$\frac{V_{in} - V_x}{R_2} + \frac{V_o - V_x}{R_1} = \frac{V_x}{R_{in}}$$

Putting $V_x = \frac{V_o}{-A}$

$$\frac{V_{in} - \left(\frac{V_o}{-A}\right)}{R_2} + \frac{V_o - \left(\frac{V_o}{-A}\right)}{R_1} = \frac{\left(\frac{V_o}{-A}\right)}{R_{in}}$$

$$\Rightarrow \frac{V_{in}}{R_2} = -\frac{V_o}{A} \frac{1}{R_2} - \frac{V_o}{R_1} - \frac{V_o}{AR_1} - \frac{V_o}{AR_{in}}$$

$$\Rightarrow \frac{V_{in}}{R_2} = -\frac{V_o}{A} \left[\frac{1}{R_2} - \frac{A}{R_1} - \frac{1}{R_1} - \frac{1}{R_{in}} \right]$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} = \frac{-A R_{in} R_1}{R_1 R_{in} + R_2 R_{in} A + R_2 R_{in} + R_1 R_2}}$$

Input Impedance (Z_{in}) = $\frac{V_{in}}{I_{in}}$

Applying KCL at node a: $I_{in} - \frac{V_x}{R_{in}} + \frac{(-AV_x - V_x)}{R_1} = 0$

$$\Rightarrow \boxed{I_{in} = V_x \left[\frac{1}{R_{in}} + \frac{(A+1)}{R_1} \right]}$$

Also, $V_x = V_{in} - I_{in} R_2$

$$I_{in} = (V_{in} - I_{in} R_2) \left[\frac{1}{R_{in}} + \frac{(A+1)}{R_1} \right] = \frac{V_{in}}{R_{in}} \left[\frac{1}{R_{in}} + \frac{(A+1)}{R_1} \right] - I_{in} R_2 \left[\frac{1}{R_{in}} + \frac{(A+1)}{R_1} \right]$$

$$\Rightarrow \boxed{Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1)}{1 + A+1}} \quad //$$

4.

$$V_+ = V_- \text{ (since } A_0 = \infty \text{)}$$

$$V_X = \frac{R_3}{R_3 + R_4} V_{out} = \frac{R_2}{R_1 + R_2} (V_{out} - V_{in}) + V_{in}$$

$$V_{out} \left(\frac{R_3}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right) = V_{in} \left(1 - \frac{R_2}{R_1 + R_2} \right)$$

$$V_{out} \left[\frac{R_3 (R_1 + R_2) - R_2 (R_3 + R_4)}{(R_1 + R_2) (R_3 + R_4)} \right] = V_{in} \left(\frac{R_1}{R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \boxed{\frac{R_1 (R_3 + R_4)}{R_3 (R_1 + R_2) - R_2 (R_3 + R_4)}}$$

5.


$$5. \quad V_{out} = -\frac{1}{R_1 C_1} \int V_{in} dt$$

$$= -\frac{1}{R_1 C_1} \int V_0 \sin \omega t dt$$

$$= -\frac{V_0}{R_1 C_1 \omega} \times \cos \omega t$$

$$\therefore \boxed{\text{Amplitude of output signal} = \frac{V_0}{R_1 C_1 \omega}}$$

6.

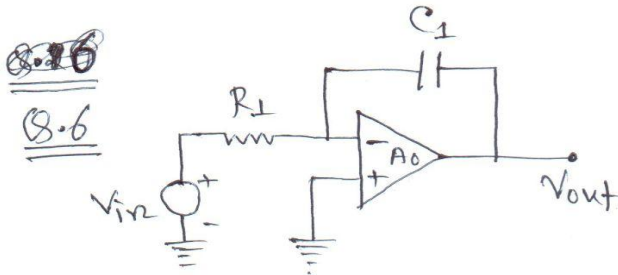

Given!

$$A = \text{Gain} = 10$$

$$A_0 \rightarrow \infty \text{ \& \; } R_1 C_1 = 10 \text{ ns}$$

$$f = ??$$

Output of inverting amplifier,

$$V_{out} = - \frac{X_c}{R_1} V_{in} = - \frac{(1/s\omega)}{R_1} V_{in}$$

$$= - \frac{1}{s R_1 C_1} V_{in}$$

$$= - \frac{1}{(j\omega) R_1 C_1} V_{in}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = A = \frac{1}{\omega R_1 C_1} = 10 \text{ (Given)}$$


$$\therefore 2\pi f R_1 C_1 = \frac{1}{10}$$

$$\Rightarrow f = \frac{1}{10 \times 2\pi \times 10 \times 10^{-9}}$$

$$= \frac{10^7}{2\pi}$$

$$\boxed{f = 1.59 \text{ MHz}}$$

7.

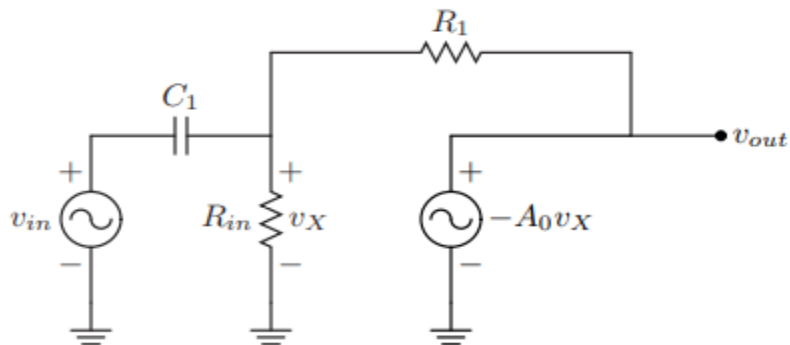

$$v_{out} = -A_0 v_X$$

$$v_X = \left[(v_{in} - v_X) s C_1 - \frac{v_X - v_{out}}{R_1} \right] R_{in}$$

$$v_X \left[1 + s R_{in} C_1 + \frac{R_{in}}{R_1} \right] = v_{in} s R_{in} C_1 + v_{out} \frac{R_{in}}{R_1}$$

$$v_X = \frac{v_{in} s R_{in} C_1 + v_{out} \frac{R_{in}}{R_1}}{1 + s R_{in} C_1 + \frac{R_{in}}{R_1}}$$

$$v_{out} = -A_0 \frac{v_{in} s R_{in} C_1 + v_{out} \frac{R_{in}}{R_1}}{1 + s R_{in} C_1 + \frac{R_{in}}{R_1}}$$

$$v_{out} \left[1 + \frac{A_0 \frac{R_{in}}{R_1}}{1 + s R_{in} C_1 + \frac{R_{in}}{R_1}} \right] = -v_{in} \frac{s R_{in} C_1 A_0}{1 + s R_{in} C_1 + \frac{R_{in}}{R_1}}$$

$$v_{out} \left[\frac{1 + s R_{in} C_1 + (1 + A_0) \frac{R_{in}}{R_1}}{1 + s R_{in} C_1 + \frac{R_{in}}{R_1}} \right] = -v_{in} \frac{s R_{in} C_1 A_0}{1 + s R_{in} C_1 + \frac{R_{in}}{R_1}}$$

$$v_{out} \left[1 + s R_{in} C_1 + (1 + A_0) \frac{R_{in}}{R_1} \right] = -v_{in} s R_{in} C_1 A_0$$

$$\frac{v_{out}}{v_{in}} = \boxed{-\frac{s R_1 R_{in} C_1 A_0}{R_1 + s R_1 R_{in} C_1 + (1 + A_0) R_{in}}}$$

$$\lim_{A_0 \rightarrow \infty} \frac{v_{out}}{v_{in}} = -s R_1 C_1$$


8.

$$\begin{aligned}
v_{out} &= -A_0 v_- \\
v_- &= v_{in} + (v_{out} - v_{in}) \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \\
v_{out} &= -A_0 \left[v_{in} + (v_{out} - v_{in}) \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \right] \\
v_{out} \left[1 + A_0 \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \right] &= -v_{in} A_0 \left[1 - \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \right] \\
v_{out} \frac{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) + A_0 \left(\frac{1}{sC_1} \parallel R_1\right)}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} &= -v_{in} A_0 \frac{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) - \left(\frac{1}{sC_1} \parallel R_1\right)}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \\
v_{out} \left\{ (1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) \right\} &= -v_{in} A_0 \left(\frac{1}{sC_2} \parallel R_2\right) \\
\frac{v_{out}}{v_{in}} &= \boxed{-A_0 \frac{\frac{1}{sC_2} \parallel R_2}{(1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)}}
\end{aligned}$$

Unity gain occurs when the numerator and denominator are the same (note that we can drop the negative sign since we only care about the magnitude of the gain):

$$\begin{aligned}
A_0 \left(\frac{1}{sC_2} \parallel R_2\right) &= (1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) \\
(A_0 - 1) \left(\frac{1}{sC_2} \parallel R_2\right) &= (1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) \\
\frac{\left(\frac{1}{sC_2} \parallel R_2\right)}{\left(\frac{1}{sC_1} \parallel R_1\right)} &\equiv \frac{A_0 + 1}{A_0 - 1}
\end{aligned}$$

9.

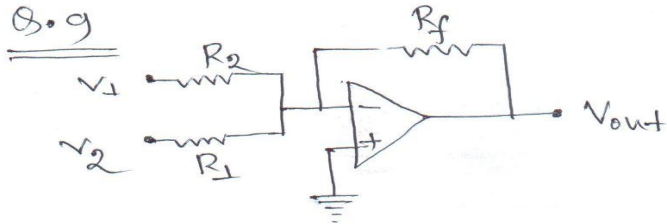


Given:

$$\begin{aligned} V_1 &= V_0 \sin \omega t \\ V_2 &= V_0 \sin(3\omega t) \\ R_1 &= R_2 = R \text{ (Say)} \\ A_o &= \infty \end{aligned}$$

we know the output of adder circuit,

$$\begin{aligned} V_{out} &= -R_f \left(\frac{V_1}{R_2} + \frac{V_2}{R_1} \right) \\ &= -\frac{R_f}{R} (V_1 + V_2) \quad [\because R_1 = R_2 = R] \\ &= -\frac{R_f V_0}{R} (\sin \omega t + \sin 3\omega t) \\ &= -\frac{2R_f V_0}{R} \left(\sin \left(\frac{3\omega t + \omega t}{2} \right) \times \cos \left(\frac{3\omega t - \omega t}{2} \right) \right) \\ \boxed{V_{out} = -\left(A' \sin 2\omega t \right) \cdot \cos \omega t} &; A' = \frac{2R_f V_0}{R} \\ &= -V_{out}' \end{aligned}$$

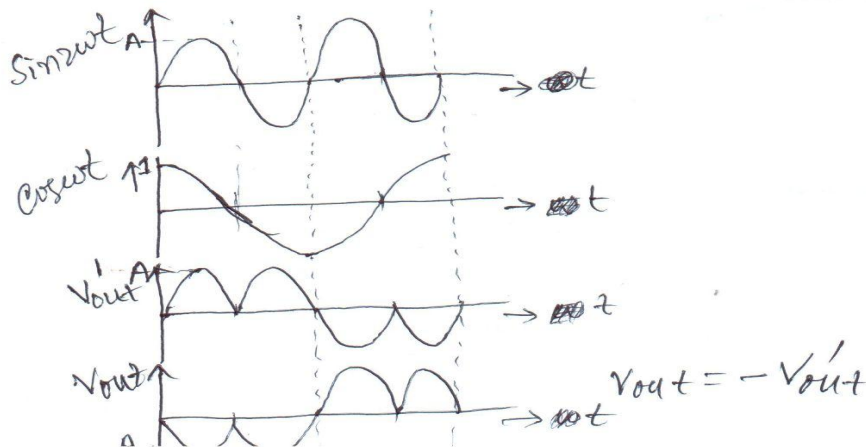

10.

$$V_Y = \begin{cases} V_{in} - V_{D,on} & V_{in} < 0 \\ V_{DD} & V_{in} > 0 \end{cases} V_{out} = \begin{cases} V_{in} & V_{in} < 0 \\ 0 & V_{in} > 0 \end{cases} I_{D1} = \begin{cases} \frac{V_{in}}{R_1} & V_{in} < 0 \\ 0 & V_{in} > 0 \end{cases}$$

Plotting $V_Y(t)$ and $V_{out}(t)$, we have

