
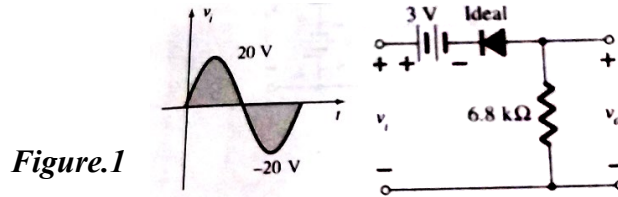


EE101 Tutorial 3

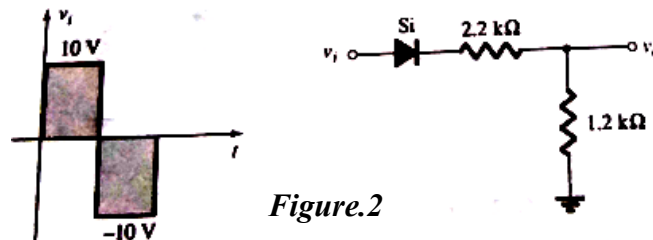
Q1. Determine V_o for network of Figure 1 for the input shown.




Q2. Determine V_o for network of Figure.2 for the input shown.



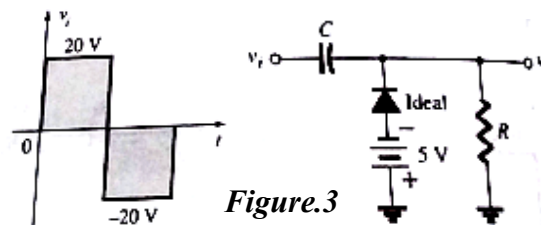Q3. Sketch V_o for network of Figure.3 for the input shown.




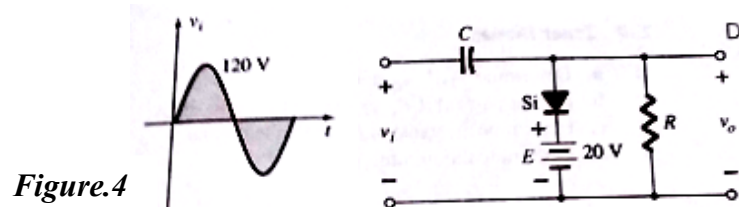Q4. Sketch V_o for network of Figure.4 for the input shown. Would it be a good approximation to consider the Diode to be ideal for configuration? Why?



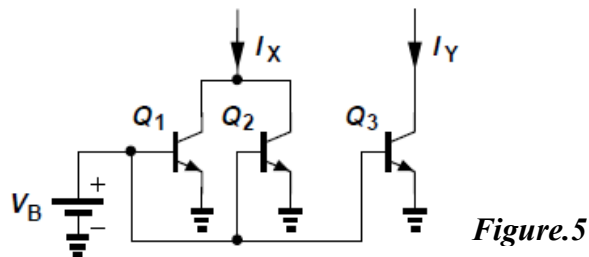Q5. In the circuit shown in the Figure.5, $I_{S1} = I_{S2} = 3 \times 10^{-16} \text{ A}$.

- Calculate V_B such that $I_X = 1 \text{ mA}$.
- With the value of V_B found in (a), choose I_{S3} such that $I_Y = 2.5 \text{ mA}$.



Q6. In the circuit shown in the Figure.6.

- If $I_{S1} = 2I_{S2} = 5 \times 10^{-16} \text{ A}$, Determine V_B such that $I_X = 1.2 \text{ mA}$.
- What value of R_C places the transistors at the edge of the active mode?

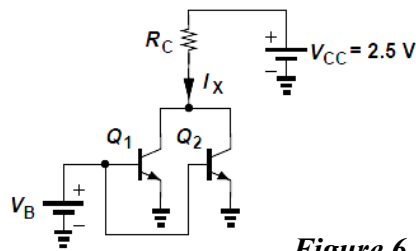


Figure.6

Q7. Calculate V_X in Figure.7 if $I_S = 6 \times 10^{-16} \text{ A}$.

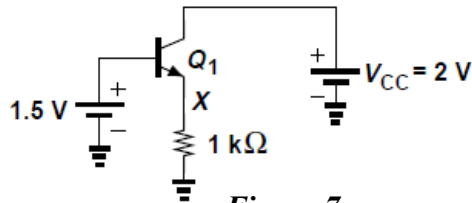


Figure.7

Q8. Consider the circuit shown in Figure.8, assuming $\beta = 100$ and $I_S = 7 \times 10^{-16} \text{ A}$. If $R_1 = 10 \text{ k}\Omega$, Determine V_B such that $I_C = 1 \text{ mA}$.

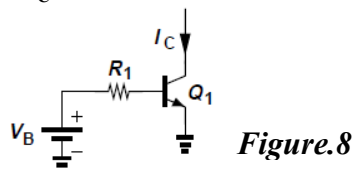


Figure.8

Q9. In the circuit of Figure.9, $I_{S1} = 3 \times 10^{-16} \text{ A}$, $I_{S2} = 5 \times 10^{-16} \text{ A}$, $\beta_1 = \beta_2 = 100$, $R_1 = 5 \text{ k}\Omega$, and $V_B = 800 \text{ mV}$. Calculate I_X and I_Y .

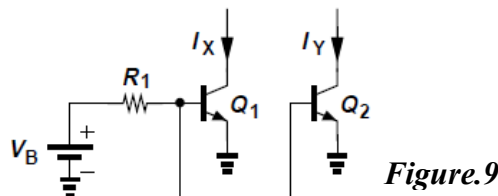


Figure.9

Q10. Most applications require that the transconductance of a transistor remain relatively constant as the signal level varies. Of course, since the signal changes the collector current, $g_m = I_C/V_T$ does vary. Nonetheless, proper design ensures negligible variation, e.g., $\pm 10\%$. If a bipolar device is biased at $I_C = 1 \text{ mA}$, what is the largest change in V_{BE} that guarantees only $\pm 10\%$ variation in g_m ?

Q11. Assume $I_S = 2 \times 10^{-17} \text{ A}$, $V_A = \infty$, and $\beta = 100$ in Figure.10. What is the maximum value of R_C if the collector-base must experience a forward bias of less than 200 mV ?

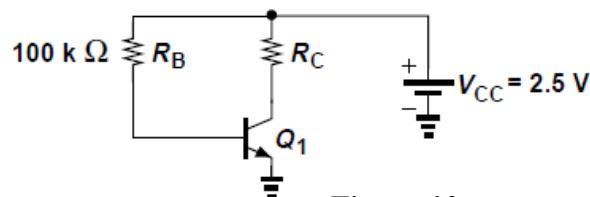


Figure.10