


## EE101 Tutorial 12

Topics: RC, RL and RLC Circuits

1.

### Chapter 7, Problem 7.

Assuming that the switch in Fig. 7.87 has been in position *A* for a long time and is moved to position *B* at  $t=0$ , find  $v_o(t)$  for  $t \geq 0$ .

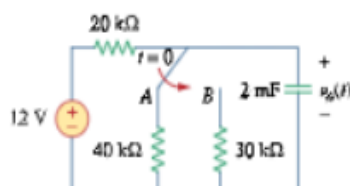

**Figure 7.87**  
For Prob. 7.7.

### Chapter 7, Solution 7.

When the switch is at position *A*, the circuit reaches steady state. By voltage division,

$$v_o(0) = \frac{40}{40 + 20}(12\text{ V}) = 8\text{ V}$$

When the switch is at position *B*, the circuit reaches steady state. By voltage division,

$$v_o(\infty) = \frac{30}{30 + 20}(12\text{ V}) = 7.2\text{ V}$$

$$R_{Th} = 20\text{ k} \parallel 30\text{ k} = \frac{20 \times 30}{50} = 12\text{ k}\Omega$$


$$\tau = R_{Th}C = 12 \times 10^3 \times 2 \times 10^{-3} = 24\text{ s}$$

$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau} = 7.2 + (8 - 7.2)e^{-t/24} = \underline{7.2 + 0.8e^{-t/24}\text{ V}}$$

2.

### Chapter 7, Problem 10.

For the circuit in Fig. 7.90, find  $v_o(t)$  for  $t > 0$ . Determine the time necessary for the capacitor voltage to decay to one-third of its value at  $t = 0$ .

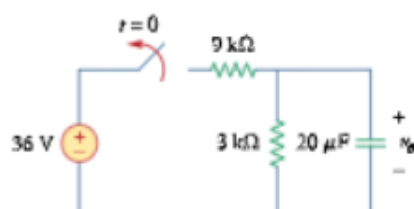

**Figure 7.90**  
For Prob. 7.10.

### Chapter 7, Solution 10.

$$\text{For } t < 0, \quad v(0^-) = \frac{3}{3+9}(36\text{ V}) = \underline{9\text{ V}}$$

For  $t > 0$ , we have a source-free RC circuit

$$\tau = RC = 3 \times 10^3 \times 20 \times 10^{-6} = 0.06\text{ s}$$

$$v_o(t) = \underline{9e^{-16.667t}\text{ V}}$$

Let the time be  $t_0$ .

$$3 = 9e^{-16.667t_0} \text{ or } e^{16.667t_0} = 9/3 = 3$$

$$t_0 = \ln(3)/16.667 = \underline{\underline{65.92\text{ ms}}}.$$

3.

### Chapter 7, Problem 11.

For the circuit in Fig. 7.91, find  $i_o$  for  $t > 0$ .


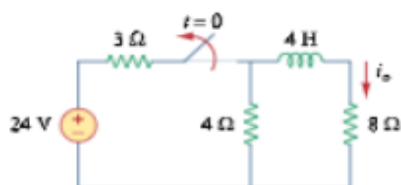


Figure 7.91

For Prob. 7.11.
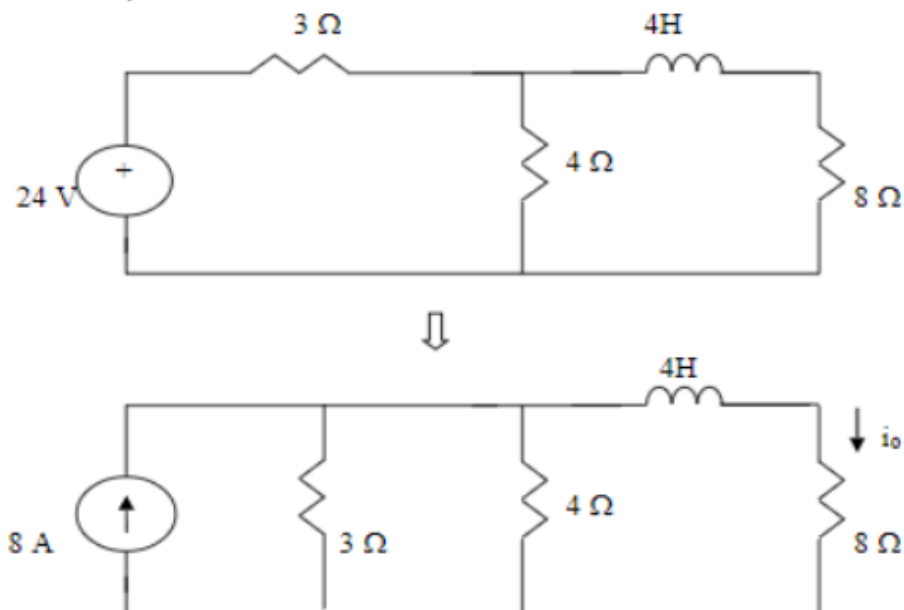
### Chapter 7, Solution 11.

For  $t < 0$ , we have the circuit shown below.



$$3//4 = 4 \times 3 / 7 = 1.7143$$

$$i_o(0^-) = \frac{1.7143}{1.7143 + 8} (8) = 1.4118 \text{ A}$$

For  $t > 0$ , we have a source-free RL circuit.

$$\tau = \frac{L}{R} = \frac{4}{4 + 8} = 1/3$$

$$i_o(t) = i_o(0) e^{-t/\tau} = 1.4118 e^{-3t} \text{ A}$$

4.

### Chapter 7, Problem 13.

In the circuit of Fig. 7.93,

$$v(t) = 20e^{-10^3 t} \text{ V}, \quad t > 0$$

$$i(t) = 4e^{-10^3 t} \text{ mA}, \quad t > 0$$

(a) Find  $R$ ,  $L$ , and  $\tau$ .

(b) Calculate the energy dissipated in the resistance for  $0 < t < 0.5 \text{ ms}$ .



Figure 7.93  
For Prob. 7.13.

### Chapter 7, Solution 13.

$$(a) \tau = \frac{1}{10^3} = 1 \text{ ms}$$

$$v = iR \longrightarrow 20e^{-1000t} = R \times 4e^{-1000t} \times 10^{-3}$$

$$\text{From this, } R = 20/4 \text{ k}\Omega = \underline{5 \text{ k}\Omega}$$

$$\text{But } \tau = \frac{L}{R} = \frac{1}{10^3} \longrightarrow L = \frac{5 \times 1000}{1000} = \underline{5 \text{ H}}$$


(b) The energy dissipated in the resistor is

$$\begin{aligned} w &= \int_0^t p \, dt = \int_0^t 80 \times 10^{-3} e^{-2 \times 10^3 t} \, dt = -\frac{80 \times 10^{-3}}{2 \times 10^3} e^{-2 \times 10^3 t} \bigg|_0^{0.5 \times 10^{-3}} \\ &= 40(1 - e^{-1}) \mu\text{J} = \underline{25.28 \mu\text{J}} \end{aligned}$$

5.

# Chapter 7, Problem 16.

Determine the time constant for each of the circuits in Fig. 7.96.

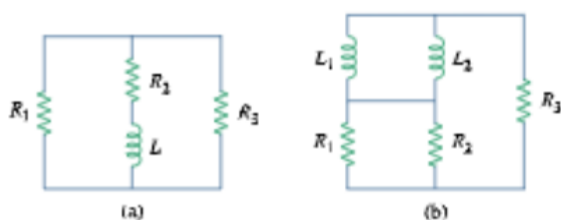

**Figure 7.96**  
For Prob. 7.16.

# Chapter 7, Solution 16.

$$\tau = \frac{L_{eq}}{R_{eq}}$$

$$(a) \quad L_{eq} = L \text{ and } R_{eq} = R_2 + \frac{R_1 R_3}{R_1 + R_3} = \frac{R_2(R_1 + R_3) + R_1 R_3}{R_1 + R_3}$$

$$\tau = \frac{L(R_1 + R_3)}{R_2(R_1 + R_3) + R_1 R_3}$$

$$(b) \quad \text{where } L_{eq} = \frac{L_1 L_2}{L_1 + L_2} \text{ and } R_{eq} = R_3 + \frac{R_1 R_2}{R_1 + R_2} = \frac{R_3(R_1 + R_2) + R_1 R_2}{R_1 + R_2}$$

$$\tau = \frac{L_1 L_2 (R_1 + R_2)}{(L_1 + L_2)(R_3(R_1 + R_2) + R_1 R_2)}$$

6.




# Chapter 7, Problem 19.

In the circuit of Fig. 7.99, find  $i(t)$  for  $t > 0$  if  $i(0) = 2$  A.



Figure 7.99  
For Prob. 7.19.

# Chapter 7, Solution 19.

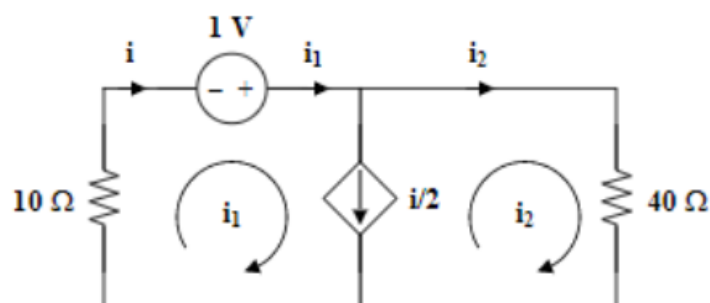

To find  $R_{th}$  we replace the inductor by a 1-V voltage source as shown above.

$$10i_1 - 1 + 40i_2 = 0$$

But  $i = i_2 + i/2$  and  $i = i_1$

i.e.  $i_1 = 2i_2 = i$

$$10i - 1 + 20i = 0 \longrightarrow i = \frac{1}{30}$$

$$R_{th} = \frac{1}{i} = 30 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{6}{30} = 0.2 \text{ s}$$

$$i(t) = \underline{2e^{-5t}u(t) \text{ A}}$$

7.

Chapter 7, Solution 39.

- (a) Before  $t = 0$ ,

$$v(t) = \frac{1}{4+1}(20) = \underline{4 \text{ V}}$$

After  $t = 0$ ,

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$\tau = RC = (4)(2) = 8, \quad v(0) = 4, \quad v(\infty) = 20$$

$$v(t) = 20 + (4 - 20)e^{-t/8}$$

$$v(t) = \underline{20 - 16e^{-t/8} \text{ V}}$$

- (b) Before  $t = 0$ ,  $v = v_1 + v_2$ , where  $v_1$  is due to the 12-V source and  $v_2$  is due to the 2-A source.

$$v_1 = 12 \text{ V}$$


To get  $v_2$ , transform the current source as shown in Fig. (a).

$$v_2 = -8 \text{ V}$$


Thus,

$$v = 12 - 8 = \underline{4 \text{ V}}$$

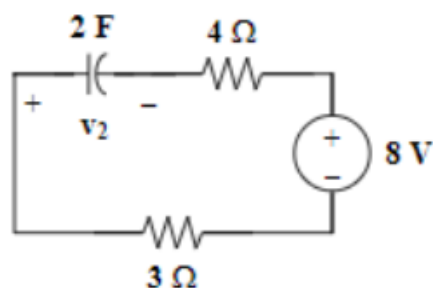After  $t = 0$ , the circuit becomes that shown in Fig. (b).



(a)

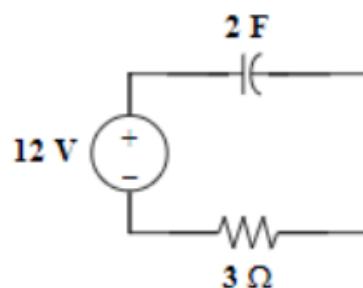

(b)

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(\infty) = 12, \quad v(0) = 4, \quad \tau = RC = (2)(3) = 6$$

$$v(t) = 12 + (4 - 12)e^{-t/6}$$

$$v(t) = \underline{12 - 8e^{-t/6} \text{ V}}$$

8.

### Chapter 7, Problem 55.

Find  $v(t)$  for  $t < 0$  and  $t > 0$  in the circuit of Fig. 7.121.


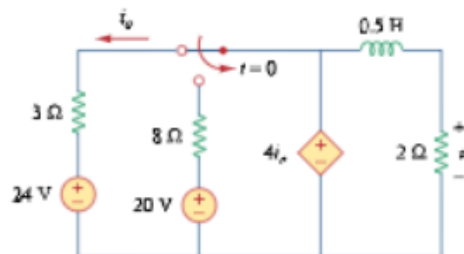


Figure 7.121

For Prob. 7.55.
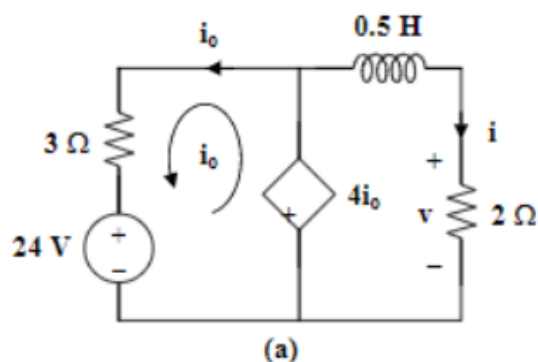
### Chapter 7, Solution 55.


For  $t < 0$ , consider the circuit shown in Fig. (a).



$$3i_o + 24 - 4i_o = 0 \longrightarrow i_o = 24$$

$$\underline{v(t) = 4i_o = 96 \text{ V}} \qquad i = \frac{v}{2} = 48 \text{ A}$$

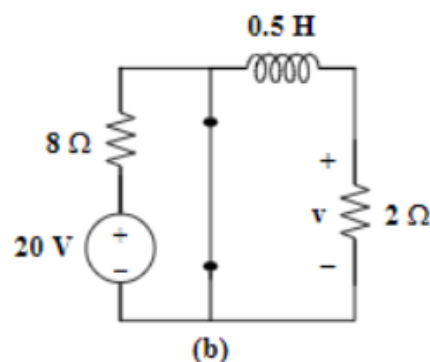For  $t > 0$ , consider the circuit in Fig. (b).



$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(0) = 48, \quad i(\infty) = 0$$

$$R_{th} = 2 \Omega, \quad \tau = \frac{L}{R_{th}} = \frac{0.5}{2} = \frac{1}{4}$$

$$i(t) = (48) e^{-4t}$$

$$\underline{v(t) = 2i(t) = 96 e^{-4t} u(t) \text{ V}}$$

9.

# Chapter 7, Problem 56.

For the network shown in Fig. 7.122, find  $v(t)$  for  $t > 0$ .

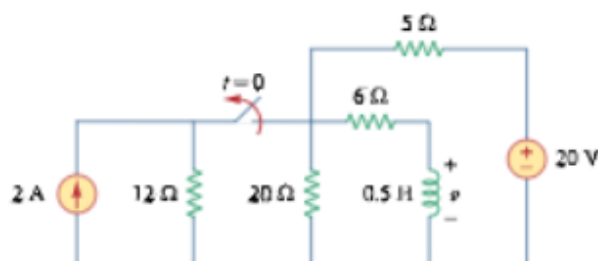


Figure 7.122


For Prob. 7.56.

# Chapter 7, Solution 56.

$$R_{eq} = 6 + 20 \parallel 5 = 10 \, \Omega, \quad \tau = \frac{L}{R} = 0.05$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

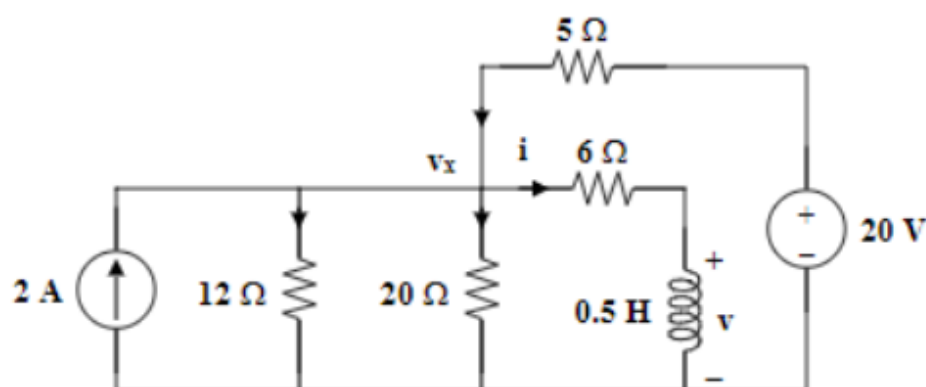$i(0)$  is found by applying nodal analysis to the following circuit.



$$2 + \frac{20 - v_x}{5} = \frac{v_x}{12} + \frac{v_x}{20} + \frac{v_x}{6} \longrightarrow v_x = 12$$

$$i(0) = \frac{v_x}{6} = 2 \, \text{A}$$

Since  $20 \parallel 5 = 4$ ,

$$i(\infty) = \frac{4}{4 + 6} (4) = 1.6$$

$$i(t) = 1.6 + (2 - 1.6) e^{-t/0.05} = 1.6 + 0.4 e^{-20t}$$

$$v(t) = L \frac{di}{dt} = \frac{1}{2} (0.4) (-20) e^{-20t}$$


$$v(t) = \underline{-4 e^{-20t} \, \text{V}}$$

10.



### Chapter 8, Solution 1.

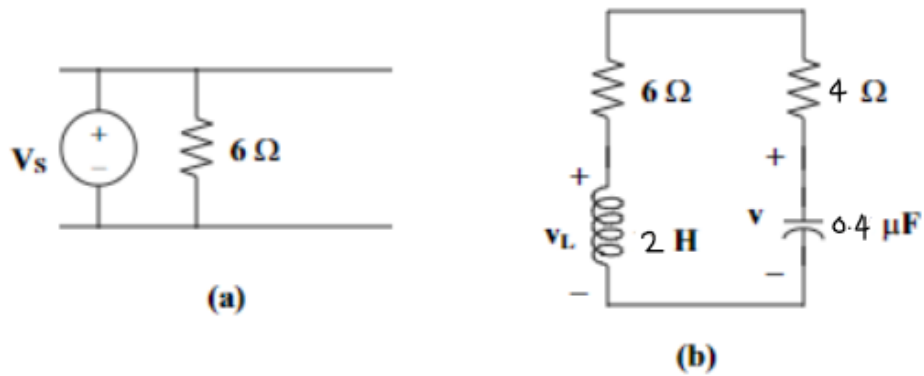(a) At  $t = 0^-$ , the circuit has reached steady state so that the equivalent circuit is shown in Figure (a).



$$i(0^-) = 12/6 = 2\text{A}, \quad v(0^-) = 12\text{V}$$

$$\text{At } t = 0^+, \quad i(0^+) = i(0^-) = \underline{2\text{A}}, \quad v(0^+) = v(0^-) = \underline{12\text{V}}$$

(b) For  $t > 0$ , we have the equivalent circuit shown in Figure (b).

$$v_L = L di/dt \text{ or } di/dt = v_L/L$$

Applying KVL at  $t = 0^+$ , we obtain,

$$v_L(0^+) - v(0^+) + 10i(0^+) = 0$$

$$v_L(0^+) - 12 + 20 = 0, \text{ or } v_L(0^+) = -8$$

$$\text{Hence, } di(0^+)/dt = -8/2 = \underline{-4\text{ A/s}}$$

$$\text{Similarly, } i_C = C dv/dt, \text{ or } dv/dt = i_C/C$$

$$i_C(0^+) = -i(0^+) = -2$$

$$dv(0^+)/dt = -2/0.4 = \underline{-5\text{ V/s}}$$

(c) As  $t$  approaches infinity, the circuit reaches steady state.

$$i(\infty) = \underline{0\text{ A}}, \quad v(\infty) = \underline{0\text{ V}}$$

11.

### Chapter 8, Problem 14.

The switch in Fig. 8.69 moves from position  $A$  to position  $B$  at  $t = 0$  (please note that the switch must connect to point  $B$  before it breaks the connection at  $A$ , a make-before-break switch). Find  $v(t)$  for  $t > 0$

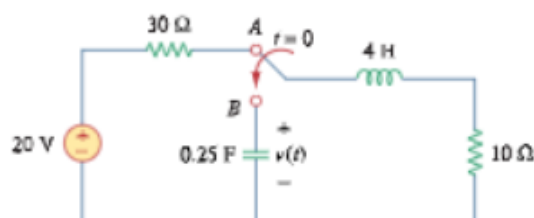


Figure 8.69

For Prob. 8.14.

### Chapter 8, Solution 14.

When the switch is in position  $A$ ,  $v(0^-) = 0$  and  $i_L(0) = \frac{20}{40} = 0.5A$ . When the switch is in position  $B$ , we have a source-free series RCL circuit.

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times 4} = 1.25$$
$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 4}} = 1$$

Since  $\alpha > \omega_o$ , we have overdamped case.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -1.25 \pm \sqrt{1.5625 - 1} = -0.5 \text{ and } -2$$

$$v(t) = Ae^{-2t} + Be^{-0.5t} \quad (1)$$

$$v(0) = 0 = A + B \quad (2)$$

$$i_C(0) = C \frac{dv(0)}{dt} = 0.5 \quad \longrightarrow \quad \frac{dv(0)}{dt} = \frac{0.5}{C} = 2$$

But  $\frac{dv(t)}{dt} = -2Ae^{-2t} - 0.5Be^{-0.5t}$

$$\frac{dv(0)}{dt} = -2A - 0.5B = 2 \quad (3)$$


Solving (2) and (3) gives  $A = -1.3333$  and  $B = 1.3333$

$$v(t) = \underline{\underline{-1.3333e^{-2t} + 1.3333e^{-0.5t} \text{ V.}}}$$

12.

### Chapter 8, Problem 24.

The switch in Fig. 8.77 moves from position *A* to position *B* at  $t = 0$  (please note that the switch must connect to point *B* before it breaks the connection at *A*, a make-before-break switch). Determine  $i(t)$  for  $t > 0$

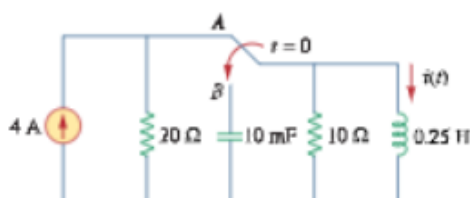

**Figure 8.77**  
For Prob. 8.24.

### Chapter 8, Solution 24.

When the switch is in position *A*, the inductor acts like a short circuit so

$$i(0^-) = 4$$

When the switch is in position *B*, we have a source-free parallel RCL circuit

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 10 \times 10^{-3}} = 5$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 10 \times 10^{-3}}} = 20$$

Since  $\alpha < \omega_o$ , we have an underdamped case.

$$s_{1,2} = -5 \pm \sqrt{25 - 400} = -5 \pm j19.365$$

$$i(t) = e^{-5t} (A_1 \cos 19.365t + A_2 \sin 19.365t)$$

$$i(0) = 4 = A_1$$

$$v = L \frac{di}{dt} \longrightarrow \frac{di(0)}{dt} = \frac{v(0)}{L} = 0$$

$$\frac{di}{dt} = e^{-5t} (-5A_1 \cos 19.365t - 5A_2 \sin 19.365t - 19.365A_1 \sin 19.365t + 19.365A_2 \cos 19.365t)$$

$$0 = \frac{di(0)}{dt} = -5A_1 + 19.365A_2 \longrightarrow A_2 = \frac{5A_1}{19.365} = 1.033$$

$$i(t) = \underline{e^{-5t} (4 \cos 19.365t + 1.033 \sin 19.365t)}$$