

## EE101 Tutorial 5

### Topic: OPERATIONAL AMPLIFIERS

Q1. An op amp exhibits the following nonlinear characteristic:

$$V_{out} = \alpha \tanh[\beta(V_{in1} - V_{in2})]$$

Sketch this characteristic and determine the small-signal gain of the op amp in the vicinity of  $V_{in1} - V_{in2} \approx 0$ .

Q2. Calculate the closed-loop gain of the noninverting amplifier shown in Fig.1. If  $A_0 = \infty$ . Verify that the result reduces to expected values if  $R_1 \rightarrow 0$  or  $R_3 \rightarrow 0$ .

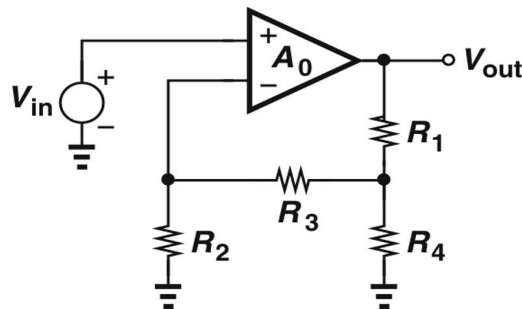


Fig. 1

Q3. The op amp used in an inverting amplifier exhibits a finite input impedance,  $R_{in}$ . Modeling the op amp as shown in Fig.2, determine the closed-loop gain and input impedance.

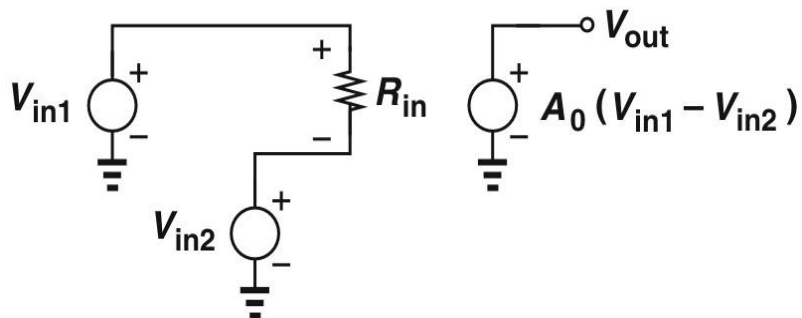


Fig. 2

Q4. Determine the closed-loop gain of the circuit depicted in Fig. 3, if  $A_o = \infty$ .

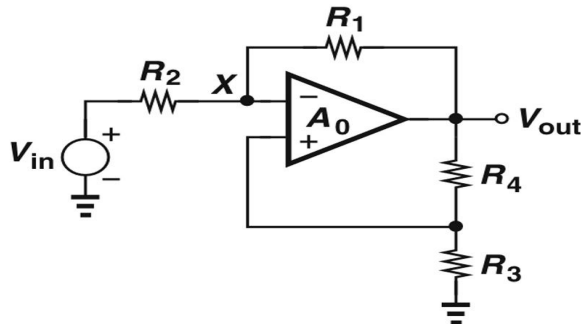


Fig. 3

Q5. The integrator of Fig. 4 senses an input signal given by  $V_{in} = V_0 \sin \omega t$ . Determine the output signal amplitude if  $A_0 = \infty$ .

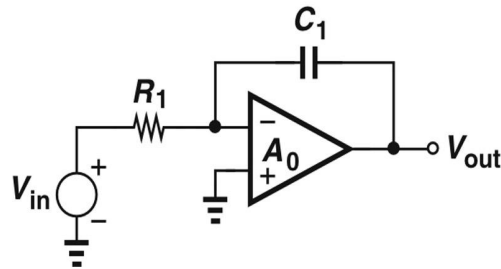


Fig. 4

Q6. The integrator of Fig. 4 is used to amplify a sinusoidal input by a factor of 10. If  $A_0 = \infty$  and  $R_1 C_1 = 10 \text{ ns}$ , Compute the frequency of the sinusoid.

Q7. Suppose the op amp in Fig. 5 exhibits a finite input impedance and is modeled as shown in Fig. 2. Determine the transfer function  $V_{out}/V_{in}$ .

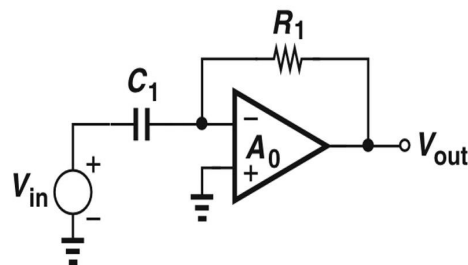


Fig. 5

Q8. Calculate the transfer function of the circuit shown in Fig. 6 if  $A_0 = \infty$ . What choice of component values reduces  $|V_{out}/V_{in}|$  to unity at all frequencies?

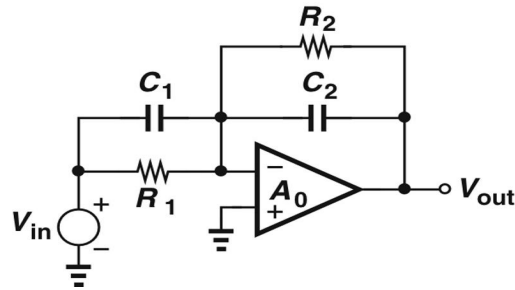


Fig. 6

Q9. Consider the voltage adder shown in Fig. 7. Plot  $V_{out}$  as a function of time if  $V_1 = V_0 \sin \omega t$  and  $V_2 = V_0 \sin(3\omega t)$ . Assume  $R_1 = R_2$  and  $A_0 = \infty$ .

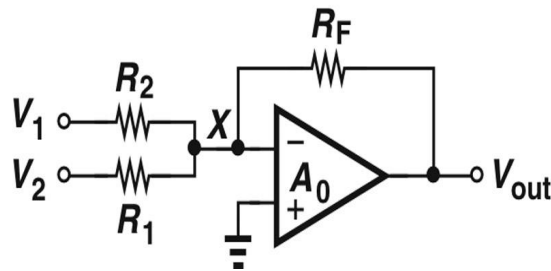


Fig. 7

Q10. Fig. 8 shows a precision rectifier producing negative cycles. Plot  $V_Y$ ,  $V_{out}$ , and the current flowing through  $D_1$  as a function of time for a sinusoidal input.

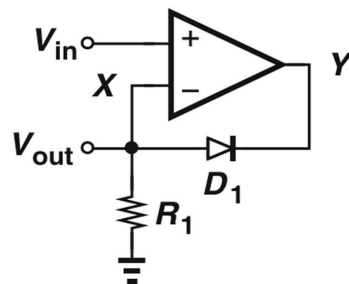


Fig. 8

