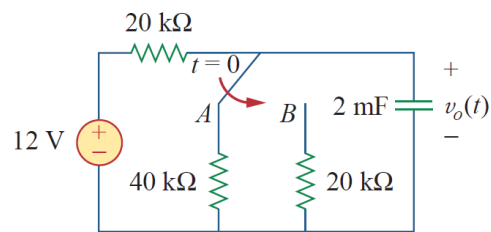


## EE101 Tutorial 12


Topics: **RC, RL and RLC Circuits**

- Q1.** Assuming that the switch in Fig. 1 has been in position A for a long time and is moved to position B at  $t=0$  find  $v_o(t)$  for  $t \geq 0$ .




**Fig. 1**

- Q2.** For the circuit in Fig. 2, find  $v_o(t)$  for  $t > 0$ . Determine the time necessary for the capacitor Voltage to decay to one-third of its value at  $t=0$ .

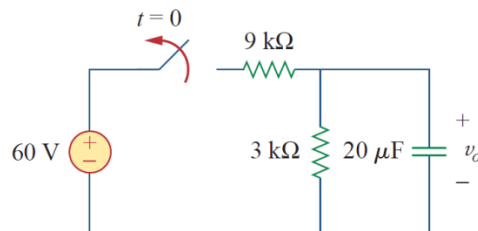

**Fig. 2**

- Q3.** For the circuit in Fig. 3, find  $i_o$  for  $t > 0$ .

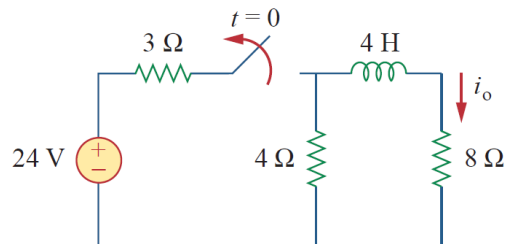

**Fig. 3**


**Q4.** In the circuit of Fig.4

$$v(t) = 20e^{-10^3 t} \text{ V}, t > 0$$

$$i(t) = 4e^{-10^3 t} \text{ mA}, t > 0$$


(a) Find  $R$ ,  $L$ , and  $\tau$ .

(b) Calculate the energy dissipated in the resistance for  $0 < t < 0.5 \text{ ms}$ .

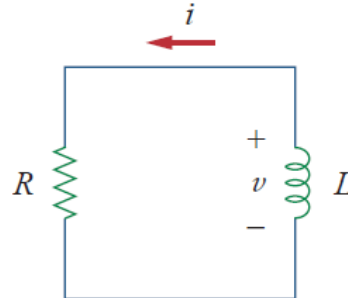


**Fig. 4**

**Q5.** Determine the time constant for each of the circuits in Fig. 5.

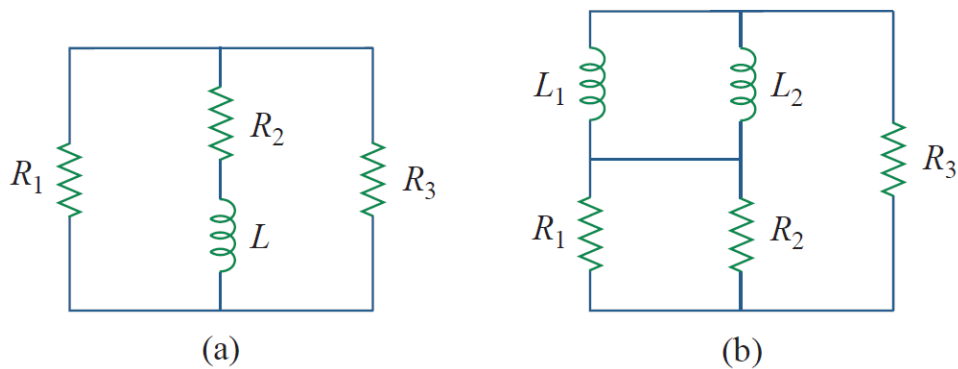


**Fig. 5**

**Q6.** In the circuit of Fig. 6, find  $i(t)$  for  $t > 0$  if  $i(0) = 2 \text{ A}$ .

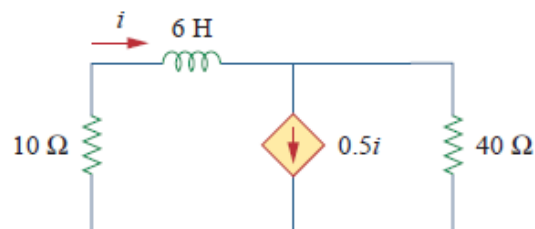


**Fig. 6**

**Q7.** Calculate the capacitor voltage for  $t < 0$  and  $t > 0$  for each of the circuits in Fig. 7.

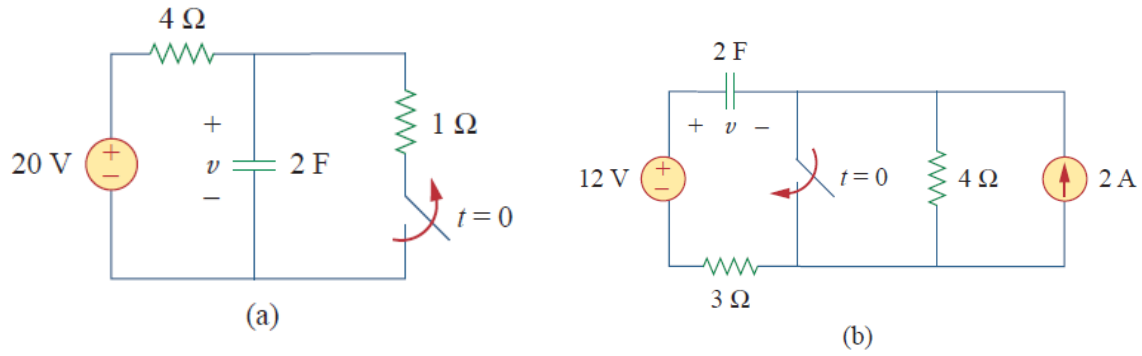


**Fig. 7**

**Q8.** Find  $v(t)$  for  $t < 0$  and  $t > 0$  in the circuit of Fig. 8.

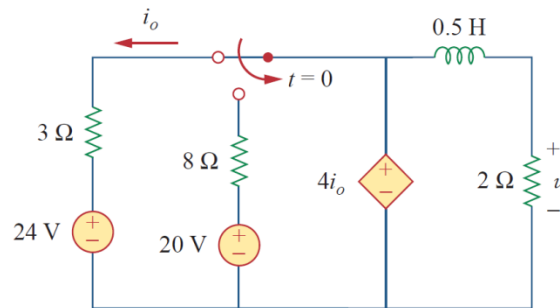

**Fig. 8**


**Q9.** For the network shown in Fig. 9, find  $v(t)$  for  $t > 0$ .

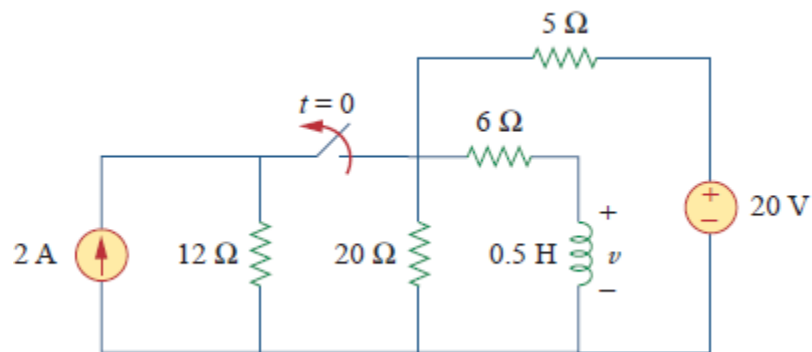

**Fig. 9**


**Q10.** For the circuit in Fig. 10, find:

- (a)  $i(0^+)$  and  $v(0^+)$
- (b)  $di(0^+)/dt$  and  $dv(0^+)/dt$ ,
- (c)  $i(\infty)$  and  $v(\infty)$ .

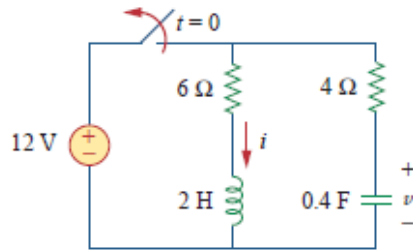


**Fig. 10**

**Q11.** The switch in Fig. 11 moves from position *A* to position *B* at  $t=0$  (please note that the switch must connect to point *B* before it breaks the connection at *A*, a make-before-break switch). Find  $v(t)$  for  $t > 0$ .

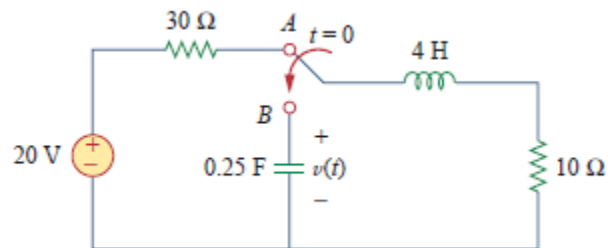

**Fig. 11**

**Q12.** The switch in Fig. 12 moves from position *A* to position *B* at  $t=0$  (please note that the switch must connect to point *B* before it breaks the connection at *A*, a make-before-break switch). Determine  $i(t)$  for  $t > 0$ .

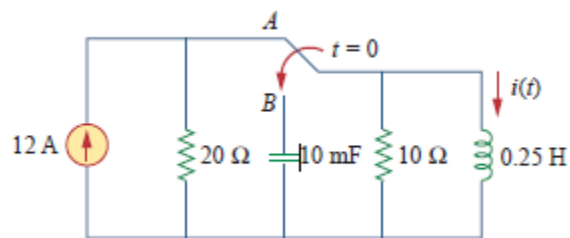

**Fig. 12**