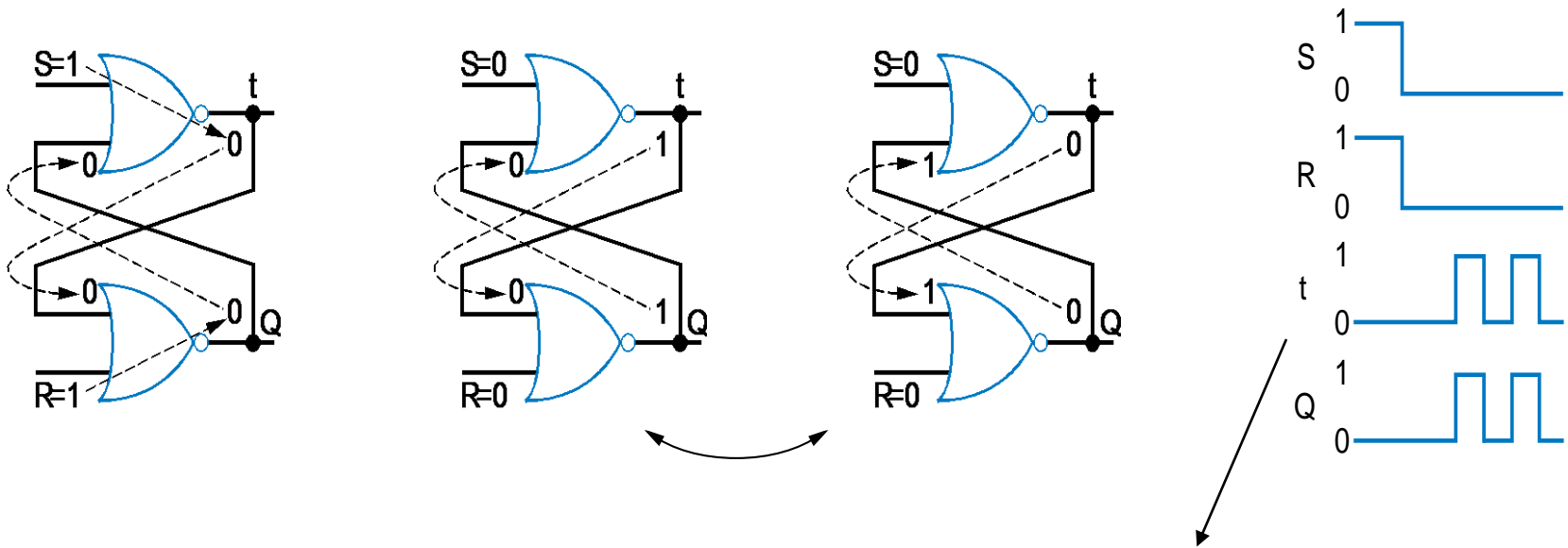



Sequential Logic Design

Problem with SR Latch

 
- Problem
 - If $S=1$ and $R=1$ simultaneously, we don't know what value Q will take



Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.



Clocks


 


- **Clock period:** time interval between pulses
 - Above signal: period = 20 ns
- **Clock cycle:** one such time interval
 - Above signal shows 3.5 clock cycles
- **Clock frequency:** $1/\text{period}$
 - Above signal: frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$
 - $1 \text{ Hz} = 1/\text{s}$

Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

 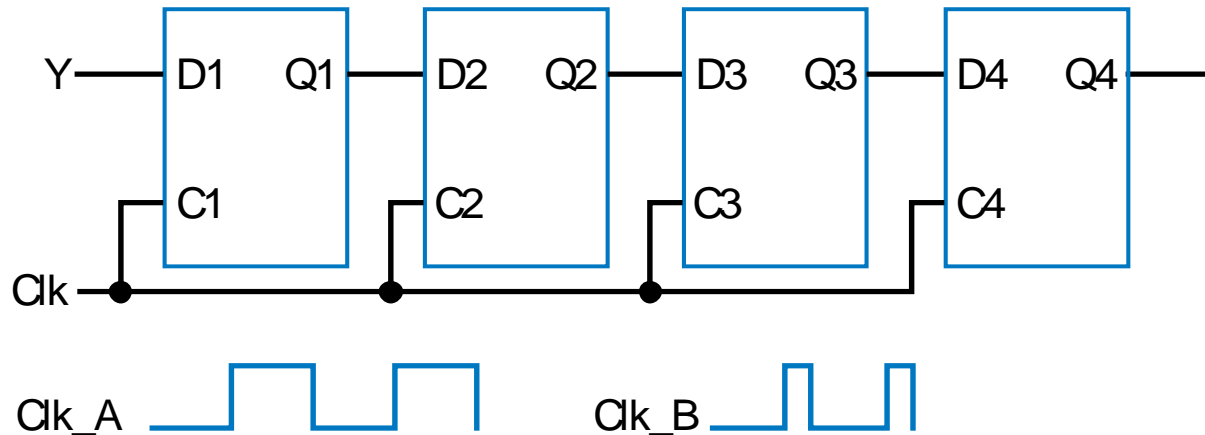
Problem with Level-Sensitive D Latch

- D latch still has problem (as does SR latch)
 - When $C=1$, through how many latches will a signal travel?
 - Depends on for how long $C=1$
 - Clk_A -- signal may travel through multiple latches
 - Clk_B -- signal may travel through fewer latches
 - Hard to pick C that is just the right length
 - Can we design bit storage that only stores a value on the rising edge of a clock signal?





D Flip-Flop

- **Flip-flop**: Bit storage that stores on clock edge, not level
- One design -- master-servant
 - Two latches, output of first goes to input of second, master latch has inverted clock signal
 - So master loaded when $C=0$, then servant when $C=1$
 - When C changes from 0 to 1, master disabled, servant loaded with value that was at D just before C changed -- i.e., value at D during rising edge of C

 


 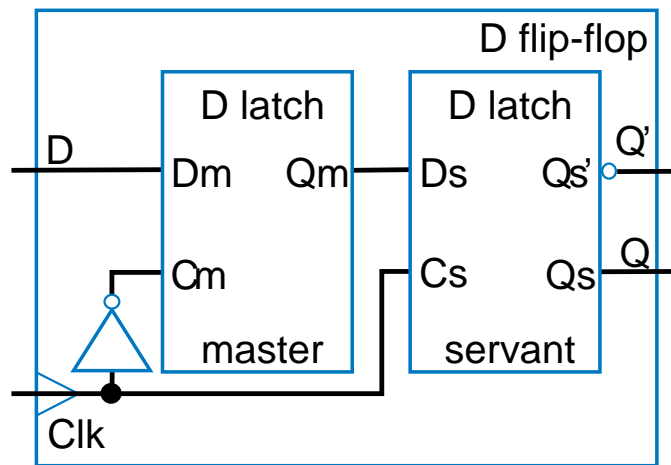*Note:
Hundreds of
different flip-
flop designs
exist*





D Flip-Flop

 The triangle means clock input, edge triggered




  Symbol for rising-edge triggered D flip-flop




Symbol for falling-edge triggered D flip-flop

 Internal design: Just invert servant clock rather than master




D Flip-Flop

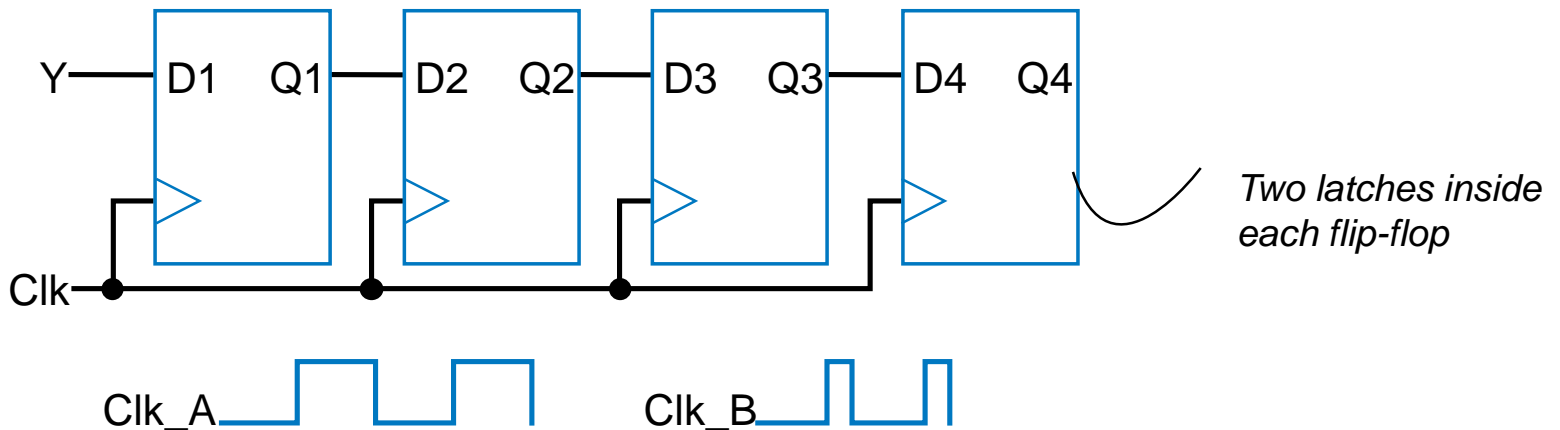- Solves problem of not knowing through how many latches a signal travels when $C=1$
 - In figure below, signal travels through exactly one flip-flop, for Clk_A or Clk_B
 - Why? Because on rising edge of Clk, all four flip-flops are loaded simultaneously -- then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is 1.




D Latch vs. D Flip-Flop

 
- Latch is level-sensitive: Stores D when C=1
- Flip-flop is edge triggered: Stores D when C changes from 0 to 1
 - Saying “level-sensitive latch,” or “edge-triggered flip-flop,” is redundant
 - Two types of flip-flops -- rising or falling edge triggered.
- Comparing behavior of latch and flip-flop:




Bit Storage Summary

 

 
Feature: $S=1$ sets Q to 1, $R=1$ resets Q to 0. Problem: $SR=11$ yield undefined Q .



 Feature: S and R only have effect when $C=1$. We can design outside circuit so $SR=11$ never happens when $C=1$. Problem: avoiding $SR=11$ can be a burden.



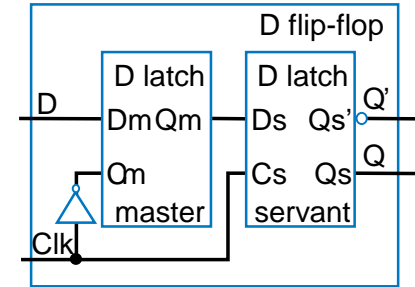
Feature: SR can't be 11 if D is stable before and while $C=1$, and will be 11 for only a brief glitch even if D changes while $C=1$. Problem: $C=1$ too long propagates new values through too many latches: too short may not enable a store.



Feature: Only loads D value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. Tradeoff: uses more gates internally than D latch, and requires more external gates than SR – but gate count is less of an issue today.

- We considered increasingly better bit storage until we arrived at the robust D flip-flop bit storage

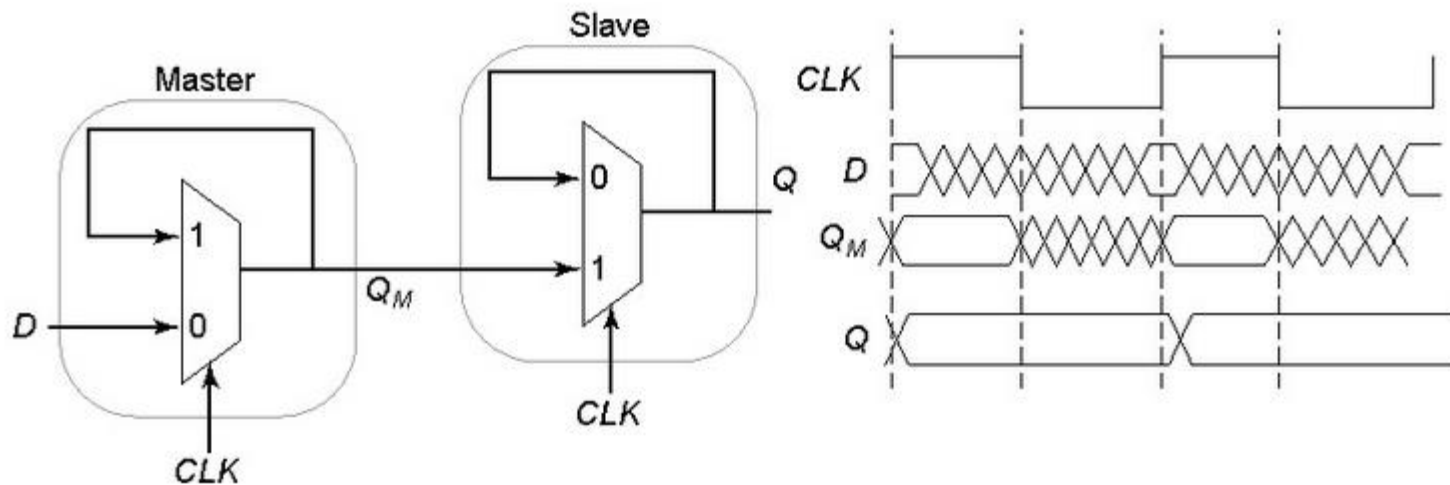Positive edge triggered registers based on multiplexers






Introduction

- Introduced increasingly complex digital building blocks
 - Gates, multiplexors, decoders, basic registers, and controllers
- Controllers good for systems with control inputs/outputs
 - **Control** input: Single bit (or just a few), representing environment event or state
 - e.g., 1 bit representing button pressed
 - **Data** input: Multiple bits collectively representing single entity
 - e.g., 7 bits representing temperature in binary
- Need building blocks for data
 - **Datapath components**, aka register-transfer-level (RTL) components, store/transform data
 - Put datapath components together to form a **datapath**

Registers

 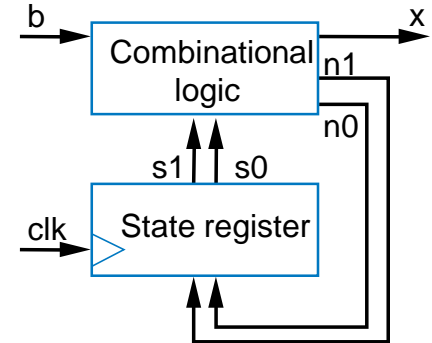 - Can store data, very common in datapaths
- Basic register : Loaded every cycle
 - Useful for implementing FSM -- stores encoded state
 - For other uses, may want to load only on certain cycles




Basic register loads on every clock cycle

How extend to only load on certain cycles?


Register with Parallel Load

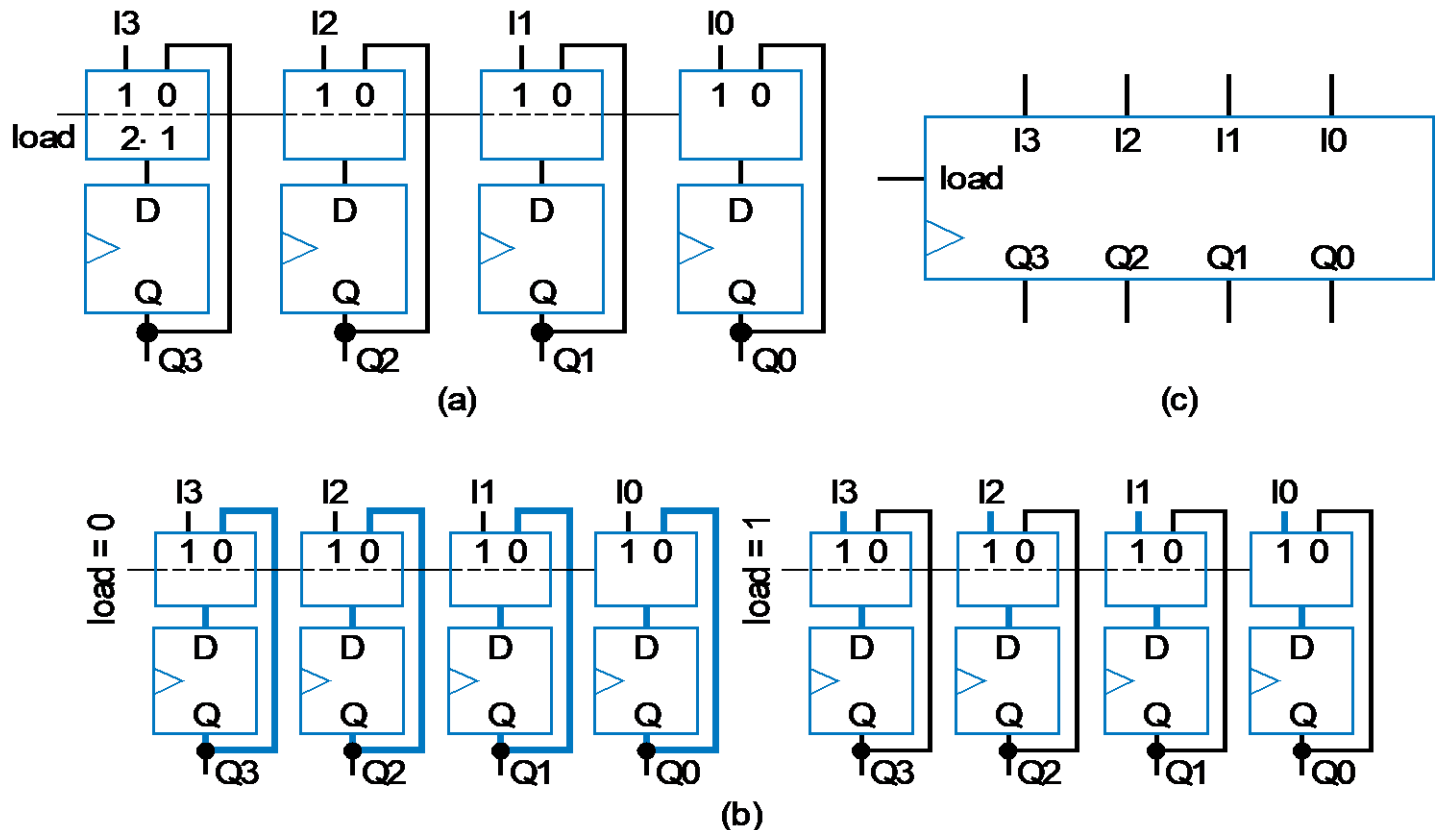- Add 2x1 mux to front of each flip-flop
- Register's load input selects mux input to pass
 - Either existing flip-flop value, or new value to load




Basic Example Using Registers

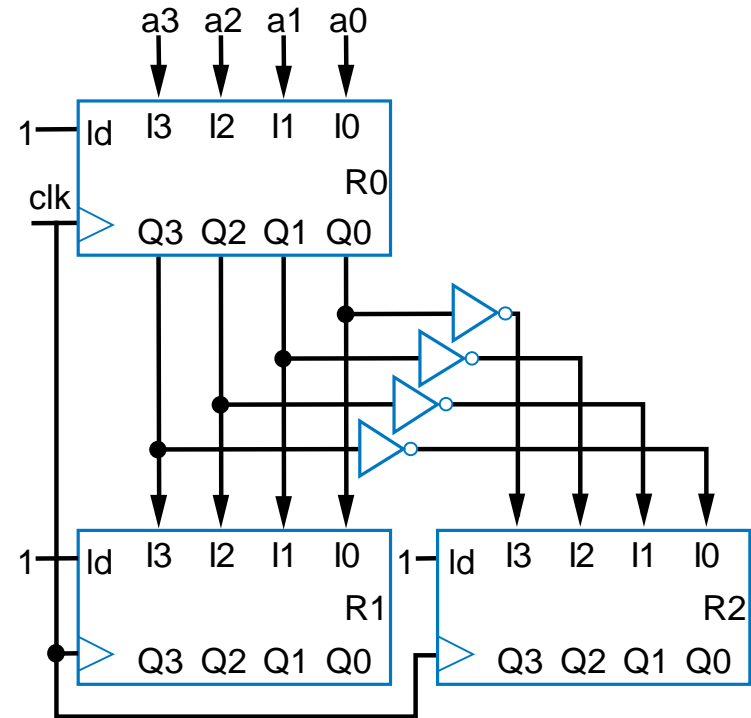- This example will show how registers load simultaneously on clock cycles
 - Notice that all load inputs set to 1 in this example -- just for demonstration purposes




Basic Example Using Registers

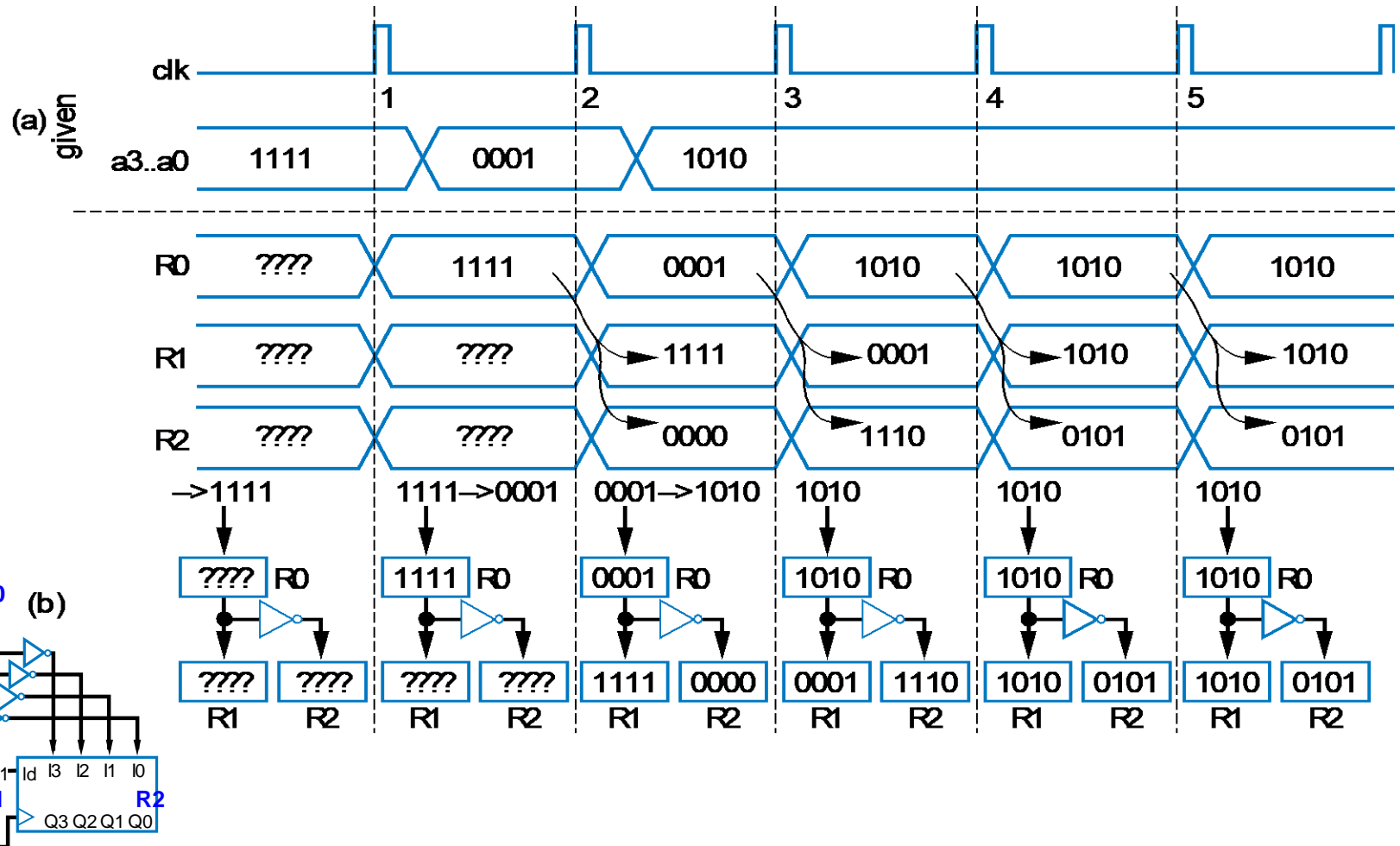


Register Example using the Load Input: Weight Sampler

 - Scale has two displays
 - Present weight
 - Saved weight
 - Useful to compare present item with previous item
- Use register to store weight
 - Pressing button causes present weight to be stored in register
 - Register contents always displayed as “Saved weight,” even when new present weight appears




Register Example: Temperature History Display

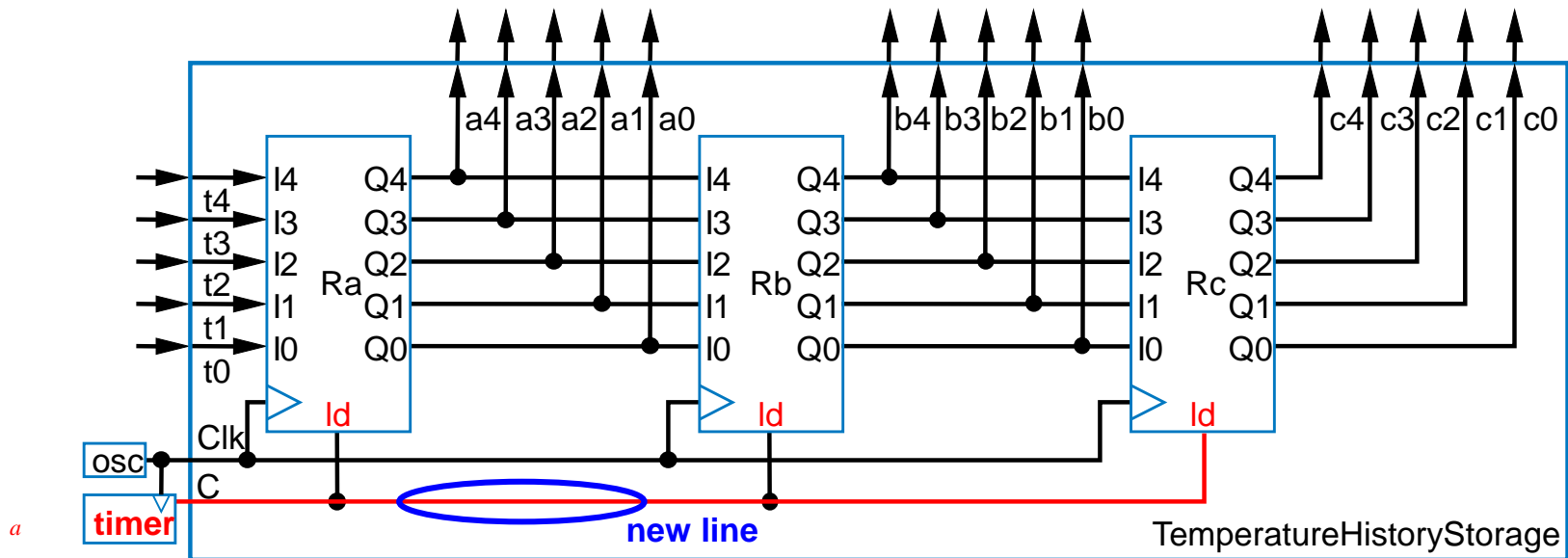- Recall Chpt 3 example
 - Timer pulse every hour
 - Previously used as clock. Better design only connects oscillator to clock inputs -- use registers with load input, connect to timer pulse.




Register Example: Above-Mirror Display

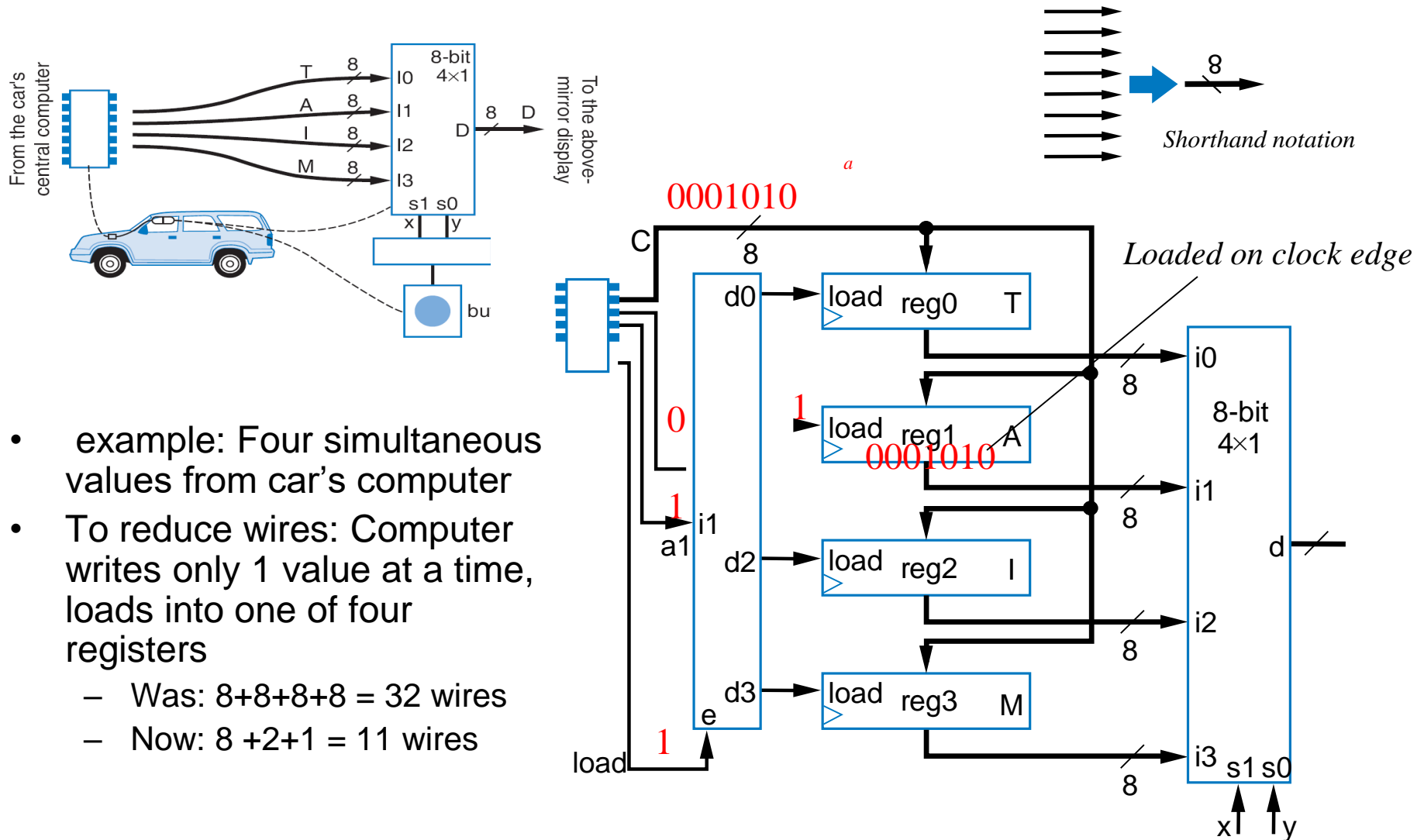

Shift Register

 - Shift right
 - Move each bit one position right
 - Shift in 0 to leftmost bit




Q: Do four right shifts on 1001, showing value after each shift

A:

1001	(original)
0100	
0010	
0001	
0000	


A dotted arrow points from the original value 1001 down to the final value 0000, indicating the sequence of shifts.

 - Implementation: Connect flip-flop output to next flip-flop's input





Shift Register

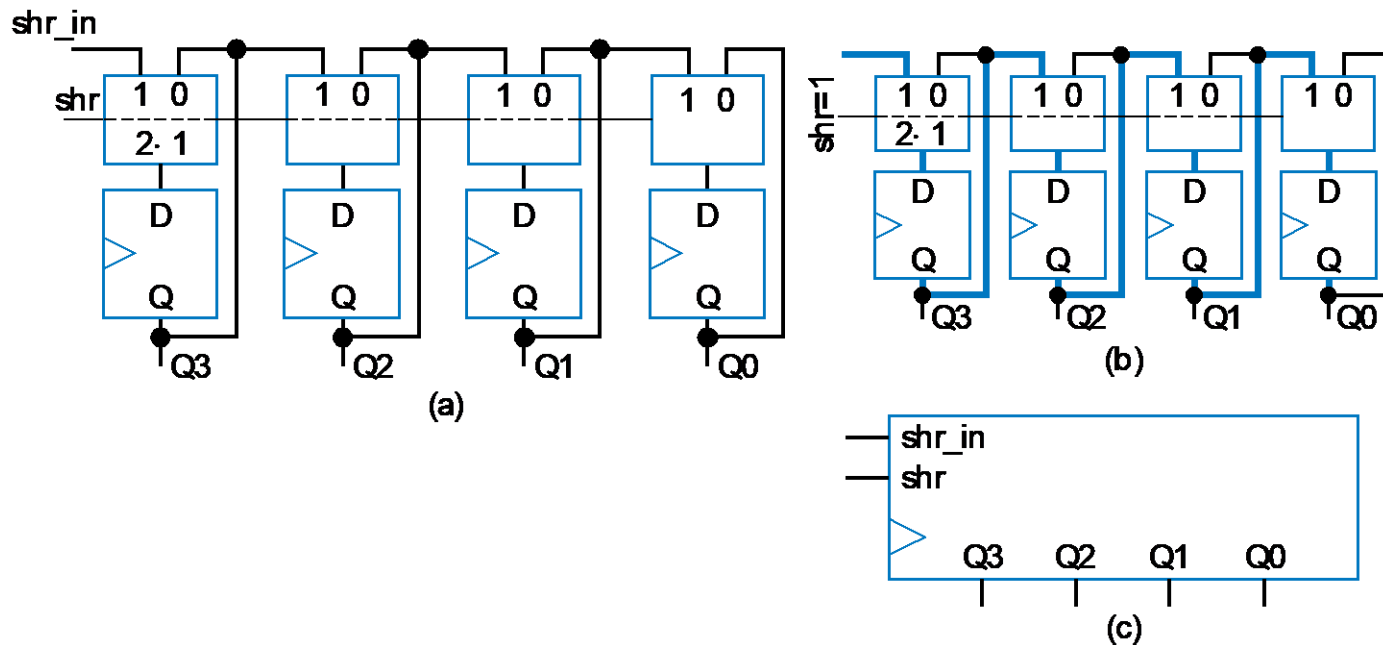- To allow register to either shift or retain, use 2x1 muxes
 - shr: 0 means retain, 1 shift
 - shr_in: value to shift in
 - May be 0, or 1
- Note: Can easily design shift register that shifts left instead





Rotate Register

  - Rotate right: Like shift right, but leftmost bit comes from rightmost bit




Shift Register Example: Above-Mirror Display

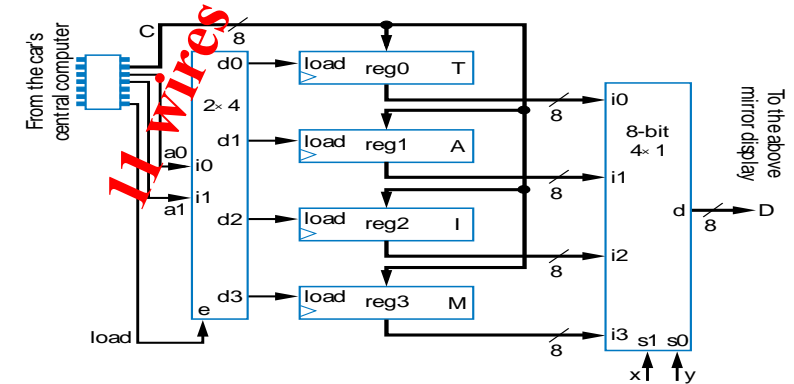 - Earlier example: $8 + 2 + 1 = 11$ wires from car's computer to above-mirror display's four registers
 - Better than 32 wires, but 11 still a lot -- want fewer for smaller wire bundles
- Use shift registers
 - Wires: $1 + 2 + 1 = 4$
 - Computer sends one value at a time, one bit per clock cycle



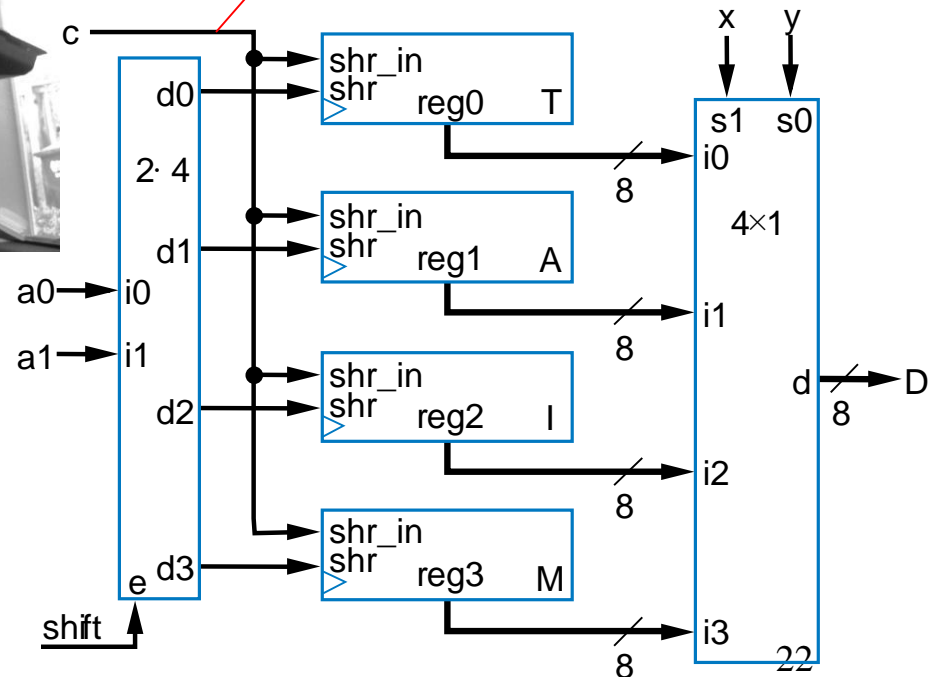Note: this line is 1 bit, rather than 8 bits like before





Multifunction Registers

- Many registers have multiple functions
 - Load, shift, clear (load all 0s)
 - And retain present value, of course
- Easily designed using muxes
 - Just connect each mux input to achieve desired function


Functions:

s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	(unused - let's load 0s)

  


Multifunction Registers

s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	Shift left

 

(a)

 


(b)

Multifunction Registers with Separate Control Inputs

ld	shr	shl	Operation
0	0	0	Maintain present value
0	0	1	Shift left
0	1	0	Shift right
0	1	1	Shift right – shr has priority over shl
1	0	0	Parallel load
1	0	1	Parallel load – ld has priority
1	1	0	Parallel load – ld has priority
1	1	1	Parallel load – ld has priority

Truth table for combinational circuit

Inputs			Outputs		Note Operation
ld	shr	shl	s1	s0	
0	0	0	0	0	Maintain value
0	0	1	1	1	Shift left
0	1	0	1	0	Shift right
0	1	1	1	0	Shift right
1	0	0	0	1	Parallel load
1	0	1	0	1	Parallel load
1	1	0	0	1	Parallel load
1	1	1	0	1	Parallel load

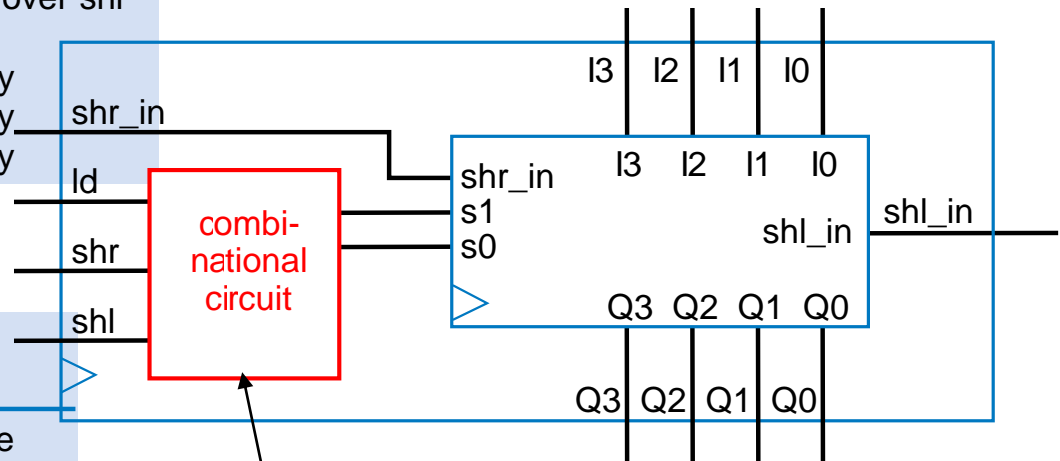

$$s1 = ld' * shr' * shl + ld' * shr * shl' + ld' * shr * shl$$

$$s0 = ld' * shr' * shl + ld$$

Register Operation Table

- Register operations typically shown using compact version of table
 - X means same operation whether value is 0 or 1
 - One X expands to two rows
 - Two Xs expand to four rows
 - Put highest priority control input on left to make reduced table simple

Inputs			Outputs		Note Operation
ld	shr	shl	s1	s0	
0	0	0	0	0	Maintain value
0	0	1	1	1	Shift left
0	1	0	1	0	Shift right
0	1	1	1	0	Shift right
1	0	0	0	1	Parallel load
1	0	1	0	1	Parallel load
1	1	0	0	1	Parallel load
1	1	1	0	1	Parallel load

ld	shr	shl	Operation
ld	shr	shl	
0	0	0	Maintain value
0	0	1	Shift left
0	1	X	Shift right
1	X	X	Parallel load

Register Design Process

- Can design register with desired operations using simple four-step process

TABLE 4.1 Four-step process for designing a multifunction register.

	Step	Description
1.	<i>Determine mux size</i>	Count the number of operations (don't forget the maintain present value operation!) and add in front of each flip-flop a mux with at least that number of inputs.
2.	<i>Create mux operation table</i>	Create an operation table defining the desired operation for each possible value of the mux select lines.
3.	<i>Connect mux inputs</i>	For each operation, connect the corresponding mux data input to the appropriate external input or flip-flop output (possibly passing through some logic) to achieve the desired operation.
4.	<i>Map control lines</i>	Create a truth table that maps external control lines to the internal mux select lines, with appropriate priorities, and then design the logic to achieve that mapping

Register Design Example

- Desired register operations
 - Load, shift left, synchronous clear, synchronous set

Step 1: Determine mux size

5 operations: above, plus maintain present value (don't forget this one!)

--> Use 8x1 mux

Step 2: Create mux operation table

Step 3: Connect mux inputs


Step 4: Map control lines

$$s2 = \text{clr}' * \text{set}$$

$$s1 = \text{clr}' * \text{set}' * \text{ld}' * \text{shl} + \text{clr}$$


$$s0 = \text{clr}' * \text{set}' * \text{ld} + \text{clr}$$

s2	s1	s0	Operation
0	0	0	Maintain present value
0	0	1	Parallel load
0	1	0	Shift left
0	1	1	Synchronous clear
1	0	0	Synchronous set
1	0	1	Maintain present value
1	1	0	Maintain present value
1	1	1	Maintain present value

 

Inputs				Outputs			Operation
clr	set	ld	shl	s2	s1	s0	
0	0	0	0	0	0	0	Maintain present value
0	0	0	1	0	1	0	Shift left
0	0	1	X	0	0	1	Parallel load
0	1	X	X	1	0	0	Set to all 1s
1	X	X	X	0	1	1	Clear to all 0s

Register Design Example

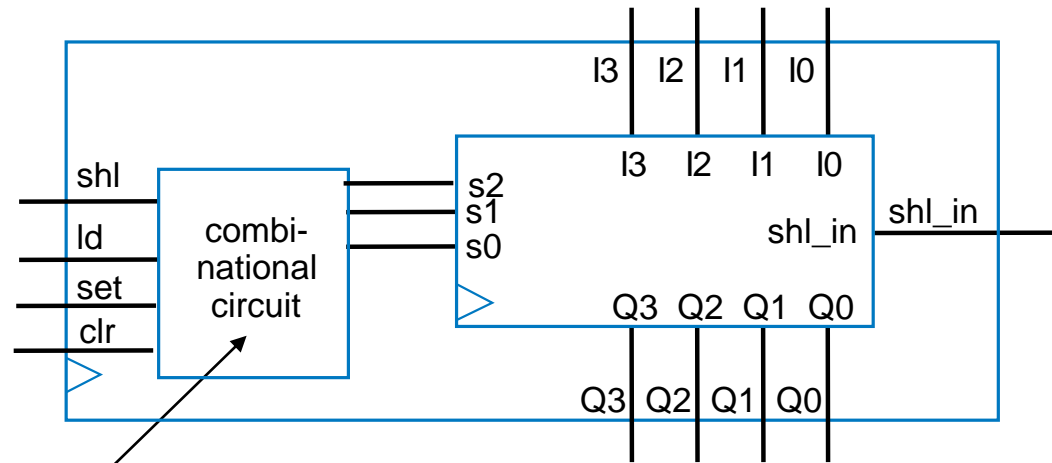

Step 4: Map control lines

$$s2 = \text{clr}' * \text{set}$$


$$s1 = \text{clr}' * \text{set}' * \text{ld}' * \text{shl} + \text{clr}$$

$$s0 = \text{clr}' * \text{set}' * \text{ld} + \text{clr}$$

Inputs				Outputs			Operation
clr	set	ld	shl	s2	s1	s0	
0	0	0	0	0	0	0	Maintain present value
0	0	0	1	0	1	0	Shift left
0	0	1	X	0	0	1	Parallel load
0	1	X	X	1	0	0	Set to all 1s
1	X	X	X	0	1	1	Clear to all 0s



Shifter Example: Temperature Averager

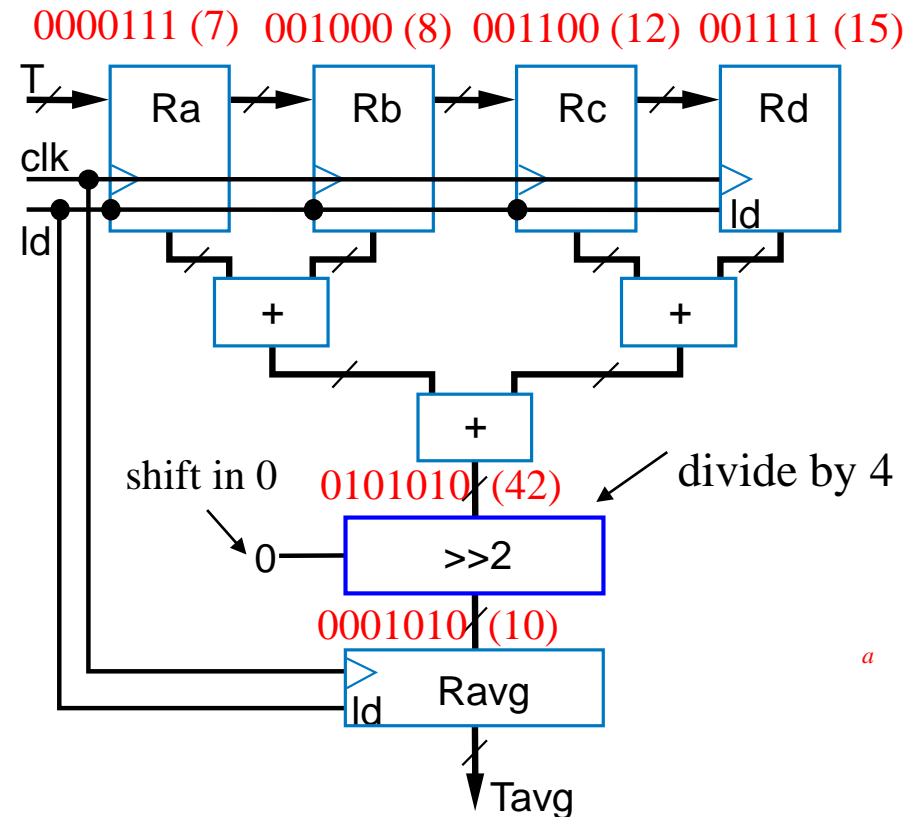- Four registers storing a history of temperatures
- Want to output the average of those temperatures
- Add, then divide by four
 - Same as shift right by 2
 - Use three adders, and right shift by two





Counters

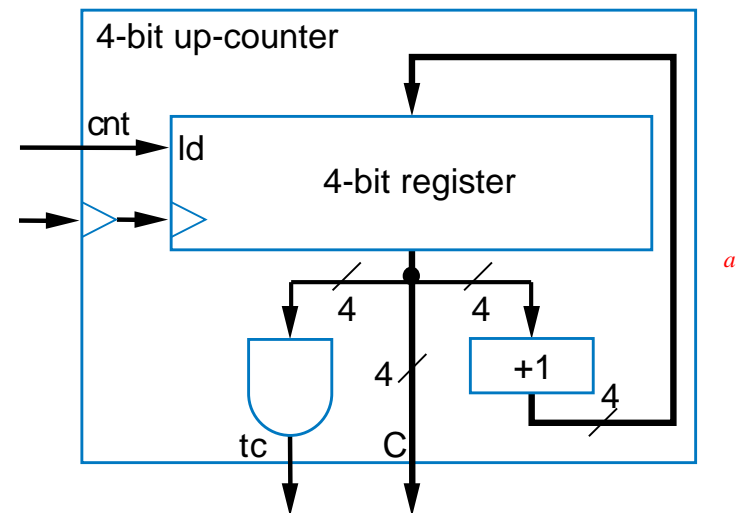 - ***N-bit up-counter***: N-bit register that can increment (add 1) to its own value on each clock cycle
 - 0000, 0001, 0010, 0011,, 1110, 1111, 0000
 - Note how count “rolls over” from 1111 to 0000
 - Terminal (last) count, tc, equals 1 during value just before rollover
- Internal design
 - Register, incrementer, and N-input AND gate to detect terminal count




Counter Example: Mode in Above-Mirror Display

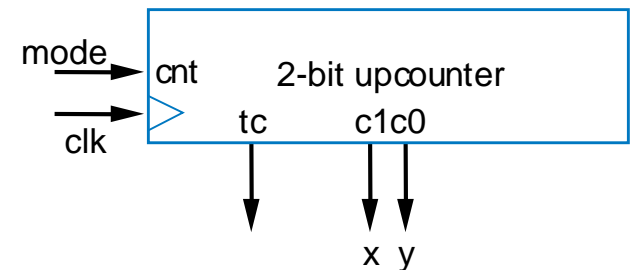 - Assumed component that incremented xy input each time button pressed: 00, 01, 10, 11, 00, 01, 10, 11, 00, ...
- Can use 2-bit up-counter
 - Assumes mode=1 for just one clock cycle during each button press
 - Recall “Button press synchronizer” example from Chapter 3




Down-Counter

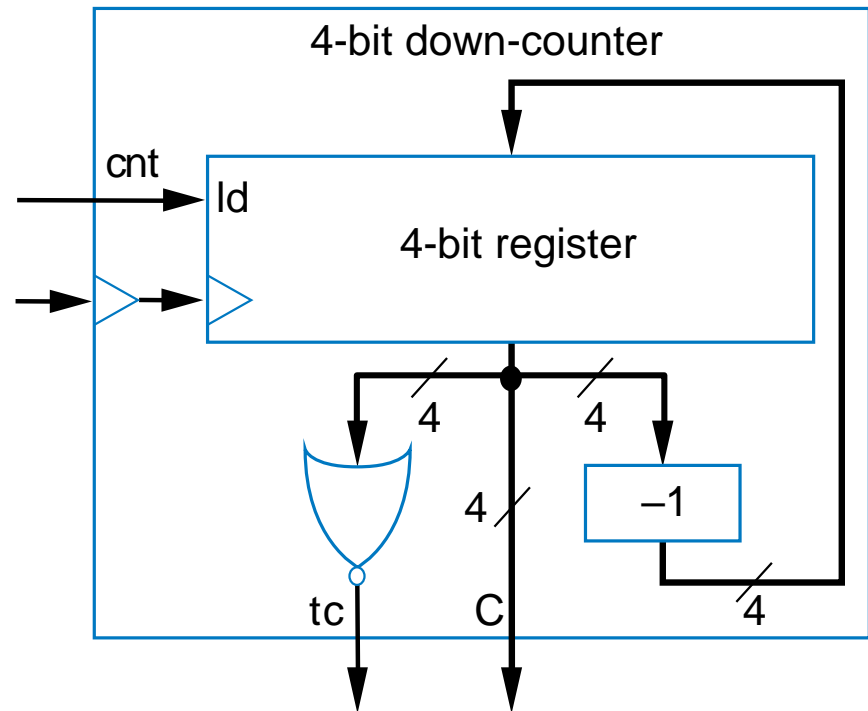- 4-bit down-counter
 - 1111, 1110, 1101, 1100, ..., 0011, 0010, 0001, 0000, 1111, ...
 - Terminal count is 0000
 - Use NOR gate to detect
 - Need decrementer (-1) – design like designed incrementer




Up/Down-Counter

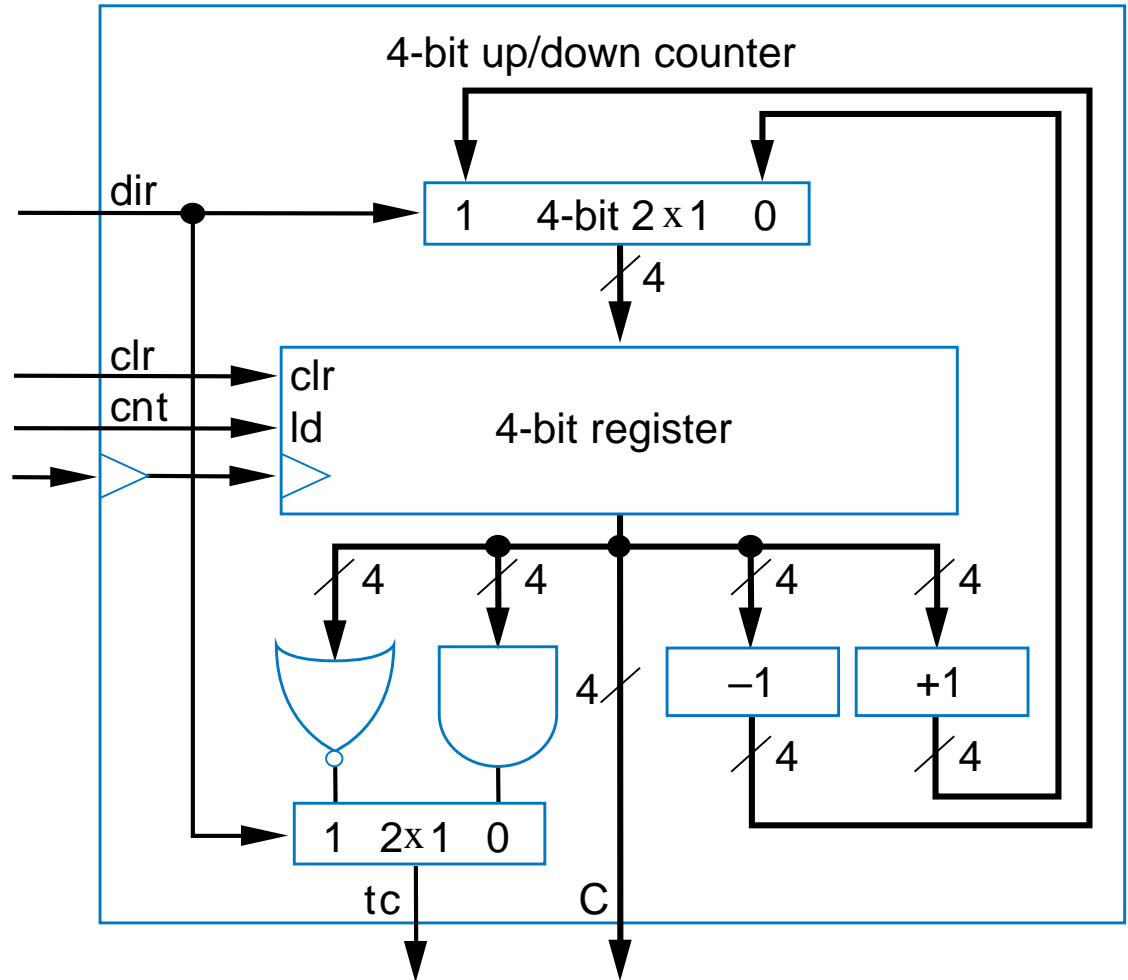- Can count either up or down
 - Includes both incrementer and decrementer
 - Use dir input to select, using 2x1: dir=0 means up
 - Likewise, dir selects appropriate terminal count value




Counter Example: Light Sequencer

 - Illuminate 8 lights from right to left, one at a time, one per second
- Use 3-bit up-counter to counter from 0 to 7
- Use 3x8 decoder to illuminate appropriate light
- Note: Used **3-bit** counter with 3x8 decoder
 - *NOT* an 8-bit counter – why not?




Counter with Parallel Load

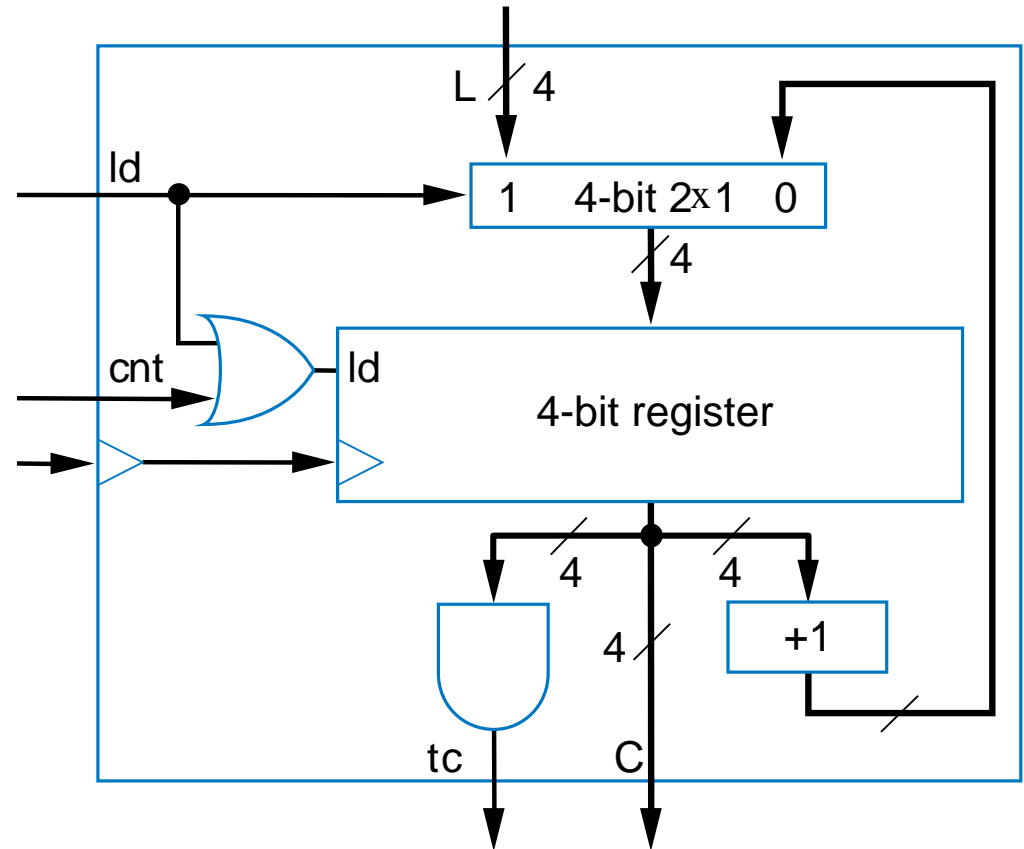- Up-counter that can be loaded with external value
 - Designed using 2x1 mux
 - ld input selects incremented value or external value
 - Load the internal register when loading external value or when counting



Counter with Parallel Load

- Useful to create pulses at specific multiples of clock
 - Not just at N-bit counter's natural wrap-around of 2^N
- Example: Pulse every 9 clock cycles
 - Use 4-bit down-counter with parallel load
 - Set parallel load input to 8 (1000)
 - Use terminal count to reload
 - When count reaches 0, next cycle loads 8.
 - Why load 8 and not 9? Because 0 is included in count sequence:
 - 8, 7, 6, 5, 4, 3, 2, 1, 0 → 9 counts

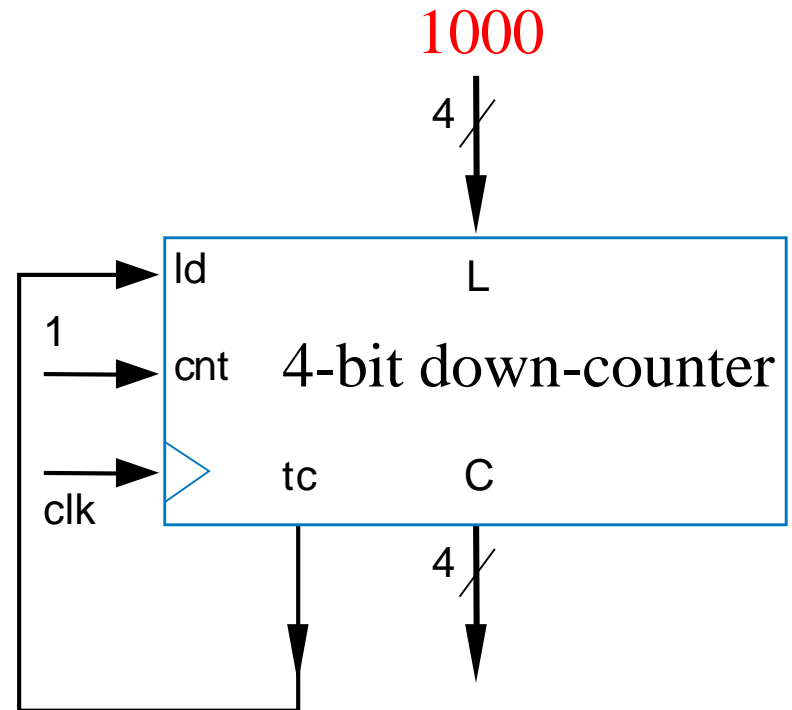

Arithmetic-Logic Unit: ALU

- **ALU**: Component that can perform any of various arithmetic (add, subtract, increment, etc.) and logic (AND, OR, etc.) operations, based on control inputs
- Motivation:
 - Suppose want multi-function calculator that not only adds and subtracts, but also increments, ANDs, ORs, XORs, etc.

TABLE 4.2 Desired calculator operations


Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	$S = A + B$	S=00010100
0	0	1	$S = A - B$	S=00001010
0	1	0	$S = A + 1$	S=00010000
0	1	1	$S = A$	S=00001111
1	0	0	$S = A \text{ AND } B$ (bitwise AND)	S=00000101
1	0	1	$S = A \text{ OR } B$ (bitwise OR)	S=00001111
1	1	0	$S = A \text{ XOR } B$ (bitwise XOR)	S=00001010
1	1	1	$S = \text{NOT } A$ (bitwise complement)	S=11110000

Multifunction Calculator without an ALU


- Can build multifunction calculator using separate components for each operation, and muxes
 - But too many wires, and wasted power computing all those operations when at any time you only use

TABLE 4.2 Desired calculator operations


Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	$S = A + B$	S=00010100
0	0	1	$S = A - B$	S=00001010
0	1	0	$S = A + 1$	S=00010000
0	1	1	$S = A$	S=00001111
1	0	0	$S = A \text{ AND } B$ (bitwise AND)	S=00000101
1	0	1	$S = A \text{ OR } B$ (bitwise OR)	S=00001111
1	1	0	$S = A \text{ XOR } B$ (bitwise XOR)	S=00001010
1	1	1	$S = \text{NOT } A$ (bitwise complement)	S=11110000

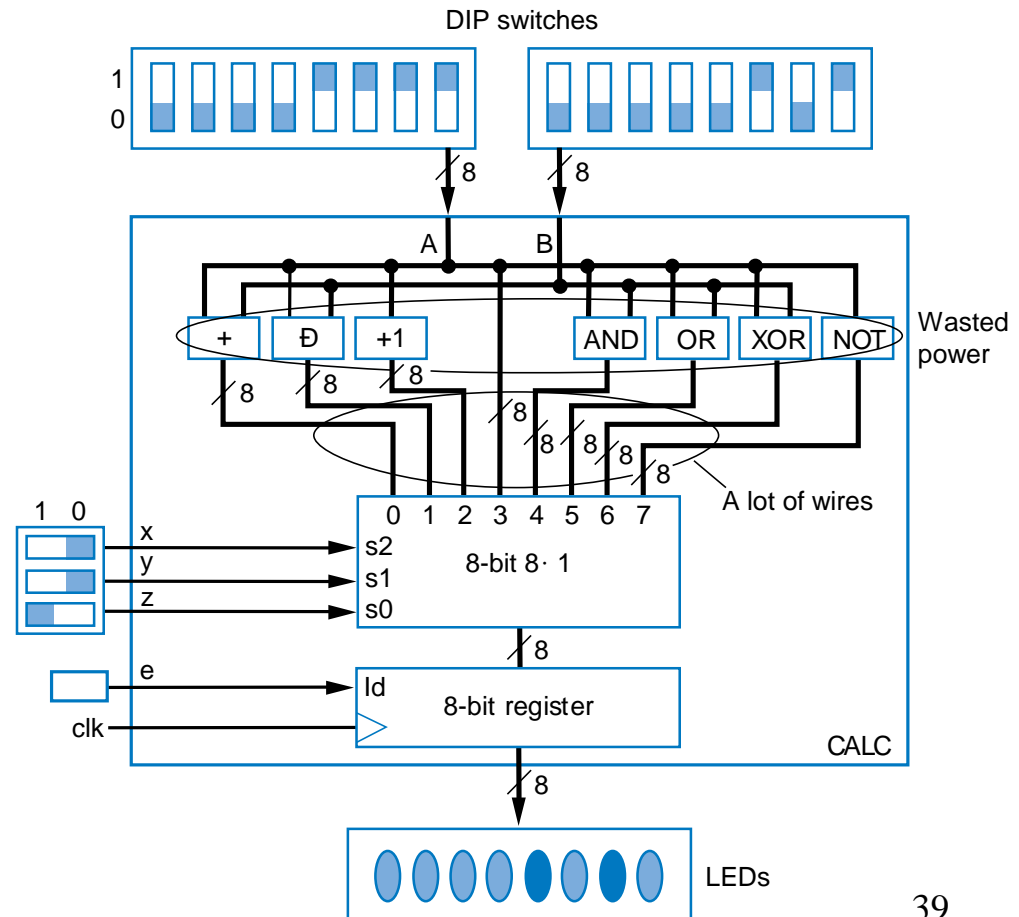

ALU Example: Multifunction Calculator

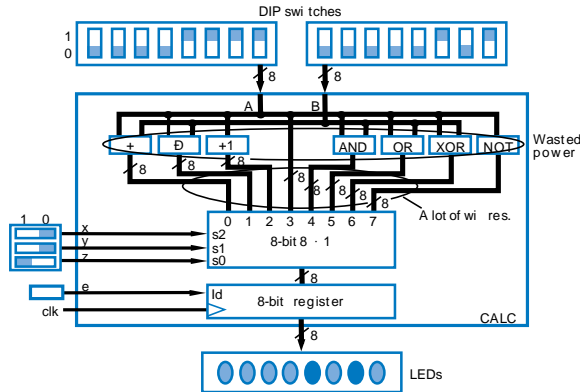

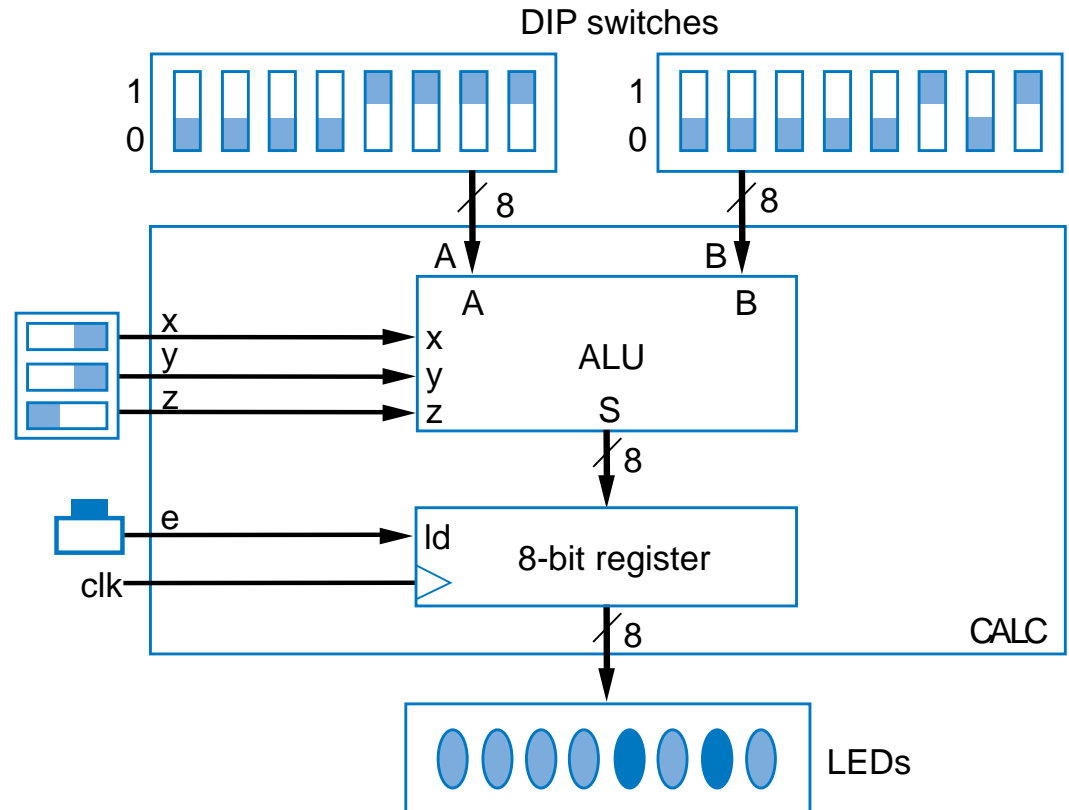- Design using ALU is elegant and efficient
 - No mass of wires
 - No big waste of power




Register Files

- ***MxN register file***





component provides
efficient access to M N-
bit-wide registers

 - If we have many registers but only need access one or two at a time, a register file is more efficient
- Ex: Above-mirror display (earlier example), but this time having 16 32-bit registers
 - Too many wires, and big mux is too slow





Register File

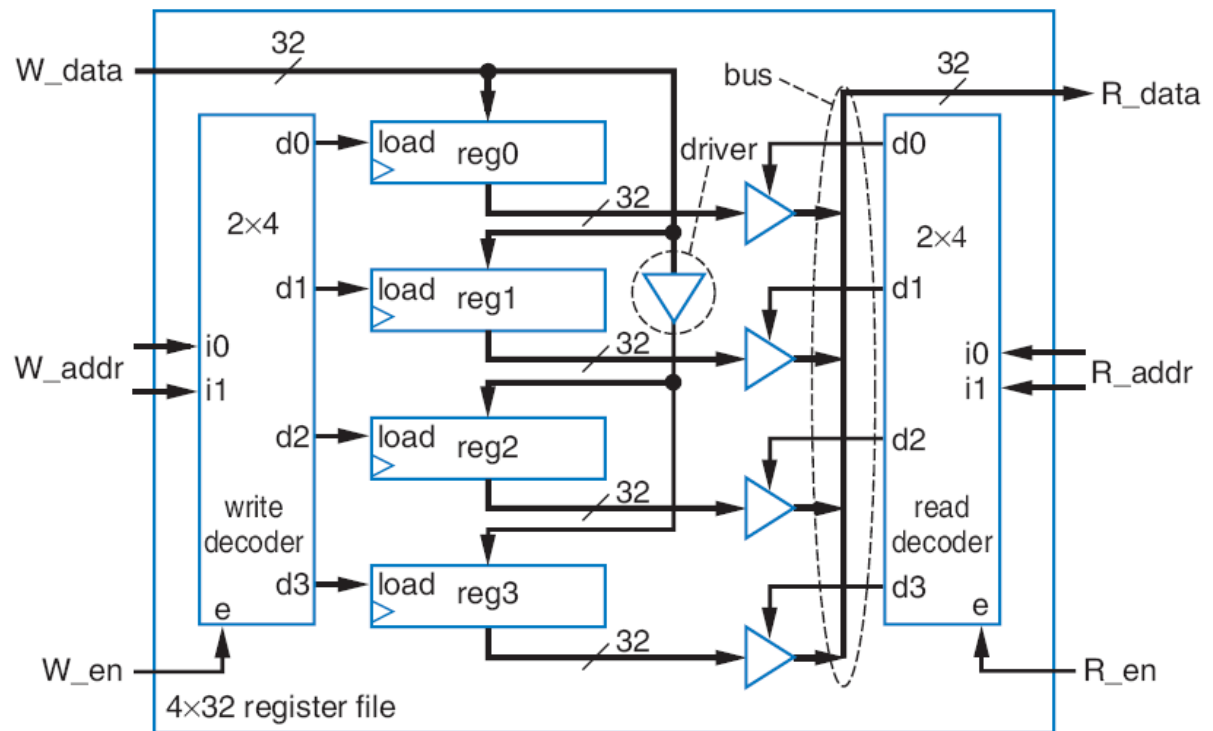   - Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read




Register File Timing Diagram

 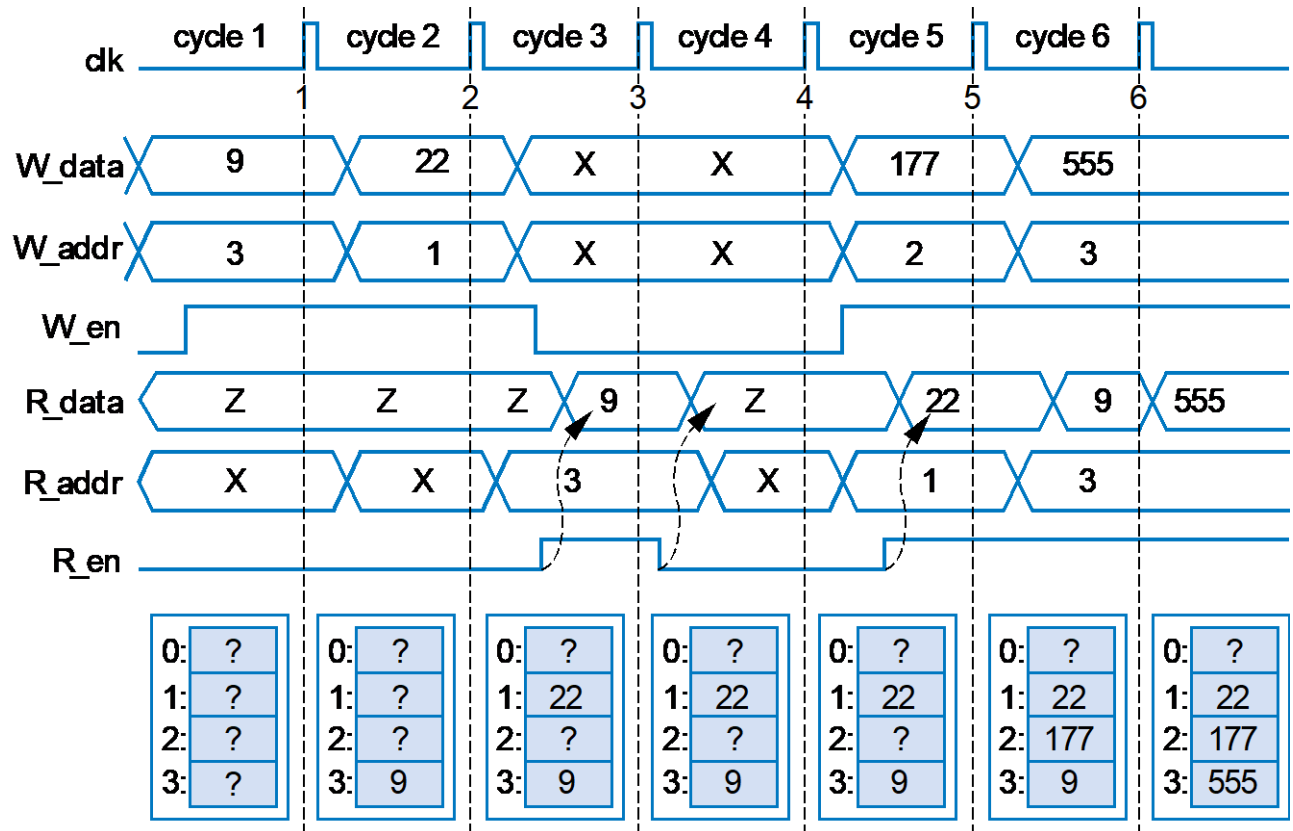- Can write one register and read one register each clock cycle
 - May be same register







Register-File Example: Above-Mirror Display

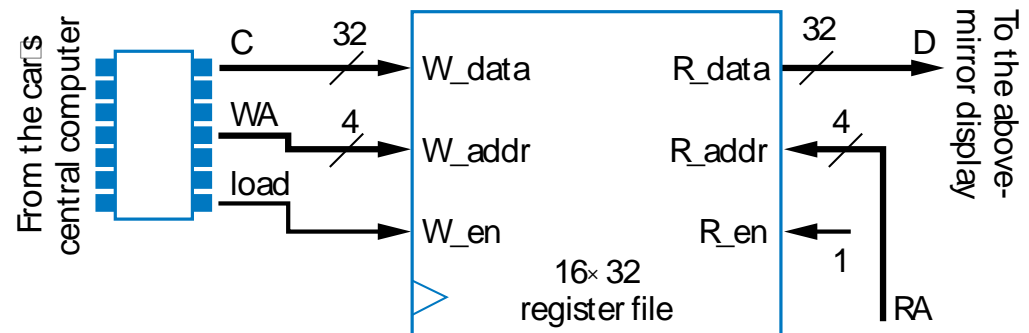- 16 32-bit registers that can be written by car's computer, and displayed
 - Use 16x32 register file
 - Simple, elegant design
- Register file hides complexity internally
 - And because only one register needs to be written and/or read at a time, internal design is simple






Register File

    - Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read




Register File Timing Diagram

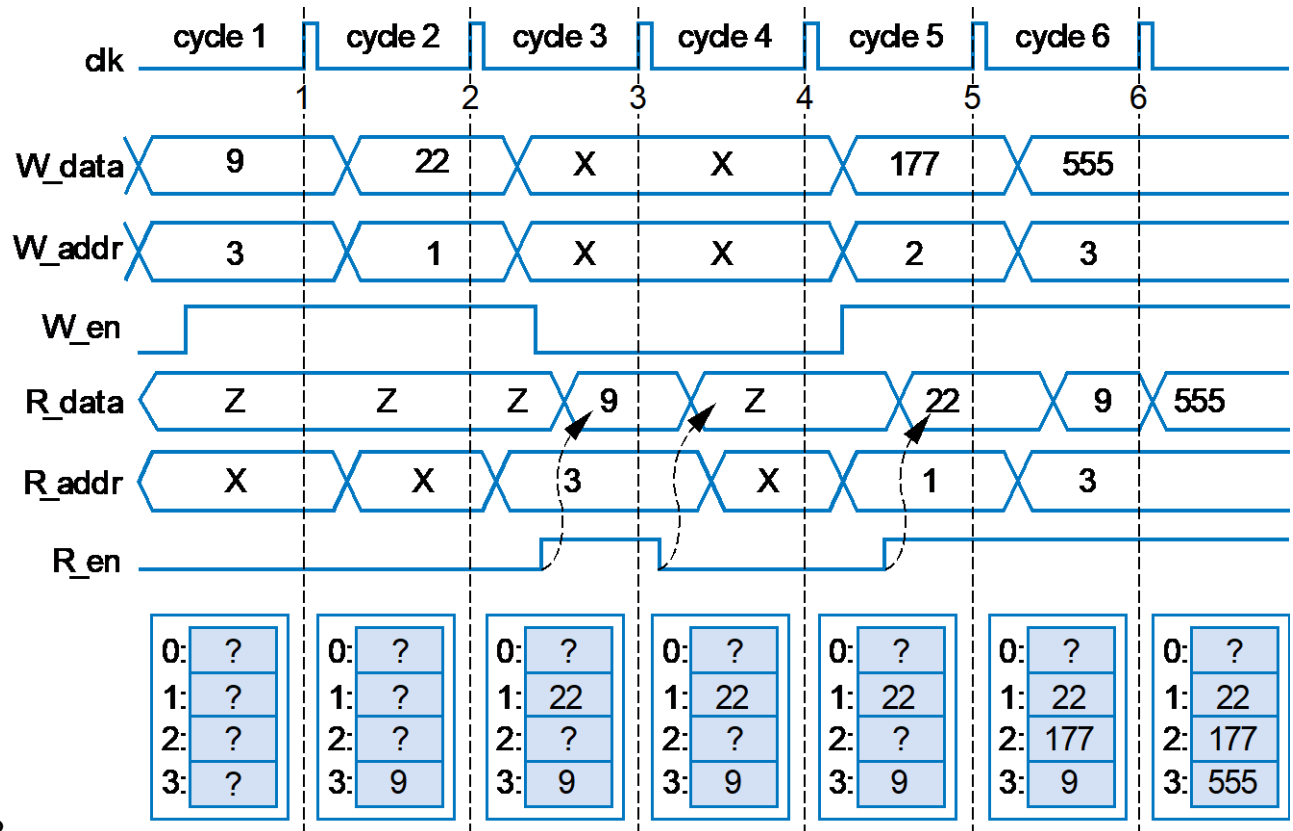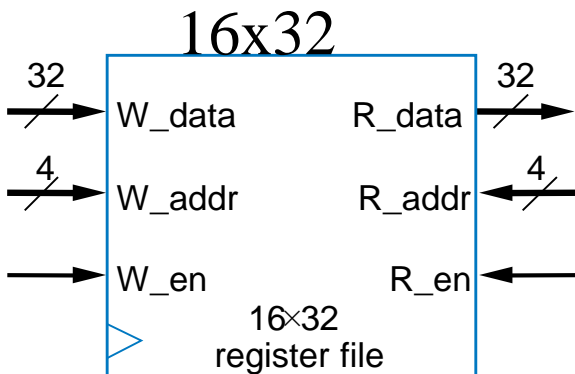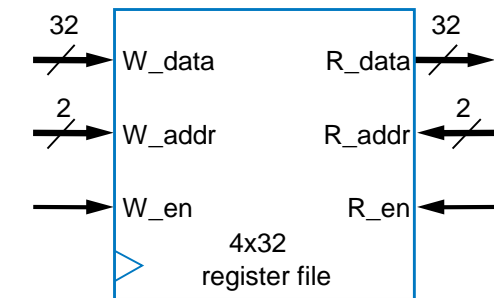
- Can write one register and read one register each clock cycle
 - May be same register




Register File -size

 


32x32

 

16x32

 


64x64


 


ALU Example:

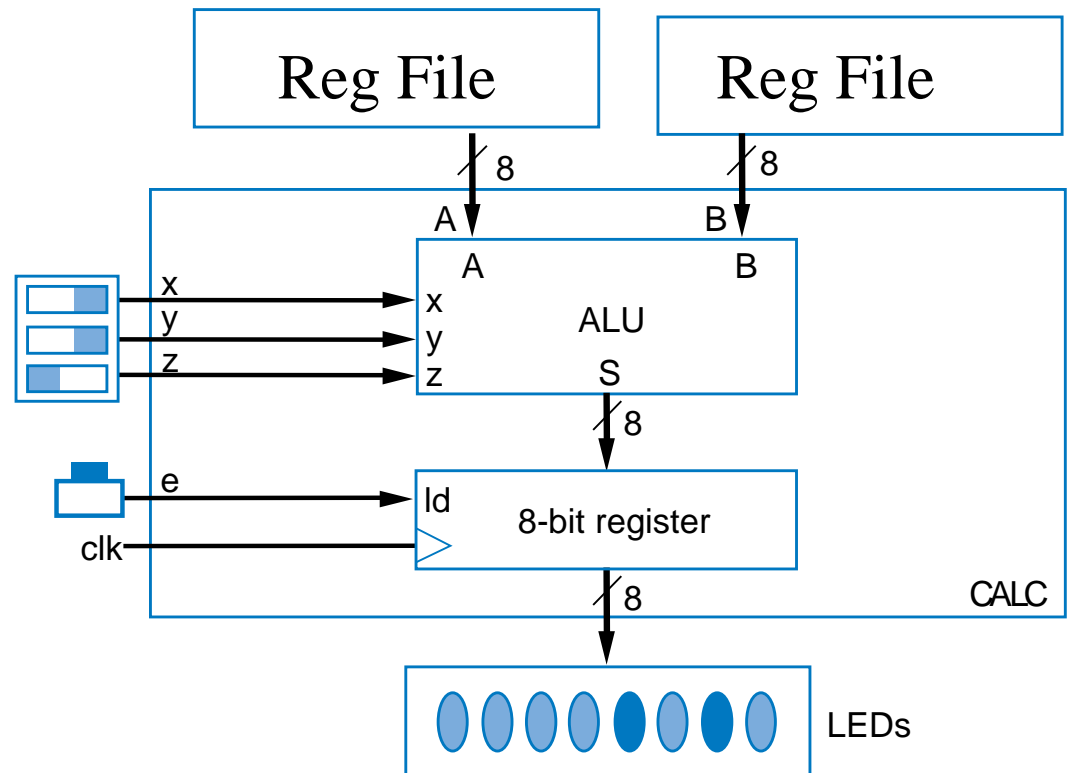
- Design using ALU is elegant and efficient



Register File with Two Ports

 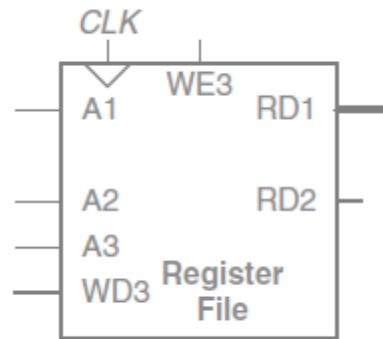

ALU Example:

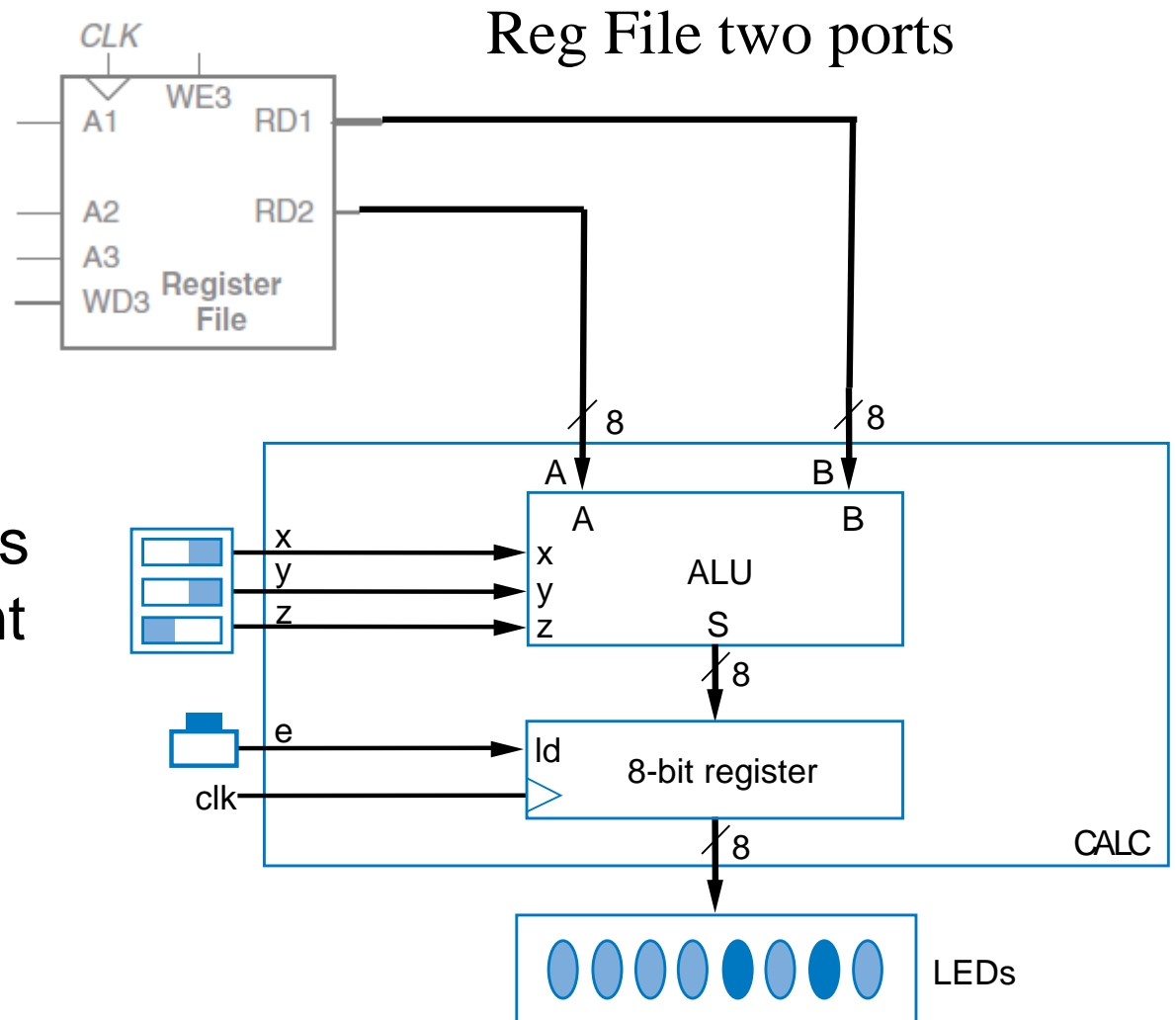

- Design using ALU is elegant and efficient