

# *Digital Systems -Sequential Logic*

---

# Introduction

- Outputs of sequential logic depend on current *and* prior input values – it has *memory*.
- Some definitions:
  - **State**: all the information about a circuit necessary to explain its future behavior
  - **Latches and flip-flops**: state elements that store one bit of state
  - **Synchronous sequential circuits**: combinational logic followed by a bank of flip-flops

# Sequential Circuits



- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information

# State Elements

- The state of a circuit influences its future behavior
- State elements store state
  - Bistable circuit
  - SR Latch
  - D Latch
  - D Flip-flop

  
# Bistable Circuit

- Fundamental building block of other state elements
- Two outputs:  $Q$ ,  $\overline{Q}$
- No inputs



 
# Bistable Circuit Analysis

- Consider the two possible cases:
  - $Q = 0$ : then  $\bar{Q} = 1$  and  $Q = 0$  (consistent)



 
- $Q = 1$ : then  $\bar{Q} = 0$  and  $Q = 1$  (consistent)



- Bistable circuit stores 1 bit of state in the state variable, Q (or  $\bar{Q}$ )
- But there are **no inputs to control the state**

# SR (Set/Reset) Latch


- SR Latch

 


- Consider the four possible cases:
  - $S = 1, R = 0$
  - $S = 0, R = 1$
  - $S = 0, R = 0$
  - $S = 1, R = 1$
 
# SR Latch Analysis

- $S = 1, R = 0$ : then  $Q = 1$  and  $\overline{Q} = 0$



 
- $S = 0, R = 1$ : then  $Q = 0$  and  $\overline{Q} = 1$





 
# SR Latch Analysis

- $S = 1, R = 0$ : then  $Q = 1$  and  $\overline{Q} = 0$



 
- $S = 0, R = 1$ : then  $Q = 0$  and  $\overline{Q} = 1$




# SR Latch Analysis

- $S = 0, R = 0$ : then  $Q = Q_{prev}$


$$Q_{prev} = 0$$

 

$$Q_{prev} = 1$$


 


 - $S = 1, R = 1$ : then  $Q = 0$  and  $\overline{Q} = 0$



  
# SR Latch Analysis

- $S = 0, R = 0$ : then  $Q = Q_{prev}$  and  $\bar{Q} = \overline{Q_{prev}}$  (**memory!**)



 
- $S = 1, R = 1$ : then  $Q = 0$  and  $\bar{Q} = 0$  (**invalid state**:  $\bar{Q} \neq \text{NOT } Q$ )



# SR Latch Symbol

- SR stands for Set/Reset Latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  inputs
  - **Set:** Make the output 1 ( $S = 1$ ,  $R = 0$ ,  $Q = 1$ )
  - **Reset:** Make the output 0 ( $S = 0$ ,  $R = 1$ ,  $Q = 0$ )
- **Must do something to avoid invalid state (when  $S = R = 1$ )**


## SR Latch Symbol

 


# D Latch

- Two inputs:  $CLK$ ,  $D$ 
  - $CLK$ : controls *when* the output changes
  - $D$  (the data input): controls *what* the output changes to
- Function
  - When  $CLK = 1$ ,  $D$  passes through to  $Q$  (the latch is *transparent*)
  - When  $CLK = 0$ ,  $Q$  holds its previous value (the latch is *opaque*)
- Avoids invalid case when  $Q \neq \text{NOT } \overline{Q}$

D Latch  
Symbol

 


# D Latch Internal Circuit

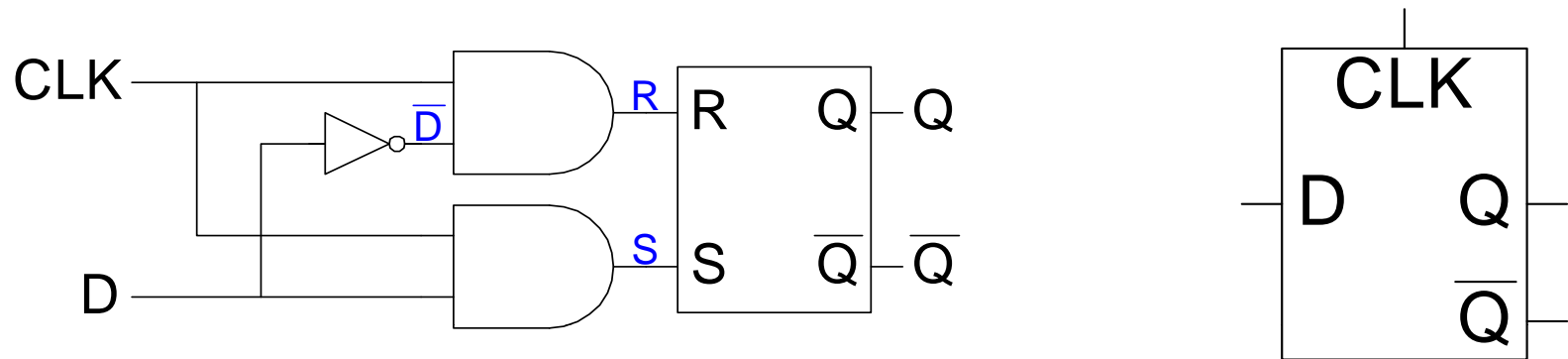

$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X					
1	0					
1	1					

# D Latch Internal Circuit

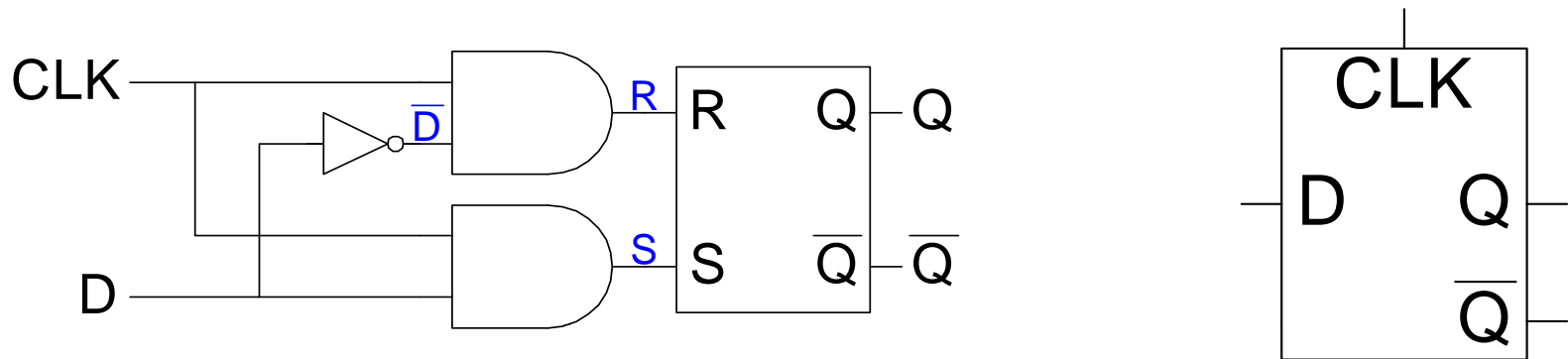


$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X	X	0	0	$Q_{prev}$	$\overline{Q}_{prev}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0

# D Flip-Flop



- Two inputs:  $CLK$ ,  $D$
- *Function*
  - The flip-flop “samples”  $D$  on the rising edge of  $CLK$ 
    - When  $CLK$  rises from 0 to 1,  $D$  passes through to  $Q$
    - Otherwise,  $Q$  holds its previous value
  - $Q$  changes only on the rising edge of  $CLK$
- A flip-flop is called an *edge-triggered* device because it is activated on the clock edge

D Flip-Flop  
Symbols



 




# D Latch

  


# D Latch

   
 
# Sequential Logic



- Sequential circuits: all circuits that aren't combinational
- A problematic circuit:



- This circuit has no inputs and 1-3 outputs
  
# Sequential Logic

- Sequential circuits: all circuits that aren't combinational
- A problematic circuit:



- This circuit has no inputs and 1-3 outputs
- It is an astable circuit that oscillates
- Its period depends on the delay of the inverters – which depends on the manufacturing process, temperature, etc
- The circuit has a *cyclic path*: output fed back to input