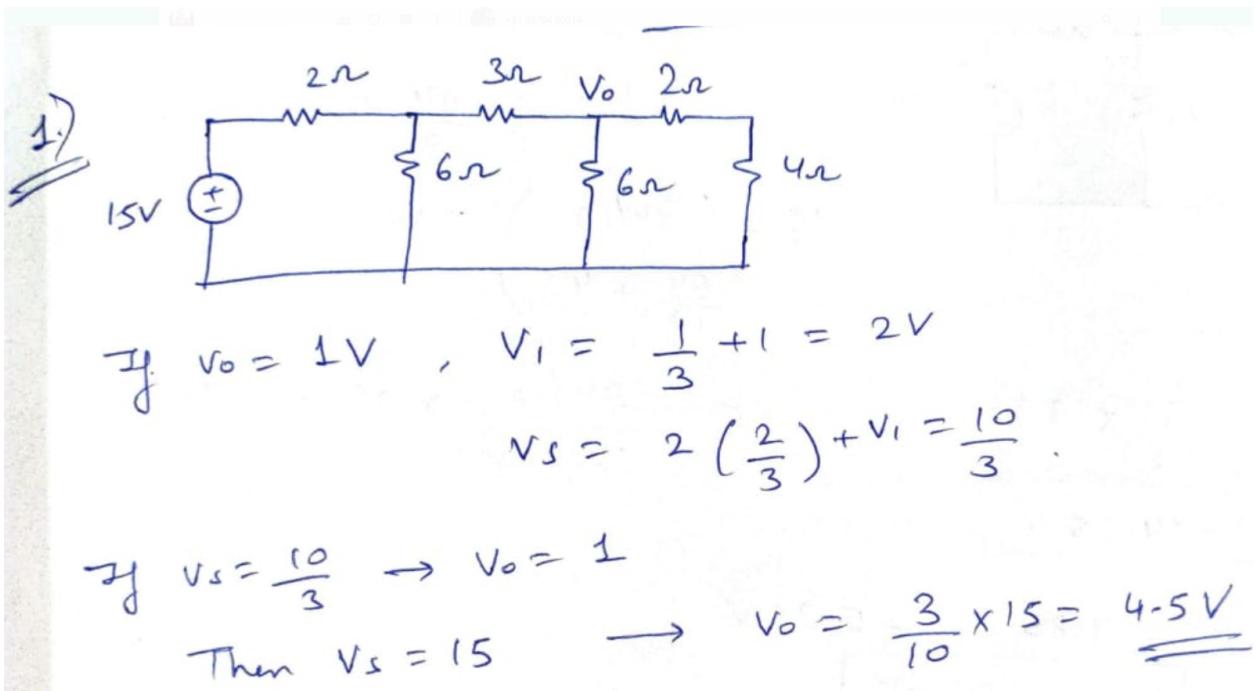


EE101 Tutorial 11 Solution Sheet


1.



2.

2.7

$V_o = ?$ using superposition principle.

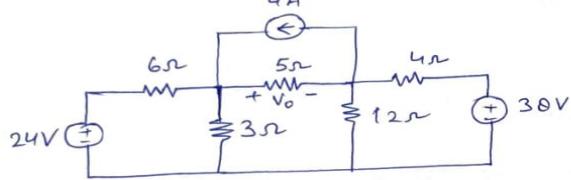


$$V_o = V_{o1} + V_{o2} + V_{o3}$$

$$V_{o1} \rightarrow 4A$$

$$V_{o2} \rightarrow 24V$$


$$V_{o3} \rightarrow 38V$$

For $V_{o1} \rightarrow$

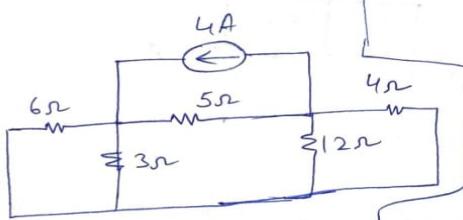


$$3/1/6 = 2\Omega$$

$$4/1/12 = 3\Omega$$

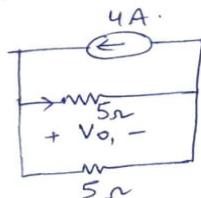

$$V_{o1} = 5 \times 2$$

$$V_{o1} = 10V$$

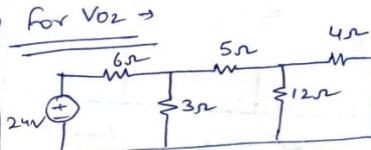

$$4/1/12 = 3\Omega$$

$$3+5=8\Omega$$

$$3/1/8 = \frac{24}{11}$$

$$V_1 = \left(\frac{24}{11} \right) \times 24$$

$$= \frac{8^4}{24/11} \times 24$$

$$= 96/11 \times 24$$


$$= 32/5$$

$$V_{o2} = \frac{5 \times V_1}{8} = \frac{5}{8} \times \frac{32}{5}$$

$$V_{o2} = 4V$$

For $V_{o3} \rightarrow$

PTO

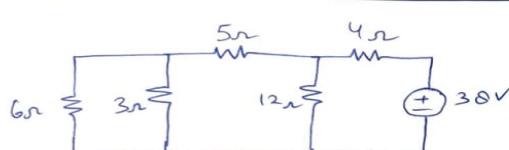

$$6/1/3 = 2\Omega$$

$$2+5=7\Omega$$

$$7/1/12 = \frac{84}{19}\Omega$$

$$V_2 = \left(\frac{84/19}{\frac{84}{19} + 4} \right) \times 38$$

$$= \frac{84/19}{160/19} \times 38 = 19.95$$


$$V_{o3} = -\frac{5}{7} \times 19.95$$

$$V_{o3} = -14.25V$$



$$V_o = 10 + 4 - 14.25 = -0.25V$$

$$V_o = -250mV$$

3.

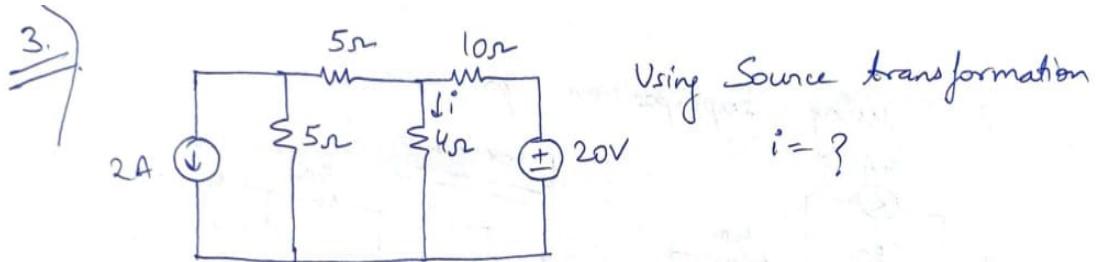

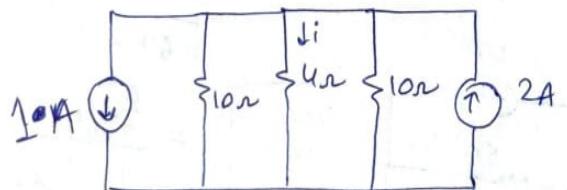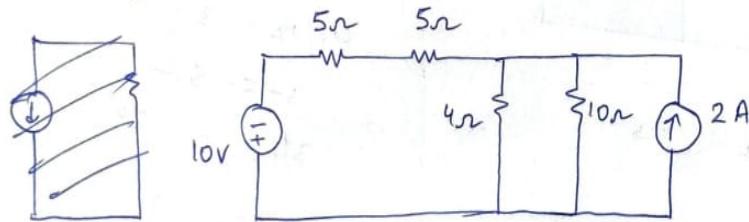Transforming the voltage source and current source



$$10//10 = 5\Omega$$


$$i = \frac{5}{5+4} \times (2-1) = \frac{5}{9} = 555.5 \text{ mA}$$

$$\boxed{i = 555.5 \text{ mA}}$$


4.

4.)

Using source transformation, find V_x

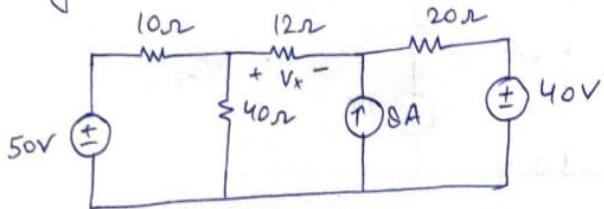


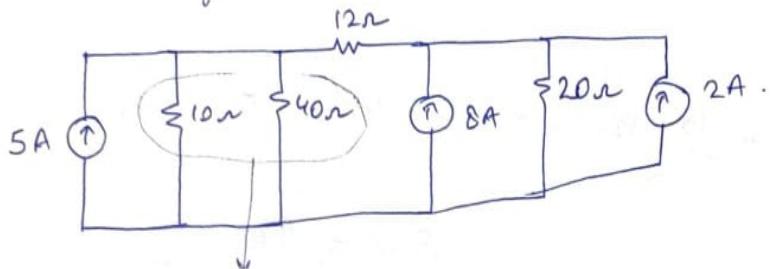\Downarrow
Voltage source \rightarrow current source.



$$10/40 = 8\Omega$$

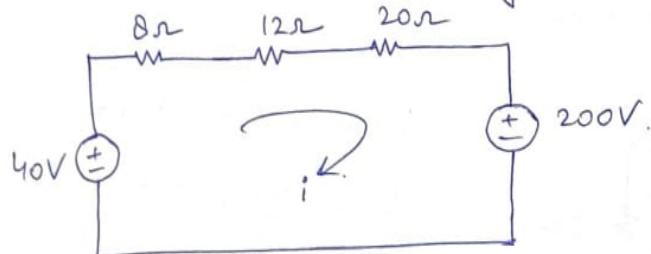current source \rightarrow voltage source.



Applying KVL.



$$-40 + (8+12+20)i + 200 = 0$$

$$i = -4 \text{ A}$$

$$V_x = 12i = 12 \times (-4)$$

$$V_x = -48 \text{ V}$$

5.

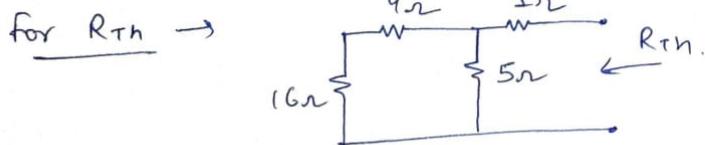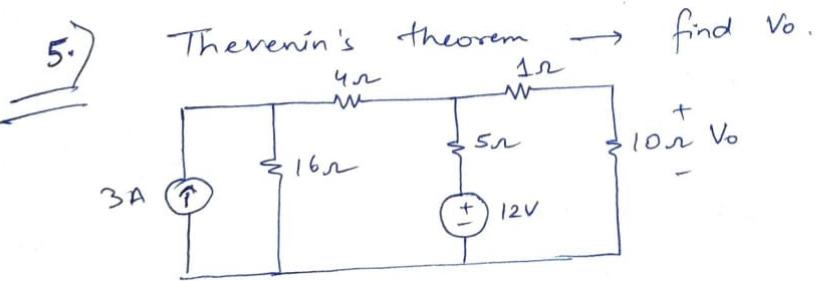


$$(16+4) \parallel 5 + 1 = R_{Th}$$

$$R_{Th} = \frac{20 \times 8}{28} + 1$$

$$R_{Th} = 5 \Omega$$

For $V_{Th} \rightarrow$

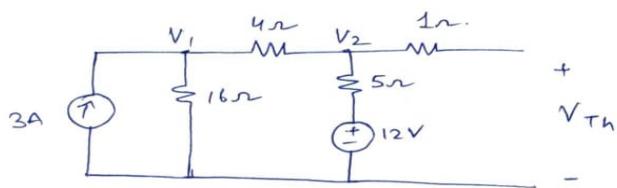

At node 1

$$3 = \frac{V_1}{16} + \frac{V_1 - V_2}{4} = 48 = 5V_1 - 4V_2 \quad \text{---(1)}$$

At node 2


$$\frac{V_1 - V_2}{4} + \frac{12 - V_2}{5} = 0 = 48 = -5V_1 + 9V_2 \quad \text{---(2)}$$

$$5V_2 = 96$$

$$V_2 = 19.2 \text{ V}$$

$$V_{Th} = V_2 = 19.2 \text{ V}$$

Now,

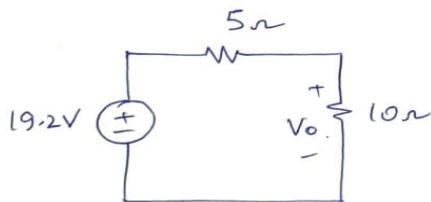

Using Voltage division.


$$V_o = \frac{10}{15} \times 19.2$$

$$V_o = 12.8 \text{ V}$$


6.

6)

Norton Equivalent → find current i .

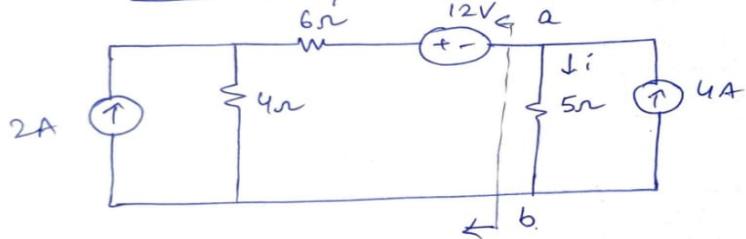


for R_N :-

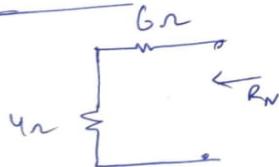

$$R_N = 6 + 4 = 10\Omega$$

for I_N :-

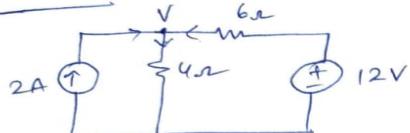


$$\begin{aligned} 2 + \frac{12-v}{6} &= \frac{v}{4} \\ \frac{12-v}{6} - \frac{v}{4} &= -2 \\ \frac{2(12-v) - 3v}{12} &= -2 \end{aligned}$$

$$\begin{aligned} \frac{24 - 2v - 3v}{12} &= -2 \\ 24 - 5v &= -24 \\ 24 + 24 &= 5v \\ v &= 9.6V \end{aligned}$$

$$-I_N = \frac{12-v}{6} = \frac{12-9.6}{6} = 0.4$$


$$I_N = -0.4A$$

Eq. ckt.

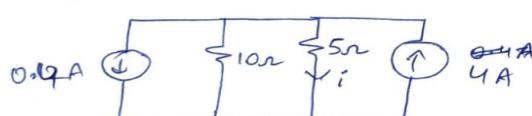


$$\begin{aligned} i &= \frac{\frac{2}{10} \times (4 - 0.4)}{\frac{18}{3}} \\ &= \frac{2}{3} \times 3.6 \\ i &= 2.4A \end{aligned}$$

7. Solution-1

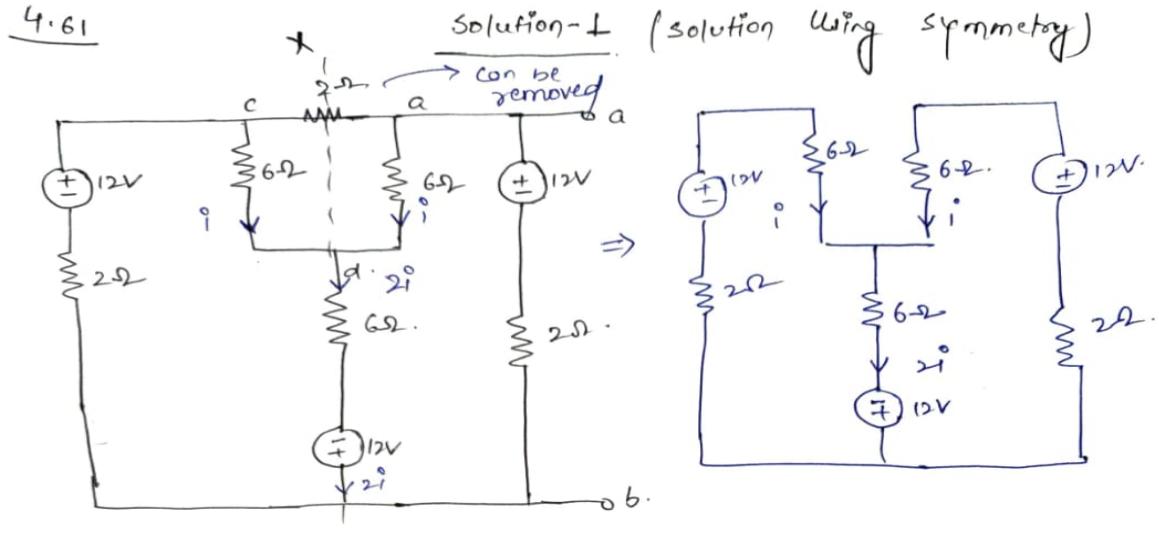

- Circuit is symmetrical at XY
- $V_a = V_c$ as 2Ω can be removed
- Currents in branches c-d and a-d will be same

Let i
splitting above circuit:-

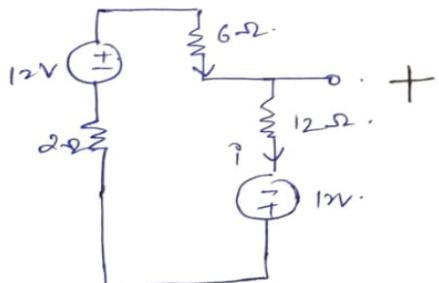

Applying KVL :-

$$-12 + 6i + 12i - 12 + 2i = 0 \Rightarrow -24 + 20i = 0 \Rightarrow i = 1.2A$$



Also,

$$V_{ab} = 12 - 2i \\ = 9.6V$$

Solution-2


4.61 Solution-2 (Y-Δ conversion)

To find R_m :

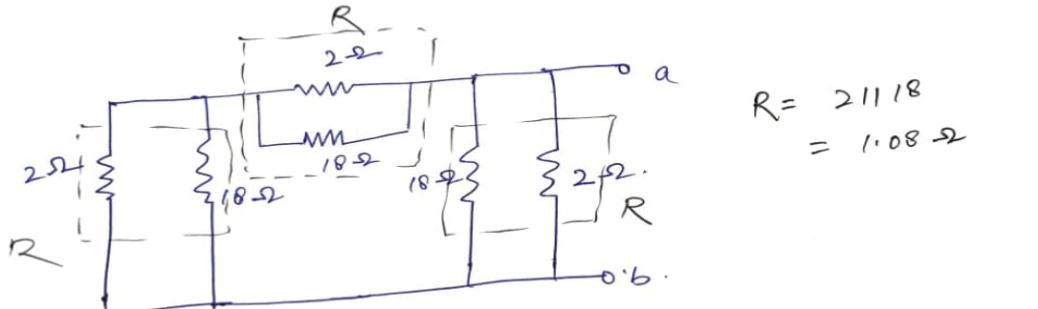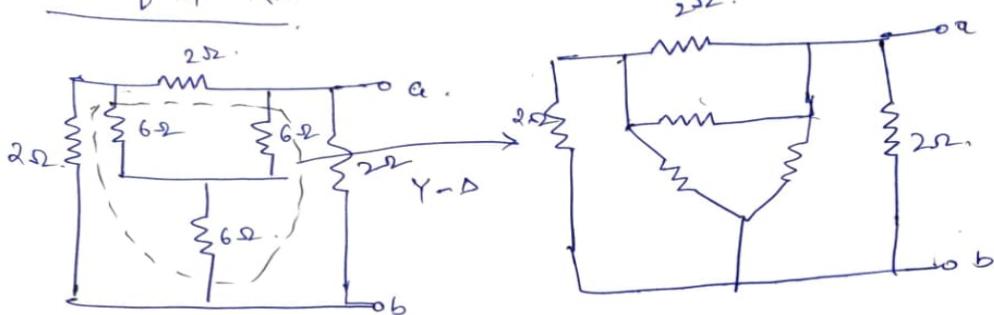

$$R = \frac{21}{11} \Omega = 1.08 \Omega$$

$$R_m = (R+R) // R = 1.2 \Omega$$

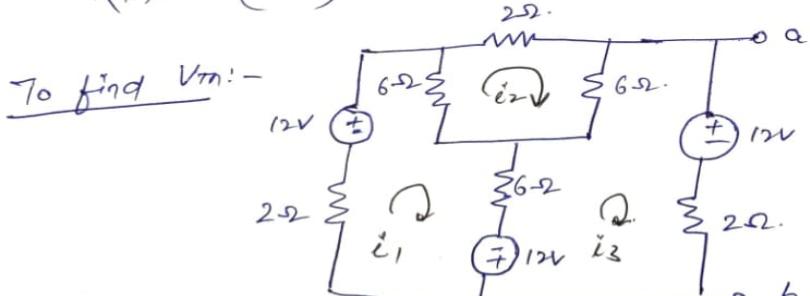

$$\text{Applying Mesh analysis: } 2i_1 - 12 + 6(i_1 - i_2) + 6(i_1 - i_3) - 12 = 0 \quad (I)$$

$$\text{Mesh 1: } 14i_1 - 6i_2 - 6i_3 - 24 = 0 \quad (II)$$


$$\text{Mesh 2: } 14i_2 - 6i_1 - 6i_3 = 0 \quad (III)$$

$$\text{Mesh 3: } -3i_1 - 7i_2 - 3i_3 = -12 \quad (IV)$$

$$\text{Solving } (I), (II) \text{ & } (IV) \quad i_3 = -1.2 \text{ A}$$

$$V_m = 12 + 2i_2 = 9.6 \text{ V} \quad / \quad I_N = \frac{V_m}{R_m} = 8 \text{ A}$$

Solution-3

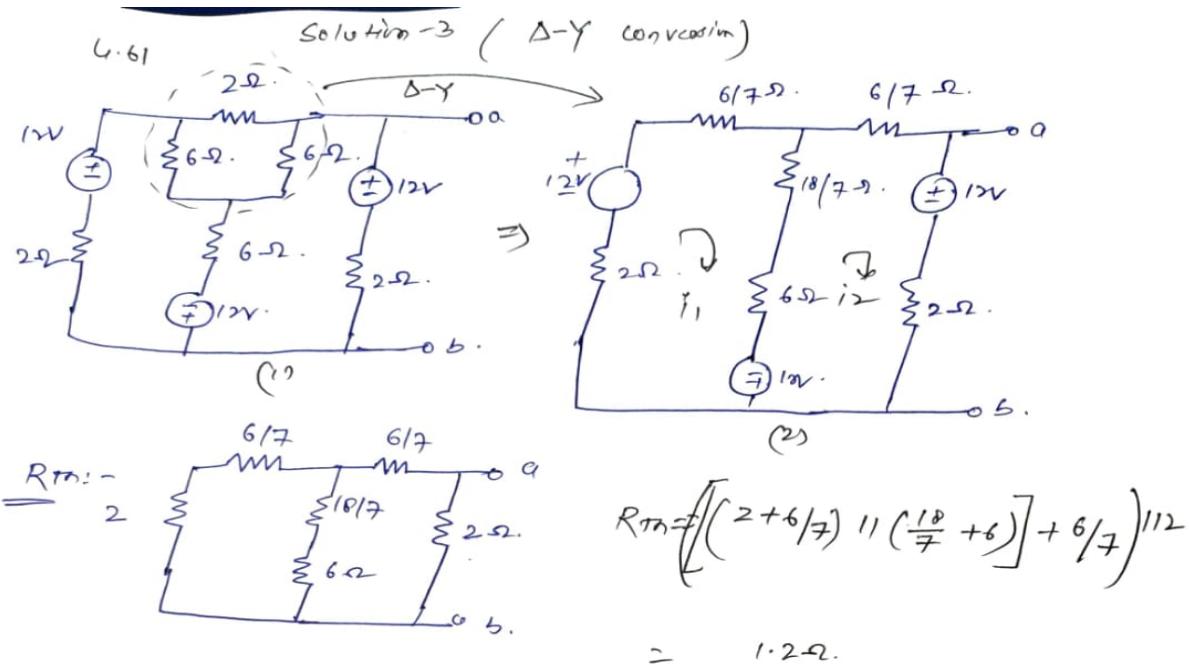

V_{Th}: Applying Mesh analysis in fig.(2)

$$-12 + 2i_1 + \frac{6}{7}i_1 + \frac{18}{7}i_2 + 6i_1 - 12 - \frac{18}{7}i_2 - 6i_2 = 0$$

$$-24 + \left(2 + \frac{6}{7} + \frac{18}{7} + 6 \right) i_1 - \left(6 + \frac{18}{7} \right) i_2 = 0 \quad \text{--- (1)}$$

$$12 + 6(i_2 - i_1) + \frac{18}{7}(i_2 - i_1) + \frac{6}{7}i_2 + 12 + 2i_2 = 0$$

$$24 + \left(6 + \frac{18}{7} + \frac{6}{7} + 2 \right) i_2 - \left(6 + \frac{18}{7} \right) i_1 = 0 \quad \text{--- (2)}$$

Solving (1) & (2)

$$V_{Th} = 9.6V \quad / \quad I_N = \frac{V_{Th}}{R_{Th}} = 8A$$

8.

To find $V_{Th} = V_x$, consider the left loop.

$$-3 + 1000i_o + 2V_x = 0 \quad \longrightarrow \quad 3 = 1000i_o + 2V_x \quad (1)$$

For the right loop,


$$V_x = -50 \times 40i_o = -2000i_o \quad (2)$$

Combining (1) and (2),

$$3 = 1000i_o - 4000i_o = -3000i_o \quad \longrightarrow \quad i_o = -1\text{mA}$$

$$V_x = -2000i_o = 2 \quad \longrightarrow \quad \underline{V_{Th} = 2}$$

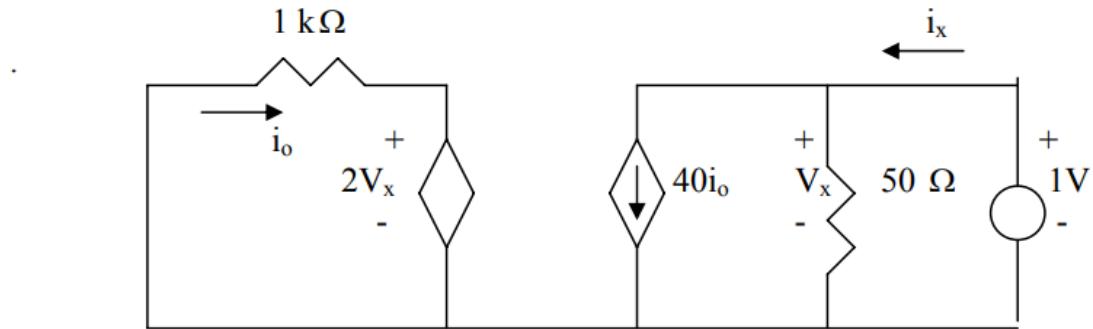To find R_{Th} , insert a 1-V source at terminals a-b and remove the 3-V independent source, as shown below.




$$V_x = 1, \quad i_o = -\frac{2V_x}{1000} = -2\text{mA}$$

$$i_x = 40i_o + \frac{V_x}{50} = -80\text{mA} + \frac{1}{50}\text{A} = -60\text{mA}$$

$$R_{Th} = \frac{1}{i_x} = -1/0.060 = \underline{-16.67\Omega}$$

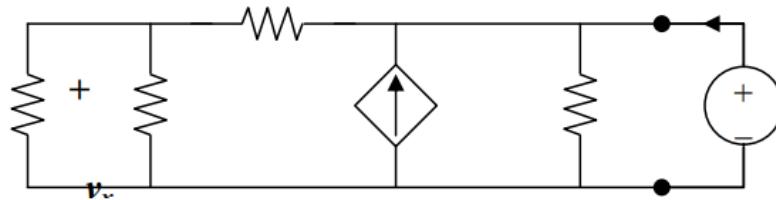9.

To find R_{Th} , remove the 50V source and insert a 1-V source at a – b, as shown in Fig. (a).



We apply nodal analysis. At node A,

$$i + 0.5v_x = (1/10) + (1 - v_x)/2, \text{ or } i + v_x = 0.6 \quad (1)$$


At node B,

$$(1 - v_0)/2 = (v_x/3) + (v_x/6), \text{ and } v_x = 0.5 \quad (2)$$

From (1) and (2), $i = 0.1$ and

$$R_{Th} = 1/i = \underline{\mathbf{10 \text{ ohms}}}$$

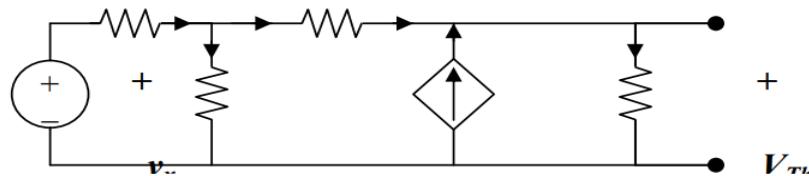To get V_{Th} , consider the circuit in Fig. (b).



$$\text{At node 1, } (50 - v_1)/3 = (v_1/6) + (v_1 - v_2)/2, \text{ or } 100 = 6v_1 - 3v_2 \quad (3)$$

$$\text{At node 2, } 0.5v_x + (v_1 - v_2)/2 = v_2/10, \text{ } v_x = v_1, \text{ and } v_1 = 0.6v_2 \quad (4)$$

From (3) and (4),


$$v_2 = V_{Th} = \underline{\mathbf{166.67 \text{ V}}}$$

$$I_N = V_{Th}/R_{Th} = \underline{\mathbf{16.667 \text{ A}}}$$

$$R_N = R_{Th} = \underline{\mathbf{10 \text{ ohms}}}$$

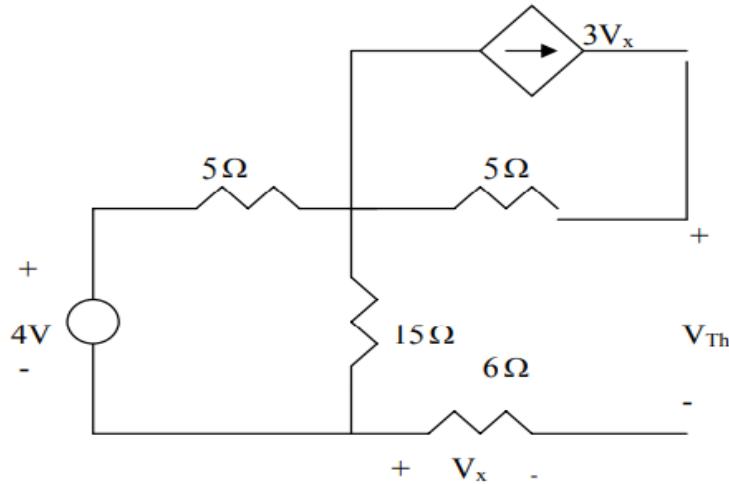
10.

We find the Thevenin equivalent across the 10-ohm resistor. To find V_{Th} , consider the circuit below.



$$V_x = 0, \quad V_{Th} = \frac{15}{15+5}(4) = 3V$$

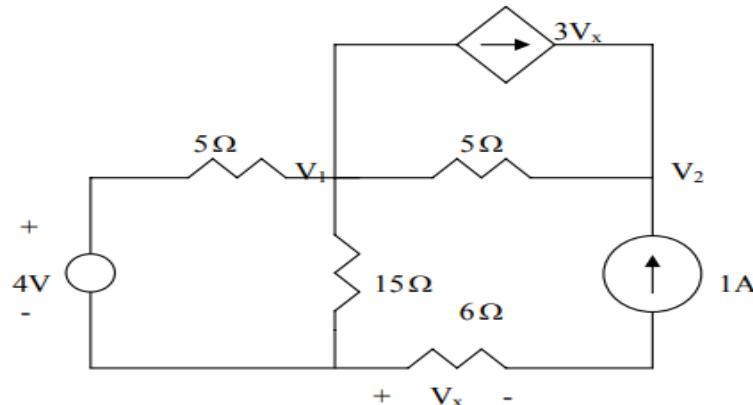To find R_{Th} , consider the circuit below:



At node 1,

$$\frac{4-V_1}{5} = 3V_x + \frac{V_1}{15} + \frac{V_1 - V_2}{5}, \quad V_x = 6 \times 1 = 6 \quad \longrightarrow \quad 258 = 3V_2 - 7V_1 \quad (1)$$

At node 2,

$$1 + 3V_x + \frac{V_1 - V_2}{5} = 0 \quad \longrightarrow \quad V_1 = V_2 - 95 \quad (2)$$

Solving (1) and (2) leads to $V_2 = 101.75$ V

$$R_{Th} = \frac{V_2}{1} = 101.75\Omega, \quad P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{9}{4 \times 101.75} = 22.11 \text{ mW}$$

