

Datapath

Adders


- Adds two N-bit binary numbers
 - 2-bit adder: adds two 2-bit numbers, outputs 3-bit result
 - e.g., $01 + 11 = 100$ ($1 + 3 = 4$)
- Can design using combinational design process , but doesn't work well for reasonable-size N
 - Why not?

Inputs				Outputs		
a1	a0	b1	b0	c	s1	s0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Why Adders Aren't Built Using Standard Combinational Design Process

- Truth table too big
 - 2-bit adder's truth table shown
 - Has $2^{(2+2)} = 16$ rows
 - 8-bit adder: $2^{(8+8)} = 65,536$ rows
 - 16-bit adder: $2^{(16+16)} = \sim 4$ billion rows
 - 32-bit adder: ...
- Big truth table with numerous 1s/0s yields big logic
 - Plot shows number of transistors for N-bit adders, using state-of-the-art automated combinational design tool

Inputs				Outputs		
a1	a0	b1	b0	c	s1	s0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	0
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

 


Q: Predict number of transistors for 16-bit adder

A: 1000 transistors for N=5, doubles for each increase of N. So transistors = $1000 \cdot 2^{(N-5)}$. Thus, for N=16, transistors = $1000 \cdot 2^{(16-5)} = 1000 \cdot 2048 = 2,048,000$. Way too many!


Alternative Method to Design an Adder: Imitate Adding by Hand

 - Alternative adder design: mimic how people do addition by hand
- One column at a time
 - Compute sum, add carry to next column



Alternative Method to Design an Adder: Imitate Adding by Hand

 - Create component for each column
 - Adds that column's bits, generates sum and carry bits



Half-Adder

- **Half-adder**: Adds 2 bits, generates sum and carry
- Design using combinational design process from Ch 2

Step 1: Capture the function



Inputs		Outputs	
a	b	co	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Step 2: Convert to equations

$$co = ab$$


$$s = a'b + ab' \text{ (same as } s = a \text{ xor } b)$$

Step 3: Create the circuit

  

Full-Adder

 - **Full-adder:** Adds 3 bits, generates sum and carry
- Design using combinational design process from Ch 2



Step 1: Capture the function

Inputs			Outputs	
a	b	ci	co	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Step 2: Convert to equations

$$co = a'bc + ab'c + abc' + abc$$

$$co = a'bc + abc + ab'c + abc + abc' + abc$$

$$co = (a' + a)bc + (b' + b)ac + (c' + c)ab$$

$$co = bc + ac + ab$$


$$s = a'b'c + a'bc' + ab'c' + abc$$

$$s = a'(b'c + bc') + a(b'c' + bc)$$

$$s = a'(b \text{ xor } c)' + a(b \text{ xor } c)$$


$$s = a \text{ xor } b \text{ xor } c$$

Step 3: Create the circuit

 


Carry-Ripple Adder

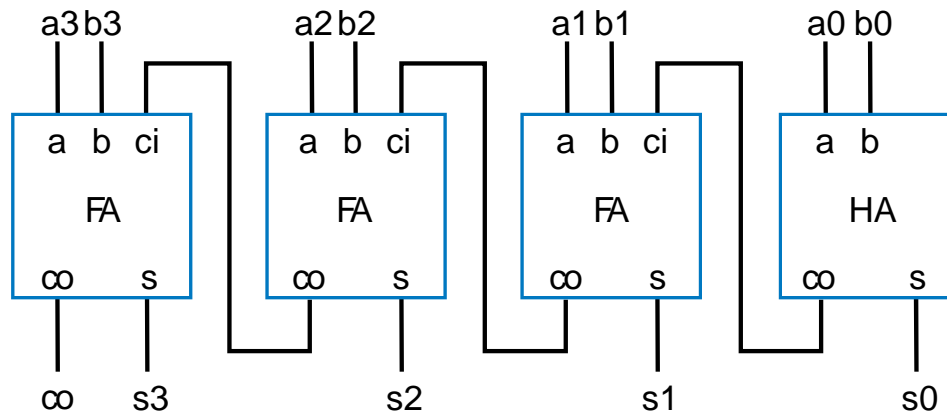- Using half-adder and full-adders, we can build adder that adds like we would by hand
- Called a **carry-ripple adder**
 - 4-bit adder shown: Adds two 4-bit numbers, generates 5-bit output
 - 5-bit output can be considered 4-bit “sum” plus 1-bit “carry out”
 - Can easily build any size adder




(a)

 


(b)

Carry-Ripple Adder

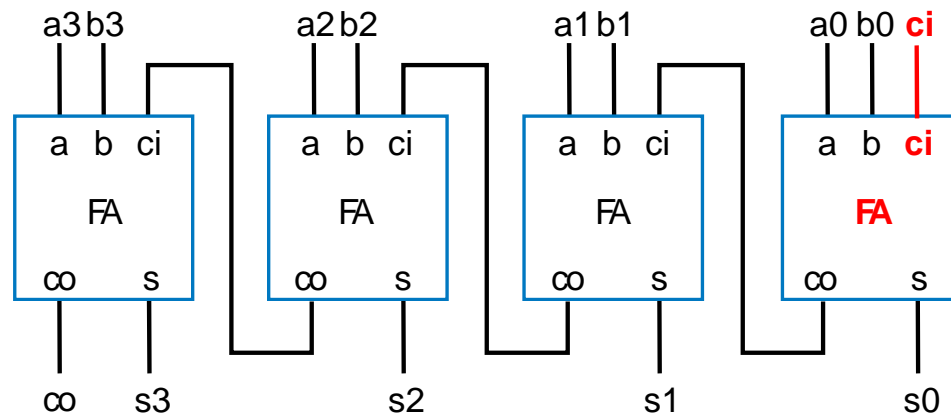- Using full-adder instead of half-adder for first bit, we can include a “carry in” bit in the addition
 - Will be useful later when we connect smaller adders to form bigger adders




(a)

 


(b)

Carry-Ripple Adder's Behavior

 

Assume all inputs initially 0

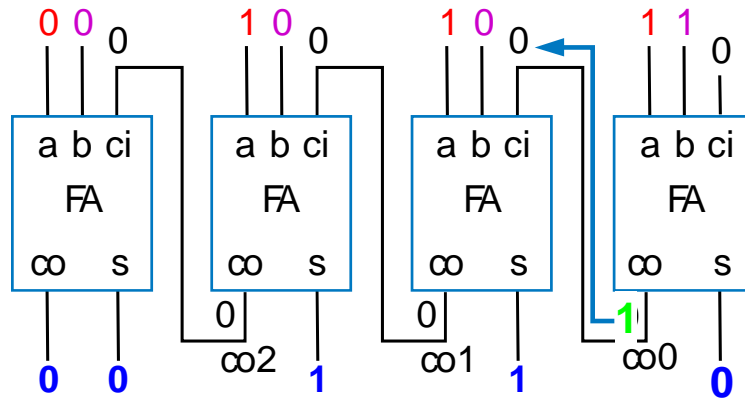


0111+0001
(answer should be 01000)

Output after 2 ns (1FA delay)


Wrong answer -- something wrong? No -- just need more time for carry to ripple through the chain of full adders.

Carry-Ripple Adder's Behavior

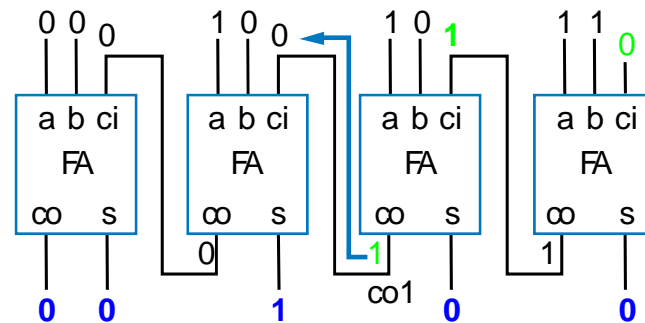


0111+0001
(answer should be 01000)

Outputs after 4ns (2 FA delays)

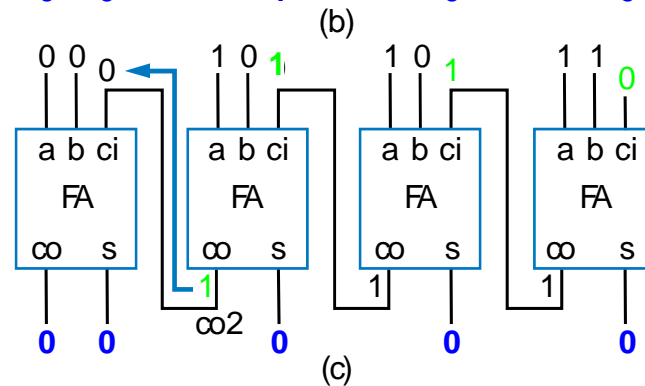



Outputs after 6ns (3 FA delays)

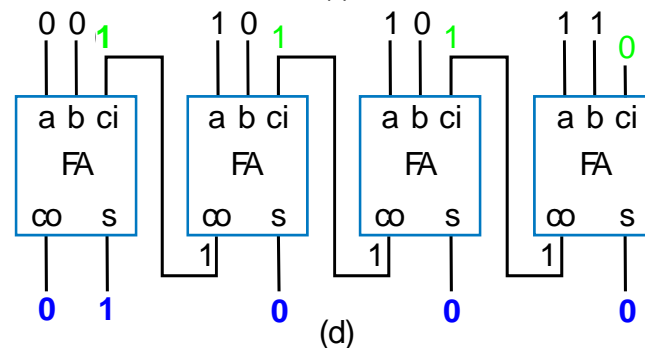

Output after 8ns (4 FA delays)

Correct answer appears after 4 FA delays

Cascading Adders

 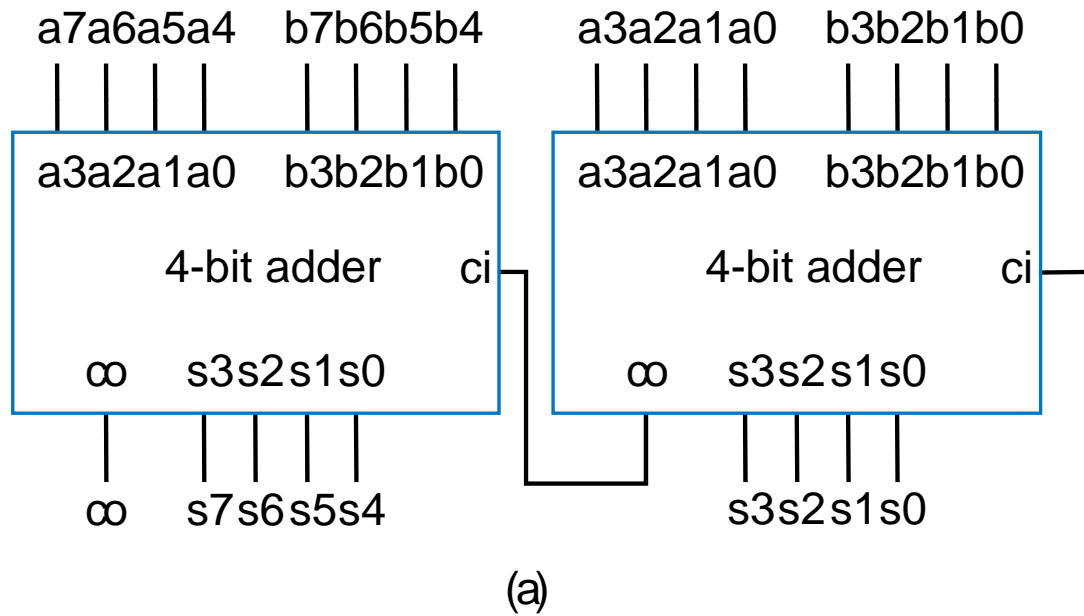

Multiplier – Array Style

- Can build multiplier that mimics multiplication by hand
 - Notice that multiplying multiplicand by 1 is same as ANDing with 1

0110	(the top number is called the <i>multiplicand</i>)
0011	(the bottom number is called the <i>multiplier</i>)
----	(each row below is called a <i>partial product</i>)
0110	(because the rightmost bit of the multiplier is 1, and $0110 * 1 = 0110$)
0110	(because the second bit of the multiplier is 1, and $0110 * 1 = 0110$)
0000	(because the third bit of the multiplier is 0, and $0110 * 0 = 0000$)
+0000	(because the leftmost bit of the multiplier is 0, and $0110 * 0 = 0000$)

00010010	(the <i>product</i> is the sum of all the partial products: 18, which is $6 * 3$)


Multiplier – Array Style


- Generalized representation of multiplication by hand

				a3	a2	a1	a0	
				x b3	b2	b1	b0	

				b0a3	b0a2	b0a1	b0a0	(pp1)
			b1a3	b1a2	b1a1	b1a0	0	(pp2)
		b2a3	b2a2	b2a1	b2a0	0	0	(pp3)
+	b3a3	b3a2	b3a1	b3a0	0	0	0	(pp4)


p7	p6	p5	p4	p3	p2	p1	p0	

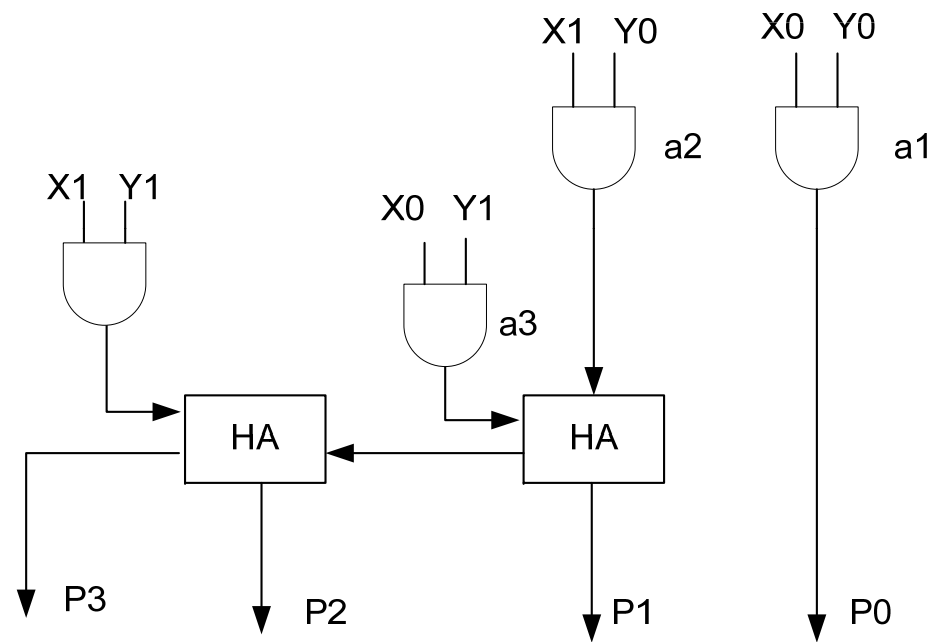

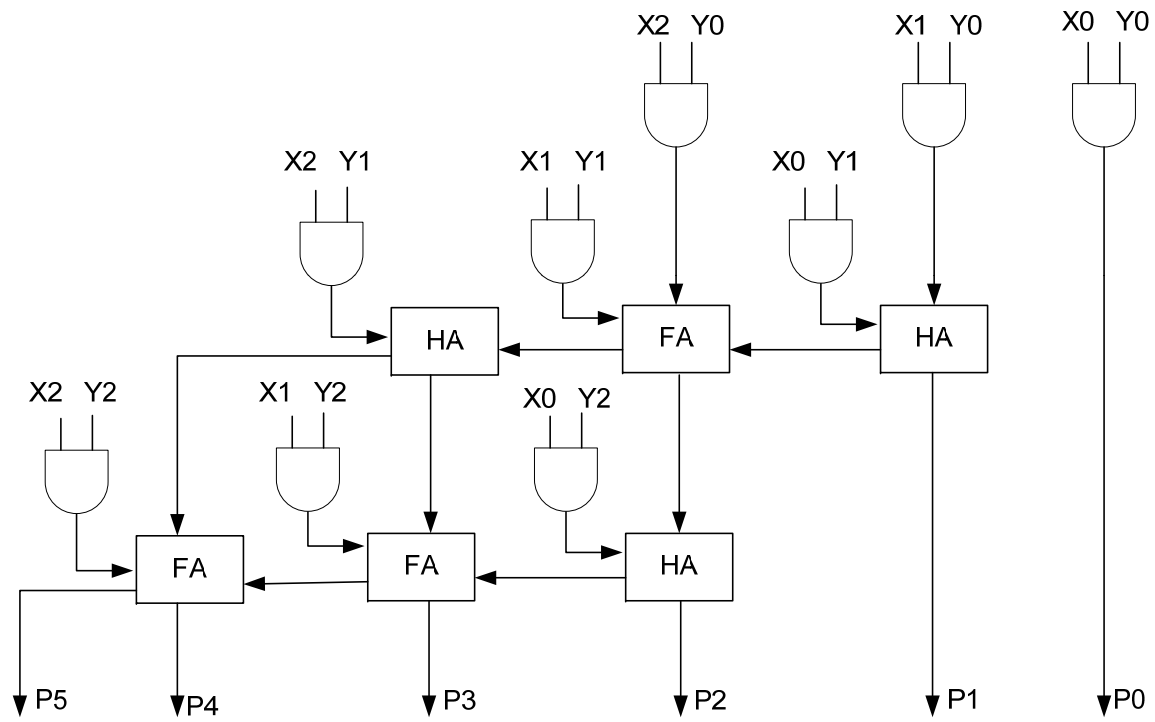



Multiplier – Array Style

- Multiplier design – array of AND gates

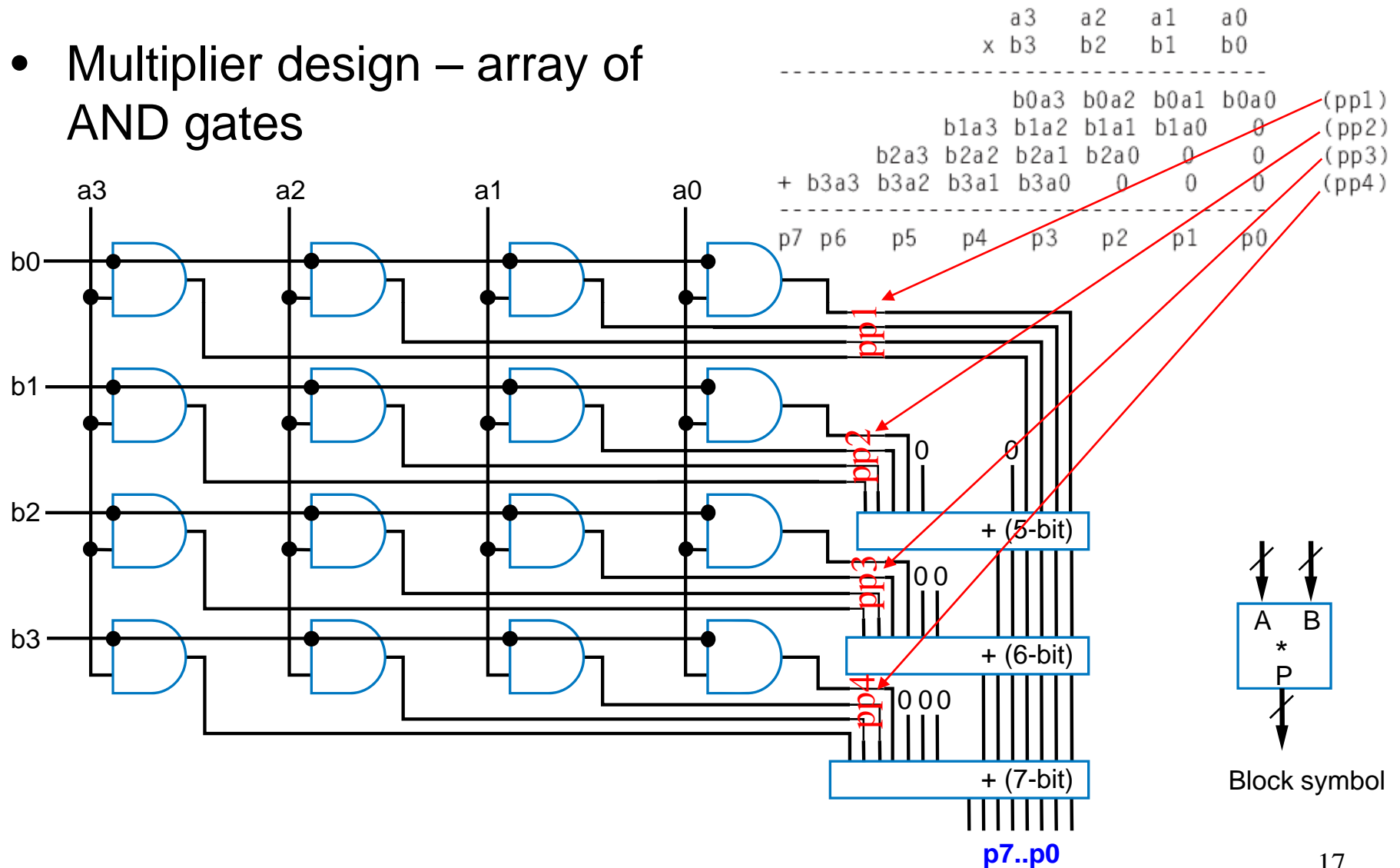

Adder/Subtractor

  - Adder/subtractor: control input determines whether add or subtract
 - Can use 2x1 mux – sub input passes either B or inverted B
 - Alternatively, can use XOR gates – if sub input is 0, B's bits pass through; if sub input is 1, XORs invert B's bits



Overflow

- Sometimes result can't be represented with given number of bits
 - Either too large magnitude of positive or negative
 - e.g., 4-bit two's complement addition of $0111 + 0001$ ($7 + 1 = 8$). But 4-bit two's complement can't represent number > 7
 - $0111 + 0001 = 1000$ WRONG answer, 1000 in two's complement is -8, not +8
 - Adder/subtractor should indicate when overflow has occurred, so result can be discarded

Detecting Overflow: Method 1

- Assuming 4-bit two's complement numbers, can detect overflow by detecting when the two numbers' sign bits are the same but are different from the result's sign bit
 - If the two numbers' sign bits are different, overflow is impossible
 - Adding a positive and negative can't exceed largest magnitude positive or negative
- Simple circuit
 - $\text{overflow} = a_3'b_3's_3 + a_3b_3s_3'$
 - Include "overflow" output bit on adder/subtractor

sign bits			
0	1	1	1
+ 0	0	0	1
<hr/>			
1	0	0	0
overflow			
(a)			
1	1	1	1
+ 1	0	0	0
<hr/>			
0	1	1	1
overflow			
(b)			
1	0	0	0
+ 0	1	1	1
<hr/>			
1	1	1	1
no overflow			
(c)			

If the numbers' sign bits have the same value, which differs from the result's sign bit, overflow has occurred.

Detecting Overflow: Method 2

- Even simpler method: Detect difference between carry-in to sign bit and carry-out from sign bit
- Yields simpler circuit: $\text{overflow} = c_3 \text{ xor } c_4$



1 1 1	0 0 0	0 0 0
0 1 1 1	1 1 1 1	1 0 0 0
+ 0 0 0 1	+ 1 0 0 0	+ 0 1 1 1
<hr/>	<hr/>	<hr/>
0 1 0 0 0	1 0 1 1 1	0 1 1 1 1
overflow	overflow	no overflow
(a)	(b)	(c)

If the carry into the sign bit column differs from the carry out of that column, overflow has occurred.

Comparators

- ***N-bit equality comparator***: Outputs 1 if two N-bit numbers are equal
 - 4-bit equality comparator with inputs A and B
 - a_3 must equal b_3 , $a_2 = b_2$, $a_1 = b_1$, $a_0 = b_0$
 - Two bits are equal if both 1, or both 0
 - $eq = (a_3b_3 + a_3'b_3') * (a_2b_2 + a_2'b_2') * (a_1b_1 + a_1'b_1') * (a_0b_0 + a_0'b_0')$
 - Recall that XNOR outputs 1 if its two input bits are the same
 - $eq = (a_3 \text{ xnor } b_3) * (a_2 \text{ xnor } b_2) * (a_1 \text{ xnor } b_1) * (a_0 \text{ xnor } b_0)$

0110 = 0111 ?

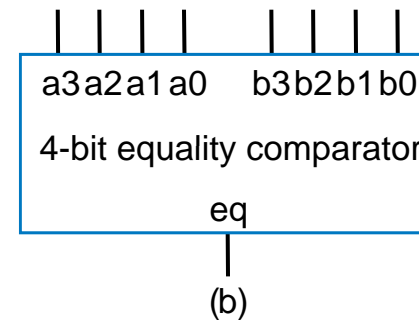 

a

Magnitude Comparator

- ***N-bit magnitude comparator:***

Indicates whether $A > B$, $A = B$, or $A < B$, for its two N-bit inputs A and B

- How design? Consider how compare by hand. First compare a_3 and b_3 . If equal, compare a_2 and b_2 . And so on. Stop if comparison not equal -- whichever's bit is 1 is greater. If never see unequal bit pair, $A = B$.

A=1011 B=1001

1011 **1**001 **Equal**

1**0**11 1**0**01 **Equal**



10**1**1 10**0**1 **Unequal**

So $A > B$

a


Magnitude Comparator

 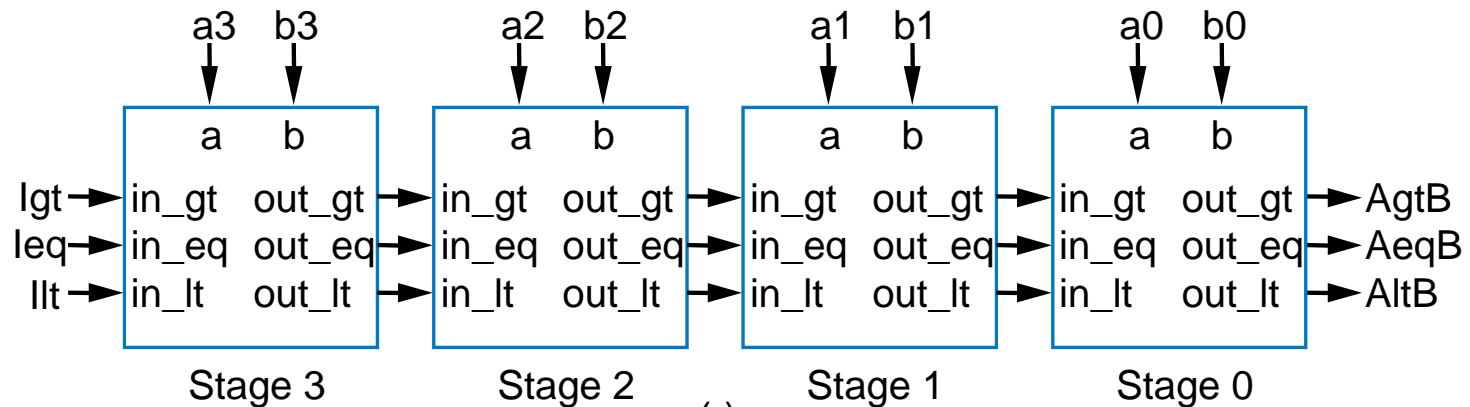- By-hand example leads to idea for design
 - Start at left, compare each bit pair, pass results to the right
 - Each bit pair called a stage
 - Each stage has 3 inputs indicating results of higher stage, passes results to lower stage



(b)


Magnitude Comparator

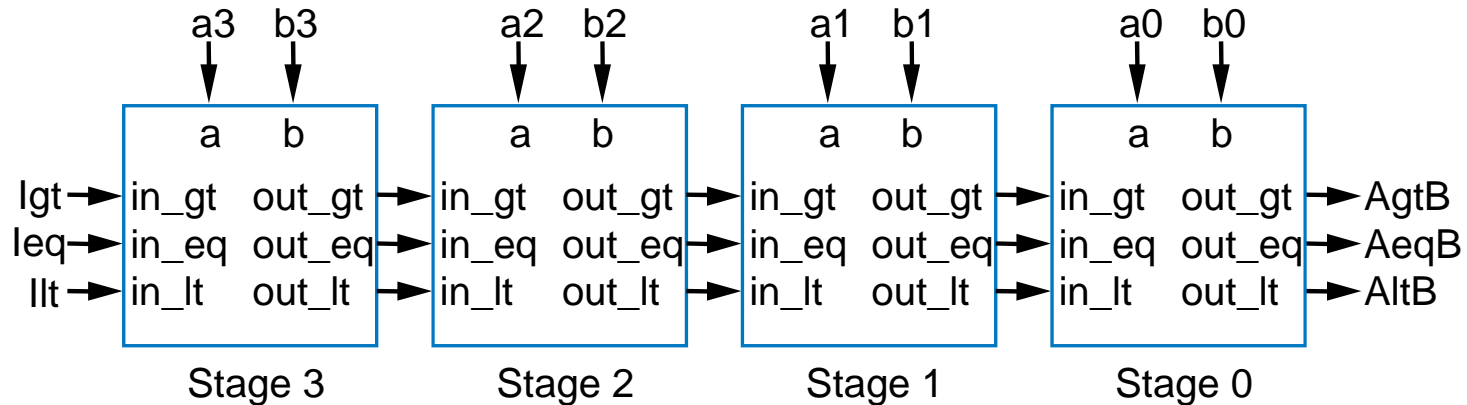

- Each stage:
 - $out_gt = in_gt + (in_eq * a * b')$
 - A > B (so far) if already determined in higher stage, or if higher stages equal but in this stage a=1 and b=0
 - $out_lt = in_lt + (in_eq * a' * b)$
 - A < B (so far) if already determined in higher stage, or if higher stages equal but in this stage a=0 and b=1
 - $out_eq = in_eq * (a \text{ XNOR } b)$
 - A = B (so far) if already determined in higher stage and in this stage a=b too
 - Simple circuit inside each stage, just a few gates (not shown)


Magnitude Comparator

- How does it work?

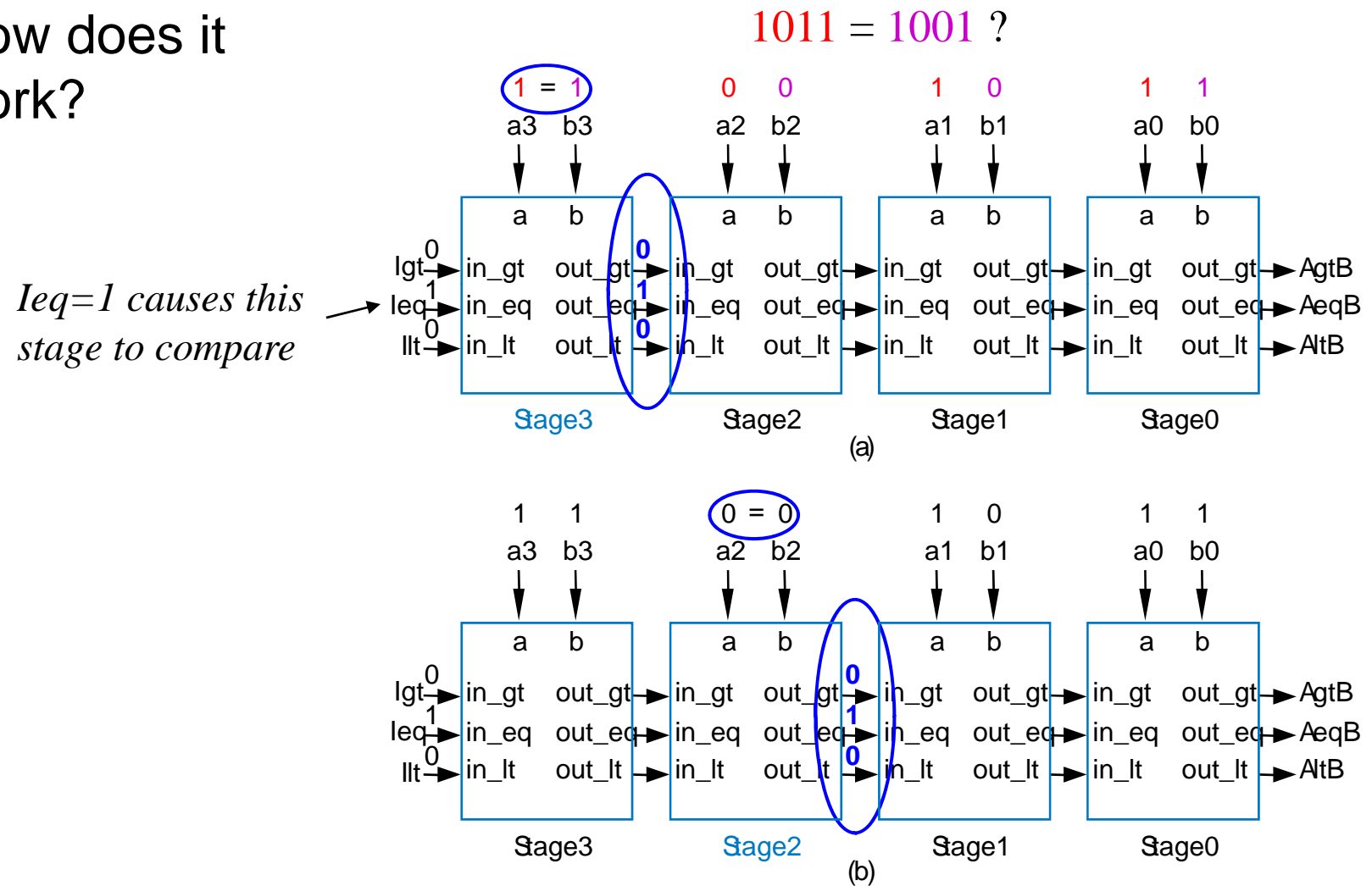


Magnitude Comparator

1011 = 1001 ?

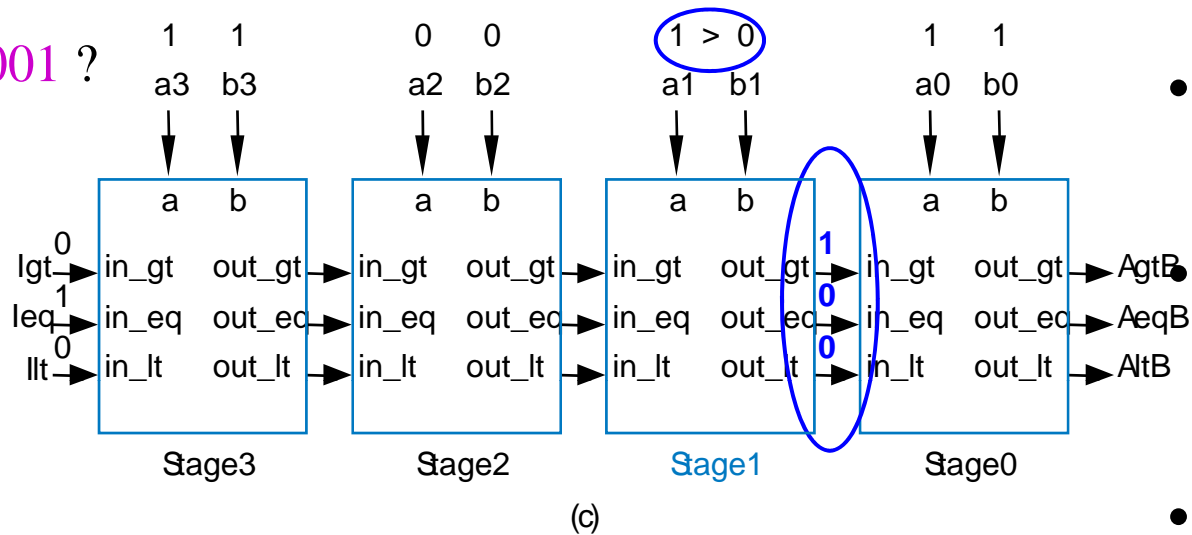



- Final answer appears on the right
- Takes time for answer to “ripple” from left to right
- Thus called “carry-ripple style” after the carry-ripple adder
 - Even though there’s no “carry” involved

a

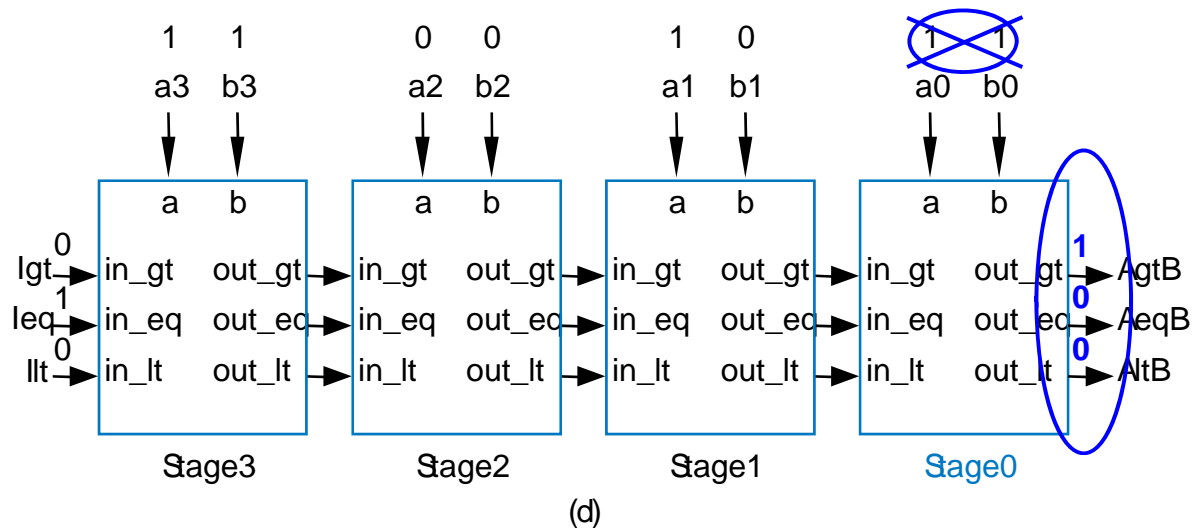


Magnitude Comparator Example: Minimum of Two Numbers

  - Design a combinational component that computes the minimum of two 8-bit numbers
 - Solution: Use 8-bit magnitude comparator and 8-bit 2x1 mux
 - If $A < B$, pass A through mux. Else, pass B.



Floating Point Addition / Subtraction

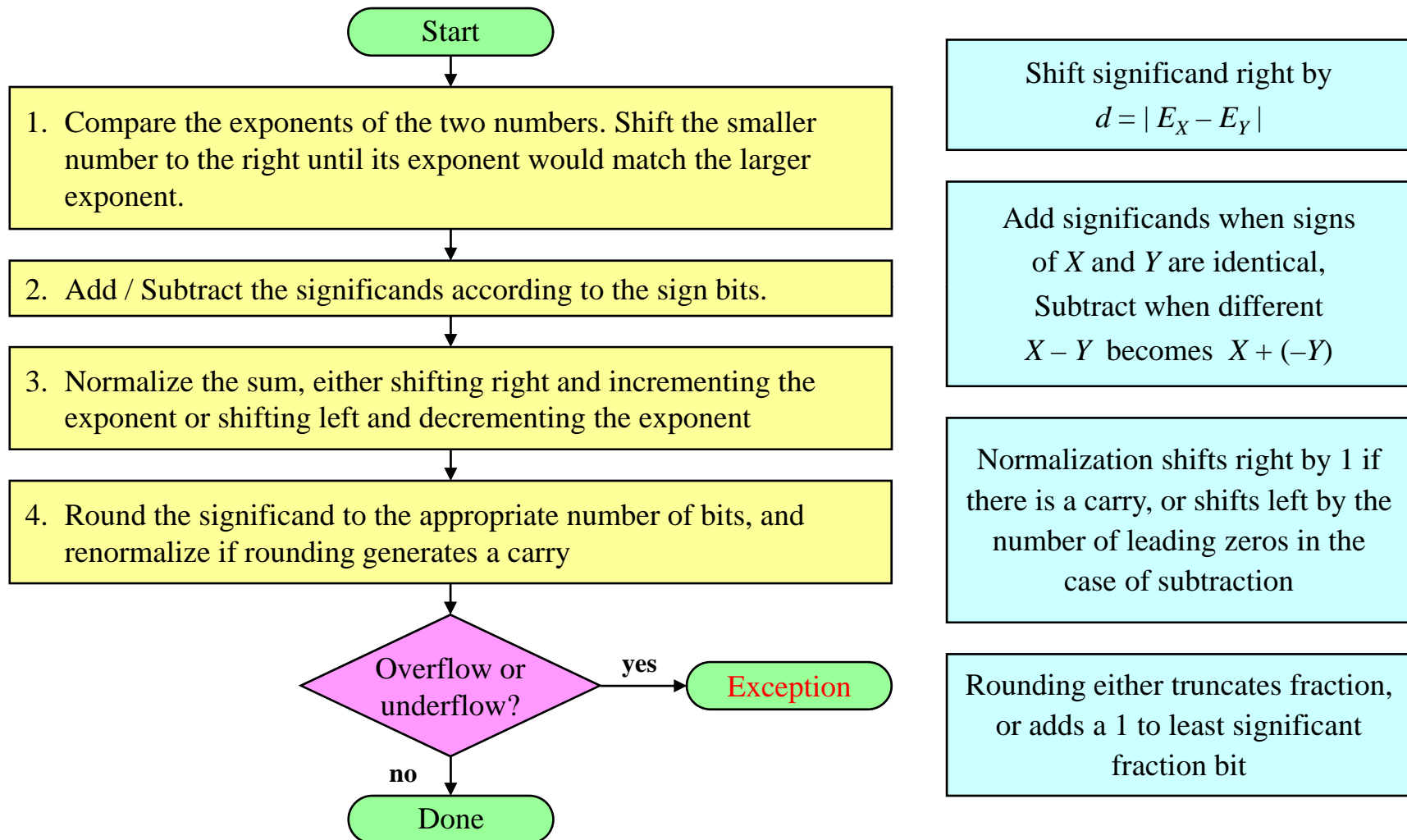

Floating Point Adder Block Diagram

